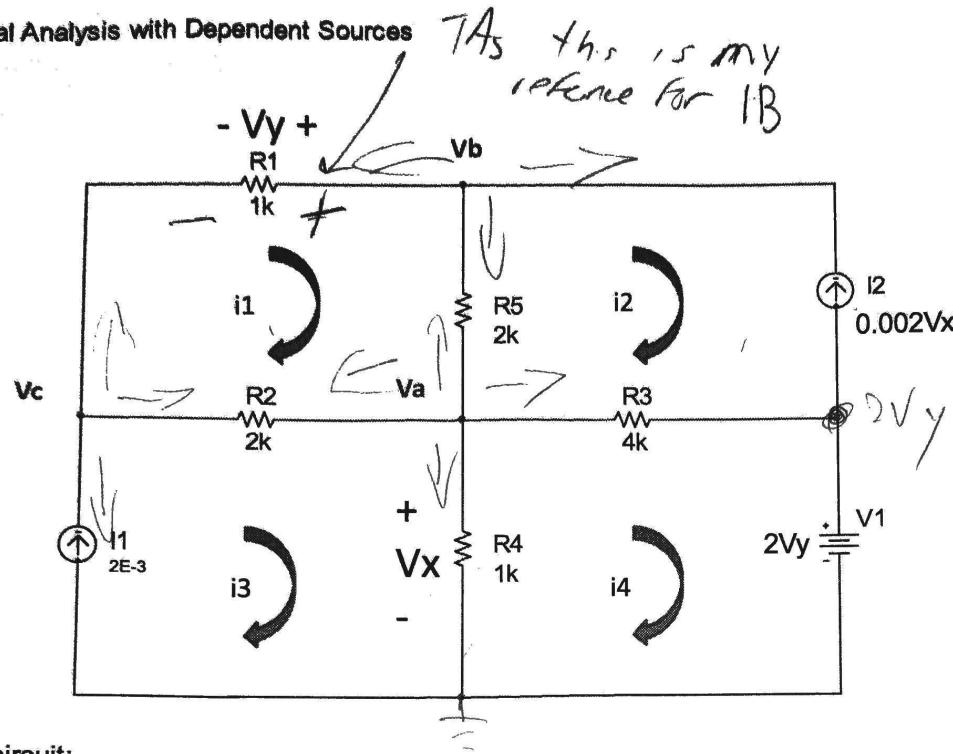


1) Mesh/Nodal Analysis with Dependent Sources



In the above circuit:

a. Use mesh analysis to determine the voltage across R_1 (V_y)

b. Verify your solution using node analysis.

$$i_1 R_1 + i_1 R_5 - i_2 R_5 + i_1 R_2 - i_3 R_2 = 0 \quad \left\{ \begin{array}{l} i_1(R_1+R_5+R_2) - i_2 R_5 - i_3 R_2 = 0 \\ i_2 + 0.002V_x = 0 \end{array} \right.$$

$$i_2 = -0.002V_x$$

$$i_3 = 2 \times 10^{-3}$$

$$i_4 R_4 - i_3 R_4 + i_4 R_3 - i_2 R_3 + 2V_y = 0$$

$$V_x = i_3 R_4 - i_4 R_4$$

$$V_y = -i_1 R_1$$

$$i_1(R_1+R_5+R_2) - i_2 R_5 - i_3 R_2 = 0$$

$$i_2 + 0.002V_x = 0$$

$$i_3 = 2 \times 10^{-3}$$

$$i_4(R_4+R_3) - i_3 R_4 - i_2 R_3 + 2V_y = 0$$

$$i_3 R_4 - i_4 R_4 - V_x = 0$$

$$-i_1 R_1 - V_y = 0$$

$$\begin{bmatrix} i_1 \\ 5000 \\ 0 \\ 0 \\ -1000 \\ -1000 \end{bmatrix} = \begin{bmatrix} i_2 \\ 2000 \\ 0 \\ 0.002 \\ 0 \\ 0 \end{bmatrix} \begin{bmatrix} V_x \\ V_y \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \quad \left\{ \begin{array}{l} i_1 \\ i_2 \\ i_3 \\ i_4 \\ V_x \\ V_y \end{array} \right. = \begin{bmatrix} 4 \\ 0 \\ 2 \\ -2 \\ 0 \\ 0 \end{bmatrix} \cdot \begin{bmatrix} 0.0019 \\ 0.0028 \\ 0.0034 \\ -1.39 \\ -1.91 \\ 0 \end{bmatrix}$$

$$V_y = -i_1 R_1$$

$$V_y = -1.913V$$

$$V_y = -VR_1$$


$$VR_1 = 1.913V$$

$$\left. \begin{array}{l}
 \text{B: } \frac{V_C - V_B}{R_1} + \frac{V_C - V_A}{R_2} - 2 \times 10^{-3} = 0 \\
 \frac{V_B - V_C}{R_1} + \frac{V_B - V_A}{R_5} - 0.002 V_x = 0 \\
 \frac{V_A - V_B}{R_5} + \frac{V_A - V_C}{R_2} + \frac{V_A}{R_4} + \frac{V_A - 2V_y}{R_3} \\
 V_B - V_C = V_y \\
 V_x = V_A
 \end{array} \right\} \quad \begin{array}{l}
 \frac{V_C + V_C - V_A - V_B}{R_1 + R_2} = 2 \times 10^{-3} \\
 \frac{V_B + V_B - V_C - V_A}{R_1 + R_5} = 0.002 V_x = 0 \\
 \frac{V_A + V_A + V_A + V_A - V_B - V_C - 2V_y}{R_5 + R_2 + R_4 + R_3} \\
 V_B - V_C - V_y = 0 \\
 \cancel{V_x} \quad V_x - V_A = 0
 \end{array}$$

$$\left[\begin{array}{cccc|c}
 V_A & V_B & V_C & V_X & V_Y \\
 \frac{-1}{2000} & \frac{-1}{1000} & \frac{3}{2000} & 0 & 0 \\
 \frac{-1}{2000} & \frac{3}{2000} & \frac{-1}{1000} & -0.002 & 0 \\
 \frac{9}{4000} & \frac{-1}{2000} & \frac{-1}{2000} & 0 & \frac{-2}{4000} \\
 0 & 1 & -1 & 0 & -1 \\
 -1 & 0 & 0 & 1 & 0
 \end{array} \right] = \left[\begin{array}{c}
 V_A \\
 V_B \\
 V_C \\
 V_X \\
 V_Y
 \end{array} \right] = \left[\begin{array}{c}
 2 \times 10^{-3} \\
 0 \\
 0 \\
 0 \\
 0
 \end{array} \right] = \left[\begin{array}{c}
 -1.39 \\
 -3.13 \\
 -1.22 \\
 -1.39 \\
 -1.91
 \end{array} \right]$$

$$\begin{aligned}
 V_B - V_C &= V_R \\
 -3.13 - (-1.22) &= -1.913 \text{ V} = VRI
 \end{aligned}$$

2) Thevenin/Norton Equivalent Circuits

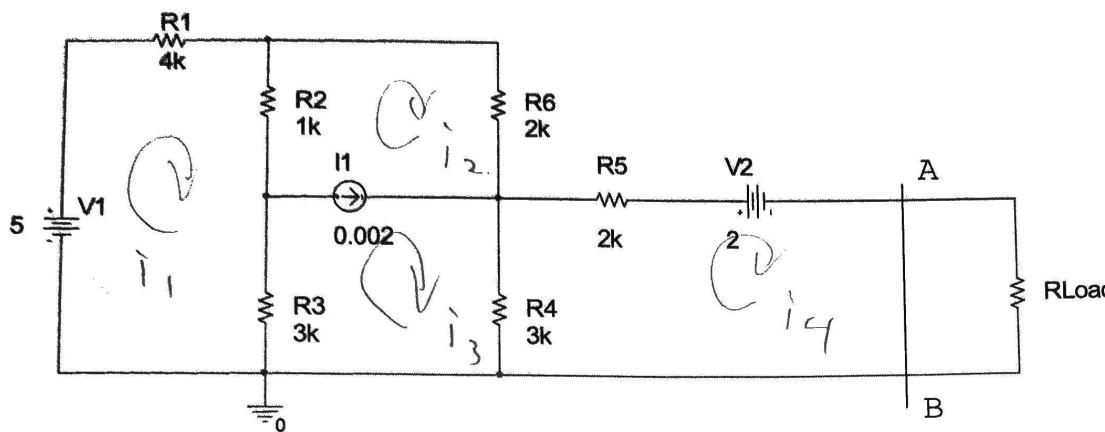

- a. Find the voltage between A and B if Rload has a resistance of $2\text{k}\Omega$.
- b. Replace Rload with an open circuit and find the voltage between A and B (V_{Thevenin}).
- c. Replace Rload with a short circuit and find the current from A to B, (I_{Norton}).
- d. Find R_{Thevenin} the resistance between A and B when looking to the left of the dashed line (Rload detached)
- e. Draw the Thevenin circuit with V_{Thevenin} , R_{Thevenin} , and R_{Load} .
- f. In this two resistor circuit, verify that when Rload is $2\text{k}\Omega$, the voltage between A and B is the same as your calculation from part a.
- g. Draw the Norton circuit, with I_{Norton} , R_{Thevenin} and R_{Load} .
- h. In this two resistor circuit, verify that when Rload is $2\text{k}\Omega$, the current through Rload is the same as your calculation from part a.

$$2A: -V_1 + i_1 R_1 + i_2 R_2 - i_2 R_L + i_1 R_3 - i_3 R_4 = 0$$

$$i_3 - i_2 = 0.002$$

$$i_2 R_2 - i_1 R_2 + i_2 R_6 + i_3 R_4 + i_3 R_4 + i_3 R_3 - i_1 R_3 = 0$$

$$i_4 R_4 - i_3 R_4 + i_4 R_5 + 2V + i_4 R_{\text{load}} = 0$$

$$\begin{aligned} V_{AB} &= V_{R_{\text{load}}} \\ &= i_4 R_{\text{load}} \\ V_{AB} &= 0.425V \end{aligned}$$

8000	-1000	-3000	0	i_1	i_2	i_3	i_4	5	0.002	0	2	9.562×10^{-4}	-8.375×10^{-4}	0.0016	2.125×10^{-4}
0	-1	1	0												
-4000	3000	6000	-3000	i_1	i_2	i_3	i_4	0	0	0	2	0	0	0	0
0	0	-3000	1000												

2 of 5

$$2B: -V_1 + i_1 R_1 + i_1 R_2 - i_2 R_2 + i_1 R_3 - i_3 R_3 = 0$$

$$i_3 - i_2 = 0.002$$

$$i_2 R_2 - i_1 R_2 + i_2 R_6 + i_3 R_4 + i_3 R_3 - i_1 R_3 = 0$$

$$\begin{bmatrix} 8000 & -1000 & -3000 \\ 0 & 1 & 1 \\ -4000 & 3000 & 8000 \end{bmatrix} \cdot \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0.002 \\ 0 \end{bmatrix} \Rightarrow \begin{bmatrix} 9.107 \times 10^{-4} \\ -9.286 \times 10^{-4} \\ 0.00107 \end{bmatrix}$$

$$V_{TH} = V_{R4} - V_2$$

$$= 3.214 \rightarrow$$

$$V_{TH} = 3.214 \checkmark$$

$$2C: -V_1 + i_1 R_1 + i_1 R_2 - i_2 R_2 + i_1 R_3 - i_3 R_3 = 0$$

$$i_3 - i_2 = 0.002$$

$$i_2 R_2 - i_1 R_2 + i_2 R_6 + i_3 R_4 - i_4 R_4 + i_3 R_3 - i_1 R_4 = 0$$

$$i_4 R_4 - i_3 R_4 + i_4 R_5 + 2V = 0$$


$$\begin{bmatrix} 8000 & -1000 & 3000 & 0 \\ 0 & 1 & 1 & 0 \\ -4000 & 3000 & 6000 & -3000 \\ 0 & 0 & -3000 & 5000 \end{bmatrix} \cdot \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 5 \\ 0.002 \\ 0 \\ -2 \end{bmatrix} \Rightarrow \begin{bmatrix} 9.807 \times 10^{-4} \\ -7.585 \times 10^{-4} \\ 0.00121 \\ 3.269 \times 10^{-4} \end{bmatrix}$$

$$i_4 = I_{AB}$$

$$I_{Norton} = 3.269 \times 10^{-4}$$

$$2D: V_{TH} = I_{Norton} R_{TH}$$

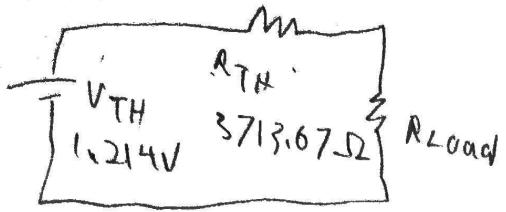
$$\frac{V_{TH}}{I_{Norton}} = R_{TH} = 3713.67 \Omega = R_{TH}$$



$$2F: V_{AB} = V_{RLoad} = \frac{V_{TH} (R_{Load})}{R_{TH} + R_{Load}}$$

$V_{AB} = 0.425V$

Verified

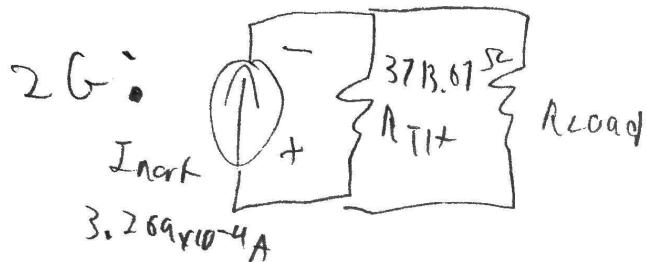


$$2H: I_{RLoad} = \frac{I_{nort} (R_{TH})}{R_{TH} + R_{Load}}$$

$I_{RLoad} = 2.125 \times 10^{-4}A$

Verified

3. Thevenin/Norton Equivalent Circuits - Dependent Sources

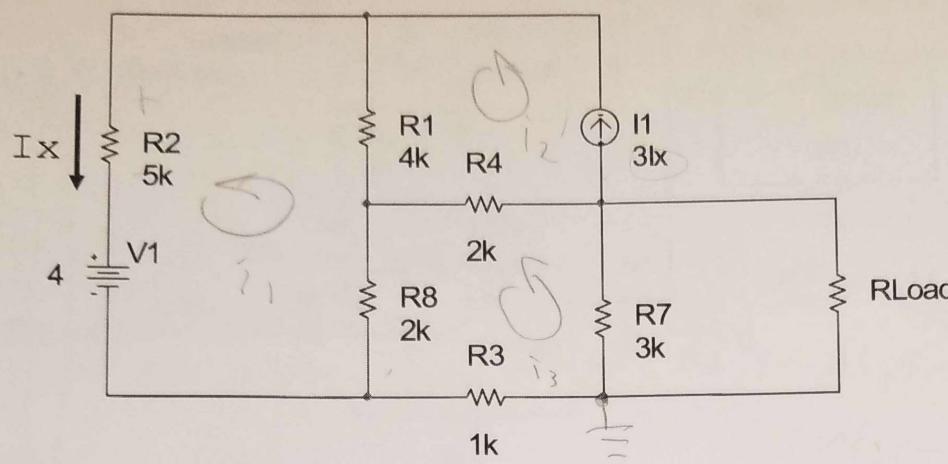a. Find V_{Thevenin} using the Open Circuit method

$$\text{3A: } \begin{aligned} i_1 &= I_x \\ i_2 &= 3I_x = 3i_1 \end{aligned}$$

b. Find I_{Norton} using the Short Circuit method

$$i_1 R_2 + 4V + i_1 R_8 - i_3 R_8 + i_1 R_1 - i_2 R_1 = 0$$

c. Find R_{Thevenin} using the test voltage/current method

$$i_3 R_4 - i_2 R_4 + i_3 R_8 - i_1 R_8 + i_3 R_3 + i_3 R_7 = 0$$

$$\left[\begin{array}{cccc} i_1 & i_2 & i_3 & I_x \\ 1 & 0 & 0 & -1 \\ -3 & 1 & 0 & 0 \\ 11000 & -4000 & -2000 & 0 \\ -2000 & -2000 & 8000 & 0 \end{array} \right] \left[\begin{array}{c} i_1 \\ i_2 \\ i_3 \\ I_x \end{array} \right] = \left[\begin{array}{c} 0 \\ 0 \\ -4 \\ 0 \end{array} \right]$$

$$\left[\begin{array}{c} 0.00133 \\ 0.004 \\ 0.00133 \\ 0.00133 \end{array} \right]$$

$$V_{TH} = VR_7$$

$$= i_3 R_7$$

$$V_{TH} = 4V$$

3B:

$$i_1 = I_x$$

$$i_2 = 3I_x = 3i_1$$

$$i_1 R_2 + 4V + i_1 R_8 - i_3 R_8 + i_1 R_1 - i_2 R_1 = 0$$

$$i_3 R_4 - i_2 R_4 + i_3 R_8 + i_3 R_3 + i_3 R_7 - i_4 R_7 = 0$$


$$i_4 R_7 - i_3 R_7 = 0$$

$$\left[\begin{array}{cccc} 1 & 0 & 0 & -1 \\ -3 & 1 & 0 & 0 \\ 11000 & -4000 & -2000 & 0 \\ -2000 & -2000 & 8000 & 0 \\ 0 & 0 & -3000 & 0 \end{array} \right] \left[\begin{array}{c} i_1 \\ i_2 \\ i_3 \\ i_4 \\ I_x \end{array} \right] = \left[\begin{array}{c} 0 \\ 0 \\ -4 \\ 0 \\ 0 \end{array} \right]$$

$$\left[\begin{array}{c} 9.52 \times 10^{-4} \\ 0.0028 \\ 0.0015 \\ 9.52 \times 10^{-4} \\ 0.0015 \end{array} \right]$$

$$i_4 = \boxed{I_{Norton} = 0.001524 A}$$

30:

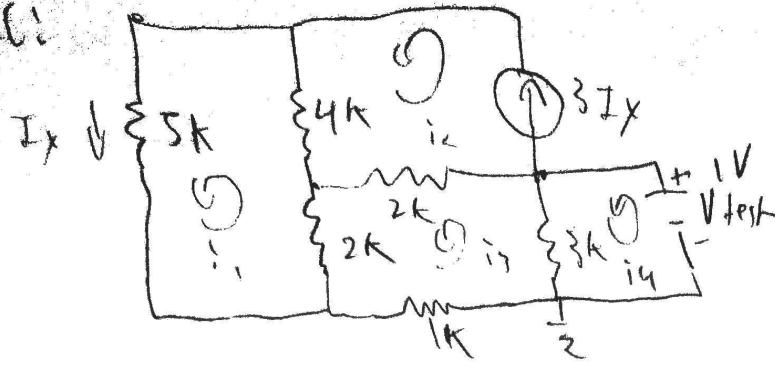

$$i_1 = I_x$$

$$i_2 = 3I_x = 3i_1$$

$$i_1 1K - i_3 2K - i_2 2K = 0$$

$$i_3 3K - i_1 2K - i_2 2K - i_4 3K = 0$$

$$i_4 3K - i_3 3K = 1$$

$$\begin{bmatrix} -9.52 \times 10^{-5} \\ -2.85 \times 10^{-4} \\ 4.76 \times 10^{-5} \\ 3.8 \times 10^{-4} \\ -9.52 \times 10^{-5} \end{bmatrix}$$

$$i_4 = I_{\text{test}}$$

$$= 3.8095 \times 10^{-4} \text{ A}$$

$$\left[\begin{array}{ccccc} i_1 & i_2 & i_3 & i_4 & I_x \\ 1 & 0 & 0 & 0 & -1 \\ 0 & 1 & 0 & 0 & 0 \\ 1(000) & 4(000) & -2(000) & 0 & 0 \\ -2(000) & -2(000) & 8(000) & -3(000) & 0 \\ 0 & 0 & -3(000) & 3(000) & 0 \end{array} \right] \left[\begin{array}{c} i_1 \\ i_2 \\ i_3 \\ i_4 \\ I_x \end{array} \right] = \left[\begin{array}{c} 0 \\ 0 \\ 0 \\ 0 \\ 1 \end{array} \right]$$

$$\frac{V_{\text{test}}}{I_{\text{test}}} = R_{TH} = \frac{1}{3.8095 \times 10^{-4}} = 2625.003 \Omega$$


$$\text{Verify: } \frac{V_{TH}}{I_{\text{test}}} = R_{TH}$$

I_{test}

$$\frac{4}{0.001924} = 2625 \Omega$$

R_{TH} is verified

4. Amplifier Circuits

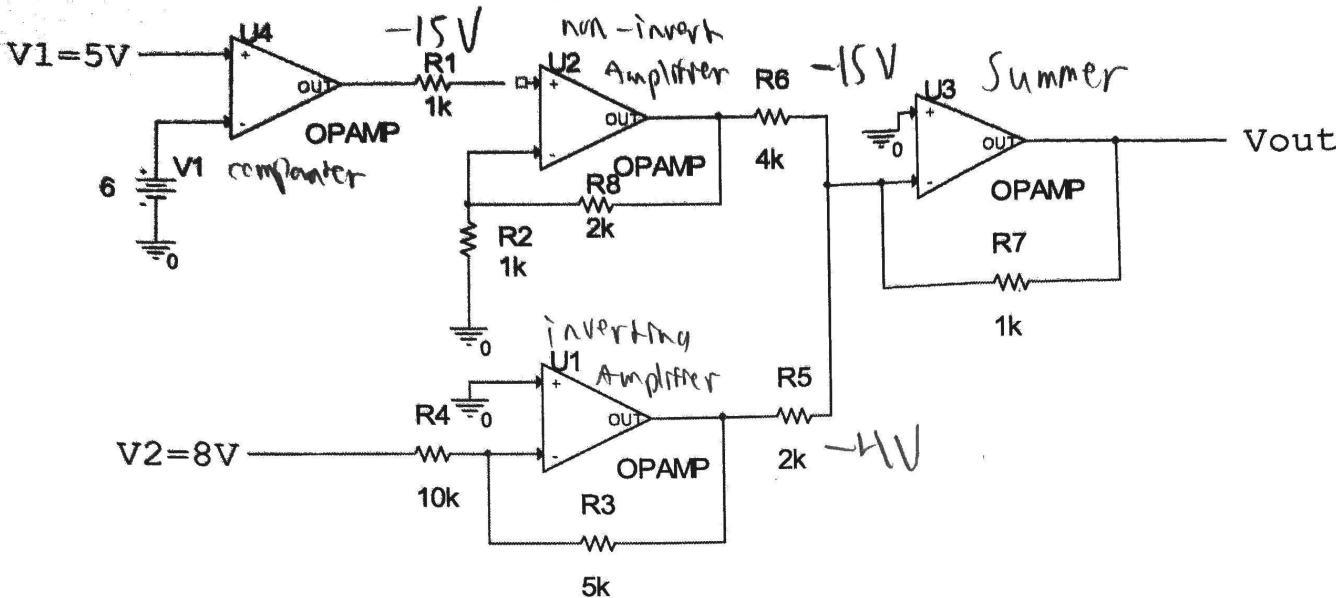R1 should be attached to U2....

- a. For the above circuit, determine the output voltage, V_{out} . The voltages supplied to the op-amps are 15V and -15V, as appropriate.

$$V_{at R_6} = \left(\frac{R_8}{R_2} + 1 \right) - 15 \text{ V}$$

$$\left(\left(\frac{2}{1} \right) + 1 \right) - 15 \text{ V}$$

$$-15 \cdot 3 = V_{at R_6}$$

$$-45 =$$

↓
WRT

$$-15V = V_{at R_6}$$

$$V_{at R_5} = -\frac{R_3}{R_4} 8 \text{ V}$$

$$= -\frac{5}{10} 8 \text{ V}$$

$$= -\frac{1}{2} 8 \text{ V}$$

$$V_{at R_5} = -4 \text{ V}$$

$$V_{out} = -\frac{1k}{2k} (-4V) - \frac{1k}{4k} (-15V)$$

$$2V + \frac{15V}{4}$$

$$2V + 3.75V =$$

$5.75V = V_{out}$

5. Amplifier Circuits: Design

a. Design a two stage amplifier such that the output of the first stage is $V_1 = -5V_{in}$ and the output of the second stage is $V_{out} = -4V_1$

b. Design an amplifier circuit with three inputs (V_1 , V_2 , and V_3) such that $V_{out} = V_1 - 2V_2 - 4V_3$

