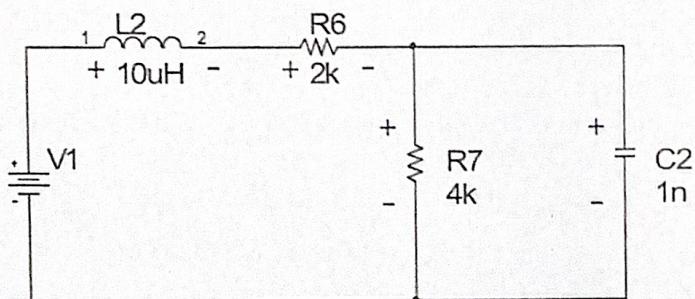


NAMES

Jamara Puskarevic
Joseph DeGraetano
Saif Ahmed
Jayson Mintz

1)





In the above circuit, the current is defined as follows:

$$V_1 = \begin{cases} 30 & t < 0 \\ 0 & 0 < t \end{cases} \quad (\text{the voltage source turns off at } t = 0)$$

- a. At $t = 0^-$ (just before the voltage changes), for the polarities indicated in the circuit, determine the voltage across each component and the current through each component.

	Voltage	Current
R6	10V	5mA
R7	20V	5mA
L2	0V	5mA
C2	20V	0A

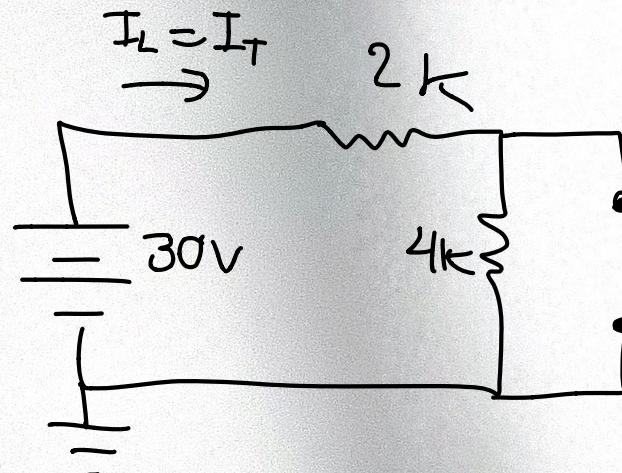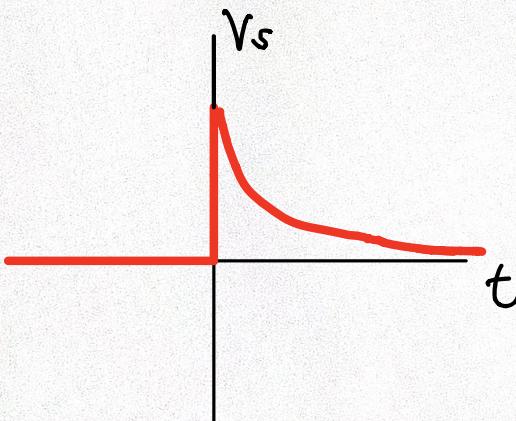

$$R_T = 2+4 = 6 \text{ k}\Omega$$

$$I_T = I_L = \frac{V_T}{R_T} = \frac{30V}{6k\Omega} = 5mA$$


$$V_{R_6} = 2k \cdot 5m = 10V$$

$$V_{R_7} = 4k \cdot 5m = 20V$$

$$V_{C_2} = V_{R_7} = 20V$$



- b. At $t = 0^+$ (just after the voltage changes), for the polarities indicated in the circuit, determine the voltage across each component and the current through each component.

	Voltage	Current
R6	10V	5mA
R7	20V	5mA
L2	0V	5mA
C2	20V	0A

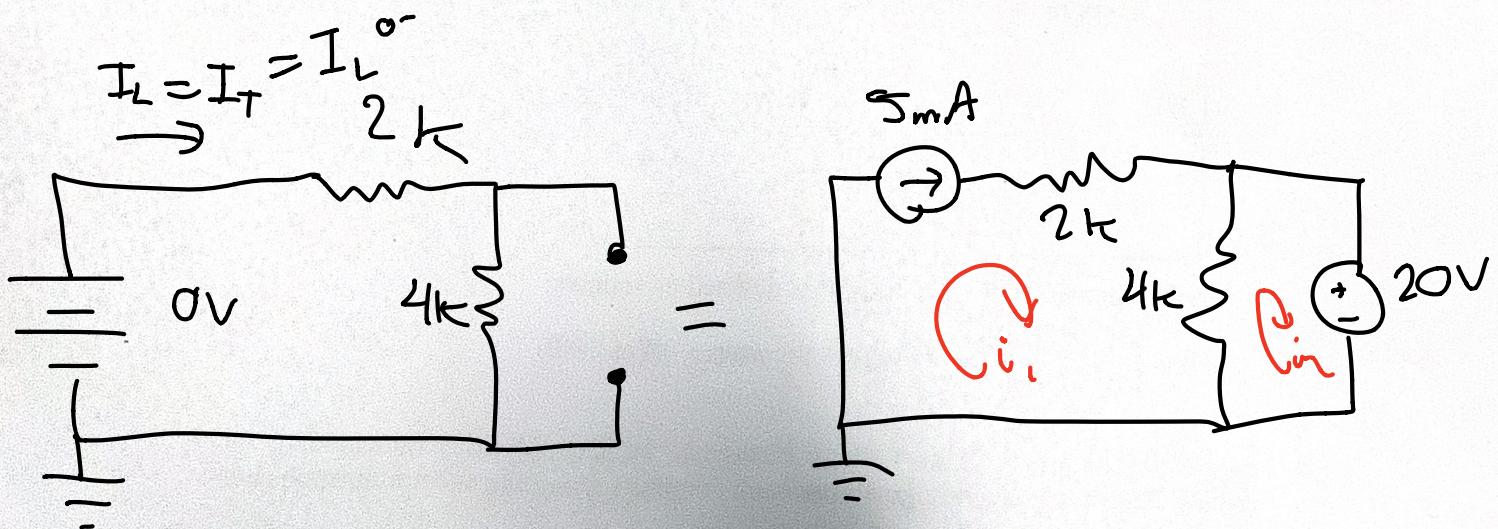

$$\left. \begin{array}{l}
 N_1) i_1 = 5 \text{ mA} \\
 i_2 R_7 - i_1 R_7 + 20V = 0 \\
 -20 = 4k (i_2 - 5 \text{ mA}) \\
 -5 \text{ mA} = i_2 - 5 \text{ mA} \\
 i_2 = 0
 \end{array} \right\} \begin{array}{l}
 I_{R_G} = I_{R_7} = i_1 = 5 \text{ mA} \\
 V_{R_G} = I_{R_G} \cdot R_G = 10V \\
 V_{R_7} = I_{R_7} \cdot R_7 = 20V
 \end{array}$$

2)

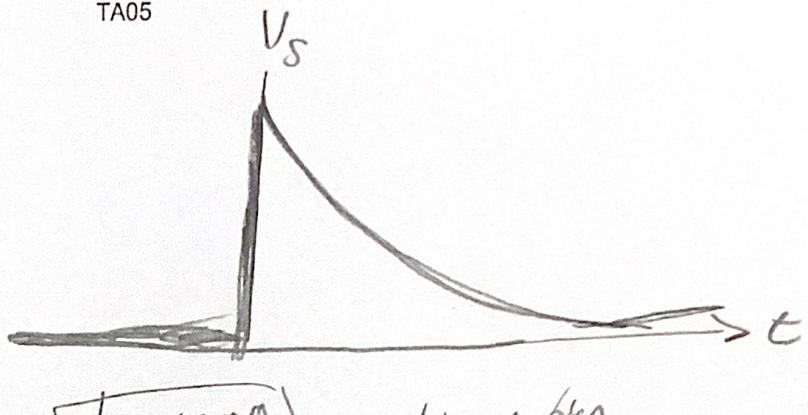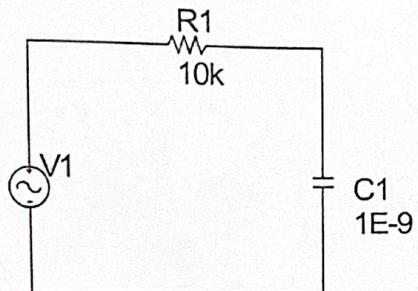

$$K = 1000 \quad \leftarrow \text{abbreviation}$$

Determine the voltage V_{C1} as a function of time for a source voltage

$$V_s = \begin{cases} 0 & t < 0 \\ 5 \exp(-5E4t) & 0 < t \end{cases} \quad V_c(t) = A_1 e^{-\frac{t}{T}} + A_2 e^{-50kt}$$

$$T = RC = 10k \cdot 10000(1E-9) = 1 \cdot \frac{10^4}{10^{10}} = 1 \cdot 10^{-5}$$

$$T = 10^5$$

$$V_c(t) = A_1 e^{-10^5 t} + A_2 e^{-50kt}$$

$$V_c(0^-) = 0 = V_c(0^+)$$

$$V_c(0^+) = 0 = A_1 e^{-0} + A_2 e^{-0} = A_1 + A_2$$

$$RC \frac{dV_{CF}}{dt} + V_{CF} = V_s$$

$$RC \cdot \frac{d(A_2 e^{-50kt})}{dt} + A_2 (e^{-50kt}) = 5 e^{-50kt}$$

$$10^{-5} \cdot (-50kt) A_2 e^{-50kt} + A_2 (e^{-50kt}) = 5 e^{-50kt}$$

$$(1 - 0.5) A_2 = 0.5 A_2 = 5$$

$$\hookrightarrow A_2 = 10$$

$$\rightarrow 0 = A_1 + 10 \rightarrow A_1 = -10$$

$$\rightarrow V_c(t) = (-10) e^{-10^5 t} + 10 e^{-50000 t}$$