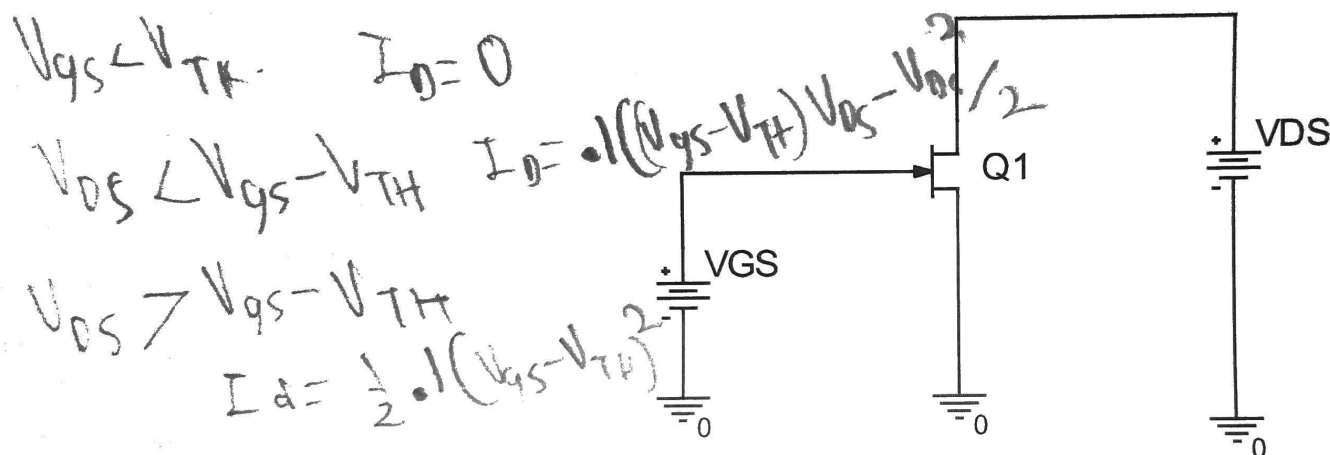


## Homework 10

Reading: 5.1-5.7


Problem1) I-V characteristics, simple biasing



The above NMOSFET has a threshold voltage of  $V_{TH} = 2.5V$  and  $K_n = 100\text{mA/V}^2$

- Use a program (Matlab, Excel, or any other tool) to plot  $I_D$ - $V_{GS}$  for  $0 < V_{GS} < 6V$  when  $V_{DS} = \{1V, 2.5V, 2V\}$  (three plots). The plots should be on the same set of axis. For each plot clearly indicate the regions where the FET is off, in Triode and in saturation. On each plot, identify  $V_{GS}$  voltage when at the off-saturation and saturation-triode transitions for the FET. (Note, this plot should be comparable to pre-lab 3.1.)
- Use a program (Matlab, Excel, or any other tool) to plot  $I_D$ - $V_{DS}$  for  $0 < V_{DS} < 6V$  when  $V_{GS} = \{2.75V, 3.0V, 2.25V\}$  (three plots). The plots should be on the same set of axis. For each plot clearly indicate the regions where the FET is in Triode and in saturation. On each plot indicate the  $V_{DS}$  voltage when the FET transitions from Triode to saturation.

## Problem 2) Basic biasing

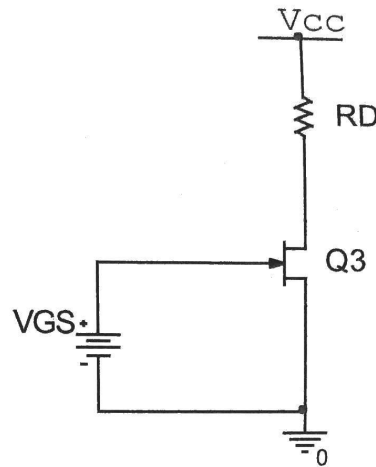

For the above circuit,  $V_{TN} = 2.5V$  and  $K_n = 100\text{mA/V}^2$

- When  $V_{GS} = 3V$  and  $V_{CC} = 15V$ , determine the range of resistor values,  $R_D$ , such that the transistor is in saturation.
- When  $V_{GS} = 3V$  and  $R_D = 500\Omega$ , determine the range of values for  $V_{CC}$  such that the transistor is in saturation.
- When  $V_{CC} = 10V$  and  $R_D = 500\Omega$ , determine the range of values of  $V_{GS}$  for each of the three regions of operation (off, Triode, saturation).

$$A: V_{CC} - V_{RD} > 0.5V$$

$$I_D = (0.5)(0.5)^2 = 0.0125$$

$$R_D \cdot I_D < 14.5V$$

$$R_D < 1160$$

$$R_D < 1160 \Omega$$

$$B: -(R_D \cdot I_D) > 0.5V - V_{CC}$$

$$-6.25 > 0.5V - V_{CC}$$

$$V_{CC} > 6.75V$$

$$C: \text{off} = V_{GS} < 2.5V$$

Confirmed on next page.

Saturation:  $I_D = 0.5 \cdot 1 (V_{GS} - 2.5)^2$   $V_{CC} - R_D \cdot I_D > V_{GS} - 2.5$

$$10 - 500(0.5 \cdot 1 (V_{GS} - 2.5)^2) - V_{GS} + 2.5 > 0$$

$$12.5 - 25(V_{GS} - 2.5)^2 - V_{GS} > 0$$

$$12.5 - 25V_{GS}^2 + 124V_{GS} - 156.25 > 0$$


$$(V_{GS} - 3.113) (\cancel{V_{GS} - 1.847}) > 0$$

$$2.5V < V_{GS} < 3.113V$$

Triode:  $V_{GS} > V_{GS,sat} \rightarrow V_{GS} > 3.113V$

## ID-VGS

## Problem 1 A

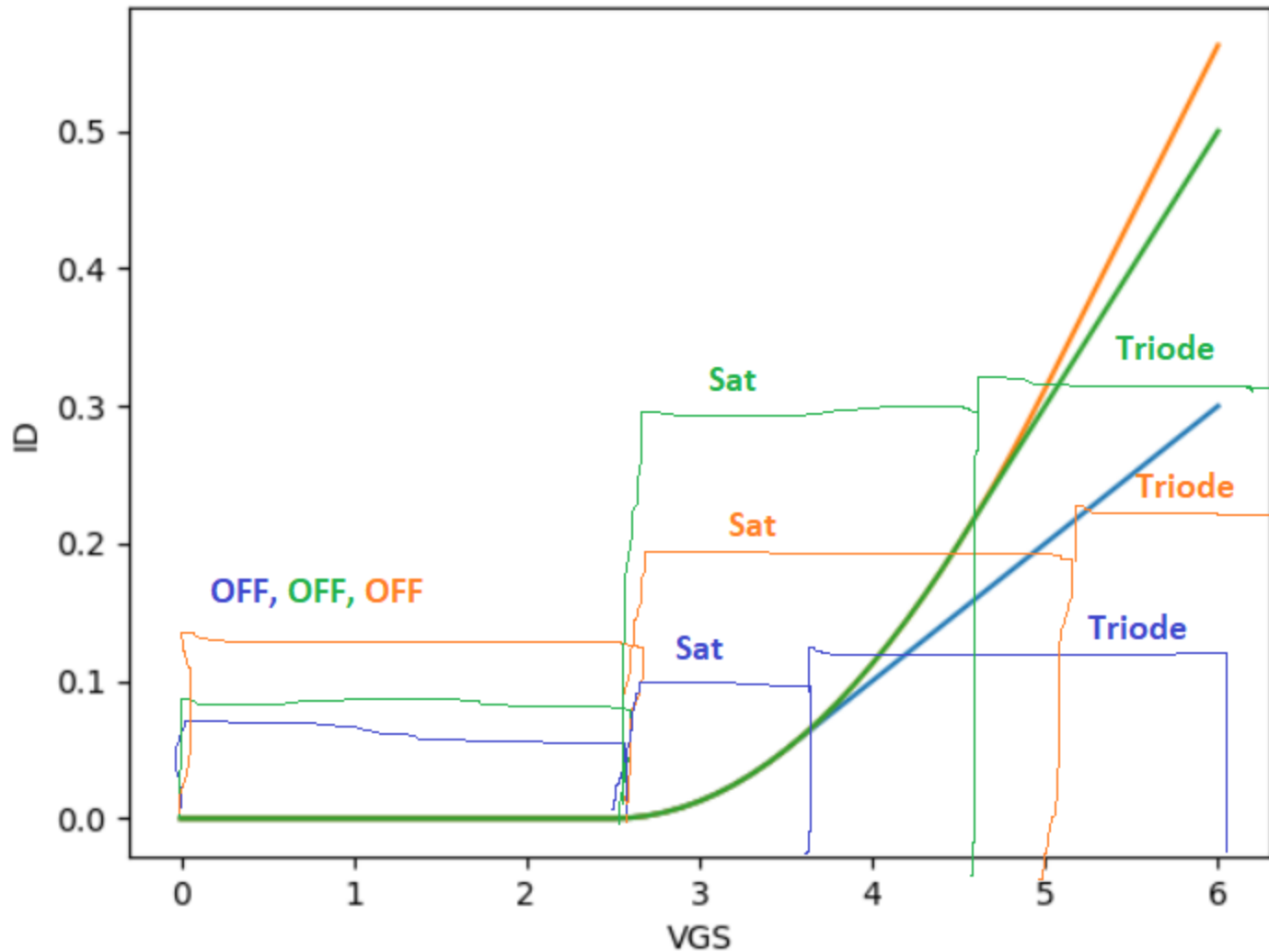

Blue :  $V_{DS} = 1V$

Orange:  $V_{DS} = 2.5V$

Green:  $V_{DS} = 2V$

Blue Plot:

Off  $\rightarrow$  Sat = 2.5V

Sat  $\rightarrow$  Tri = 3.5V

Orange Plot:

Off  $\rightarrow$  Sat = 2.5V

Sat  $\rightarrow$  Tri = 5V


Green Plot:

Off  $\rightarrow$  Sat = 2.5V

Sat  $\rightarrow$  Tri = 4.5V

## ID-VDS

## Problem 1 B

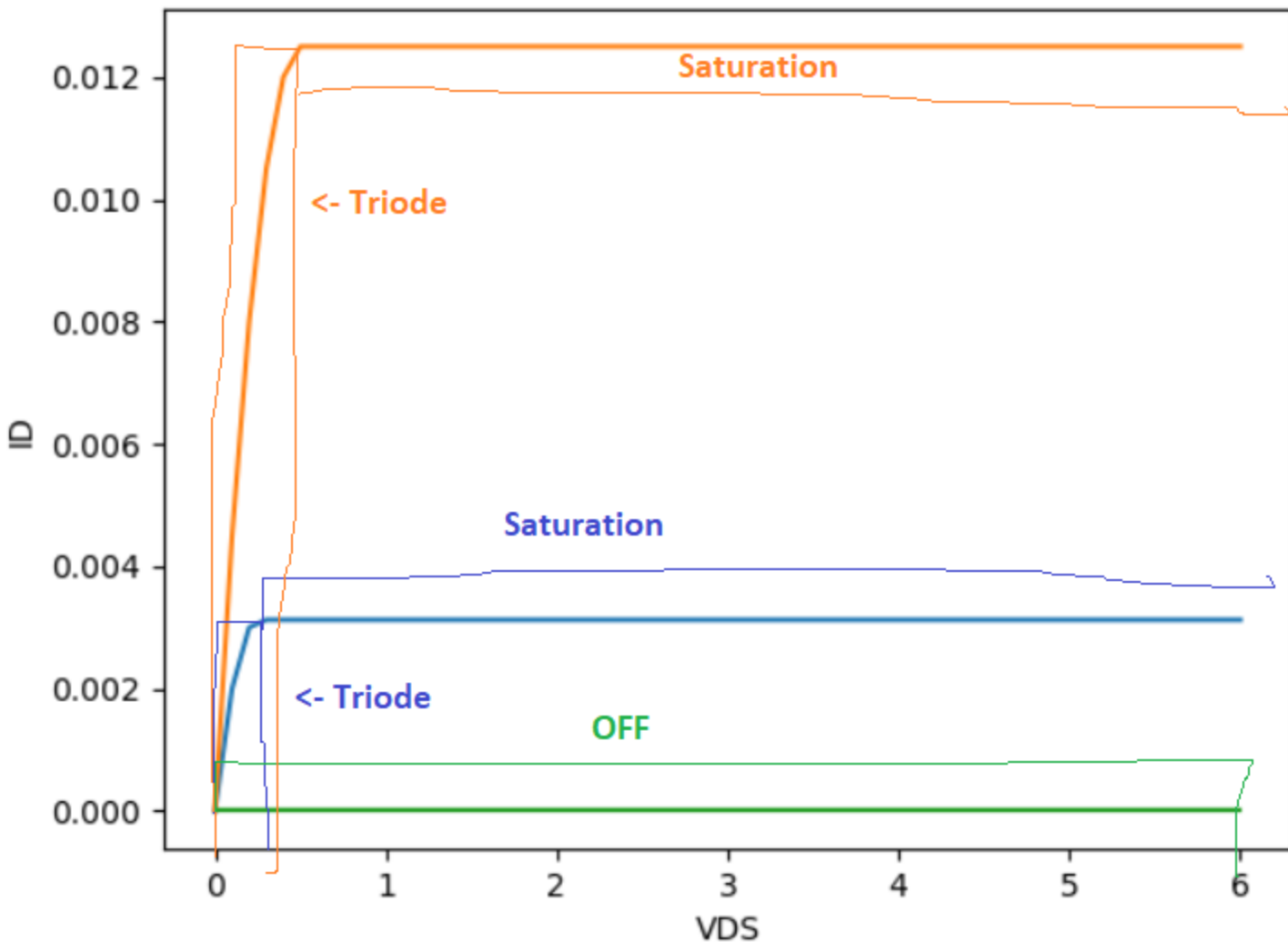

Blue:  $V_{GS} = 2.75V$

Orange:  $V_{GS} = 3V$

Green:  $V_{GS} = 2.25V$

Blue Plot:

Triode  $\rightarrow$  Sat = 0.25V

Orange Plot:

Triode  $\rightarrow$  Sat = 0.5V

Green Plot:

Triode  $\rightarrow$  Sat : Never

```

#IE HW 10 Prob 1 A

from matplotlib import pyplot as plt
import numpy as np

vgs = np.arange(0, 6.1, 0.1)

vg = 0
vds = 1
id = []
id2 = []
id3 = []
vtn = 2.5
kn = 0.1
while vg < 6:
    if vg < vtn:
        id.append(0)
    else:
        if vds < (vg - vtn):
            print("vgs triode", vg)
            current = kn * ((vg - vtn) * vds - vds ** 2 / 2);
            id.append(current)

        else:
            print("vgs saturation", vg)
            current = kn * (vg - vtn) ** (2) / 2
            id.append(current)
    vg += 0.1

print("next set of values vd = 2.5")
vg = 0
vds = 2.5
while vg < 6:
    if vg < vtn:
        id2.append(0)
    else:
        if vds < (vg - vtn):
            print("vgs triode", vg)
            current = kn * ((vg - vtn) * vds - vds ** 2 / 2);
            id2.append(current)

        else:
            print("vgs saturation", vg)
            current = kn * (vg - vtn) ** (2) / 2
            id2.append(current)
    vg += 0.1

print("next set of values vd = 2")
vg = 0
vds = 2
while vg < 6:
    if vg < vtn:
        id3.append(0)
    else:
        if vds < (vg - vtn):

```

```
        print("vgs triode", vg)
        current = kn * ((vg - vtn) * vds - vds ** 2 / 2);
        id3.append( current)

    else:
        print("vgs saturation", vg)
        current = kn * (vg - vtn) ** (2) / 2
        id3.append(current)
    vg+= 0.1

plt.plot(vgs,id)
plt.plot(vgs, id2)
plt.plot(vgs, id3)
plt.xlabel("VGS")
plt.ylabel("ID")
plt.title('ID-VGS')
plt.show()
```

```

#IE HW 10 Prob 1 B

from matplotlib import pyplot as plt
import numpy as np

vds = np.arange(0, 6.1, 0.1)

vd = 0
vgs = 2.75
id = []
id2 = []
id3 = []
vtn = 2.5
kn = 0.1
while vd < 6:
    if vgs < vtn:
        id.append(0)
    else:
        if vd < (vgs - vtn):
            print("vds triode", vd)
            current = kn * ((vgs - vtn) * vd - vd ** 2 / 2);
            id.append(current)

        else:
            print("vds saturation", vd)
            current = kn * (vgs - vtn) ** (2) / 2
            id.append(current)
        vd += 0.1

print("next set of values vgs = 3.0")

vd = 0
vgs = 3
while vd < 6:
    if vgs < vtn:
        id2.append(0)
    else:
        if vd < (vgs - vtn):
            print("vds triode", vd)
            current = kn * ((vgs - vtn) * vd - vd ** 2 / 2);
            id2.append(current)

        else:
            print("vds saturation", vd)
            current = kn * (vgs - vtn) ** (2) / 2
            id2.append(current)
        vd += 0.1

print("next set of values vgs = 2.25")

vd = 0
vgs = 2.25
while vd < 6:
    if vgs < vtn:

```



```

        id3.append(0)
    else:
        if vd < (vgs- vtn):
            print("vds triode", vd)
            current = kn * ((vgs - vtn) * vd - vd ** 2 / 2);
            id3.append( current)

        else:
            print("vds saturation", vd)
            current = kn * (vgs - vtn) ** (2) / 2
            id3.append(current)
    vd+= 0.1

plt.plot(vds,id)
plt.plot(vds, id2)
plt.plot(vds, id3)
plt.xlabel("VDS")
plt.ylabel("ID")
plt.title('ID-VDS')
plt.show()

```