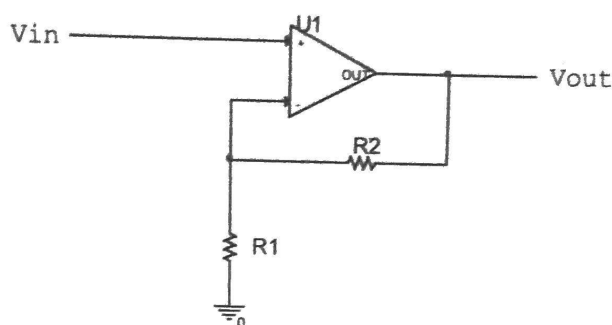



Homework 4

Reading: Chapter 2.5-2.8

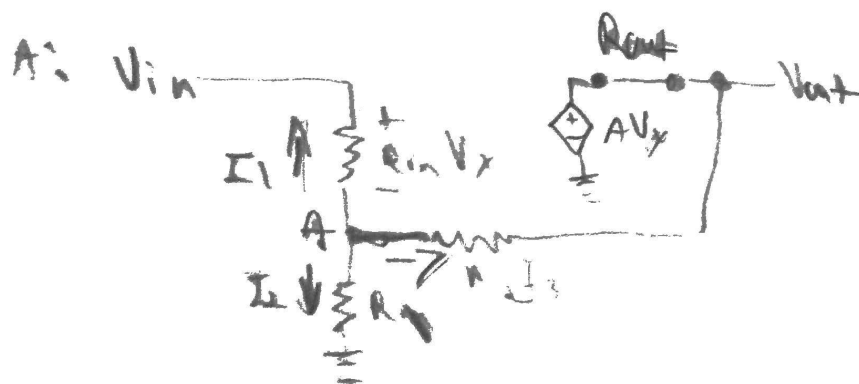1) Finite Gain



- Redraw the circuit, replacing the op-amp (not the dashed box) itself with the ideal op-amp dependent source model ($R_{in} \rightarrow \infty$, $R_{out} \rightarrow 0$, and $A_{internal} \rightarrow \infty$).
- Use circuit analysis to determine the relationship between the input and output voltages in terms of R_1 , R_2 , and $A_{internal}$.
- Given the part b result, for an internal op-amp gain of 10^6 and $R_1 = 1k\ \Omega$, what value of R_2 results in the overall gain, V_{out}/V_{in} , being reduced to 90% of its ideal value.
- Given your part c result, why is the internal gain of the op-amp unlikely to affect the non-inverting amplifier gain under typical usage?



$$I_1 + I_2 + I_3 = 0$$

$$0 = \frac{V_a}{R_1} + \frac{V_a - V_{out}}{R_2} = 0$$

$$V_{out} = A(V_{in} - V_a) = A(V_{in} - V_a)$$

$$V_{out} = AV_{in} - AV_a$$

$$\frac{(V_{out} - AV_{in})}{A} = -V_a$$

$$\frac{-V_{out} + AV_{in}}{A \cdot R_1} + \frac{-V_{out} + AV_{in}}{R_2 \cdot A} - \frac{V_{out}}{R_2} = 0$$

$$\frac{-V_{out}}{A \cdot R_1} + \frac{V_{in}}{R_1} - \frac{V_{out}}{R_2 \cdot A} + \frac{V_{in}}{R_2} - \frac{V_{out}}{R_2} = 0$$

$$V_{in} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = V_{out} \left(\frac{1}{A \cdot R_1} + \frac{1}{A \cdot R_2} + \frac{1}{R_2} \right)$$

$$B: \frac{V_{out}}{V_{in}} = \frac{A(R_1 + R_2)}{R_1 + R_2 + AR_1}$$


$$1C: .9 \frac{V_{out}}{V_{in}} = \frac{10^8 (1K + R_2)}{1K + R_2 + 10^9} = .9 \left(1 + \frac{R_2}{R_1} \right)$$

$$R_2 = 1.11 \times 10^8$$


D: To get .9 of the expected ratio you need 10^9 ohms which is functionally open circuit which isn't common.

2) Common mode and differential mode input resistance. Assume the op-amps are ideal.


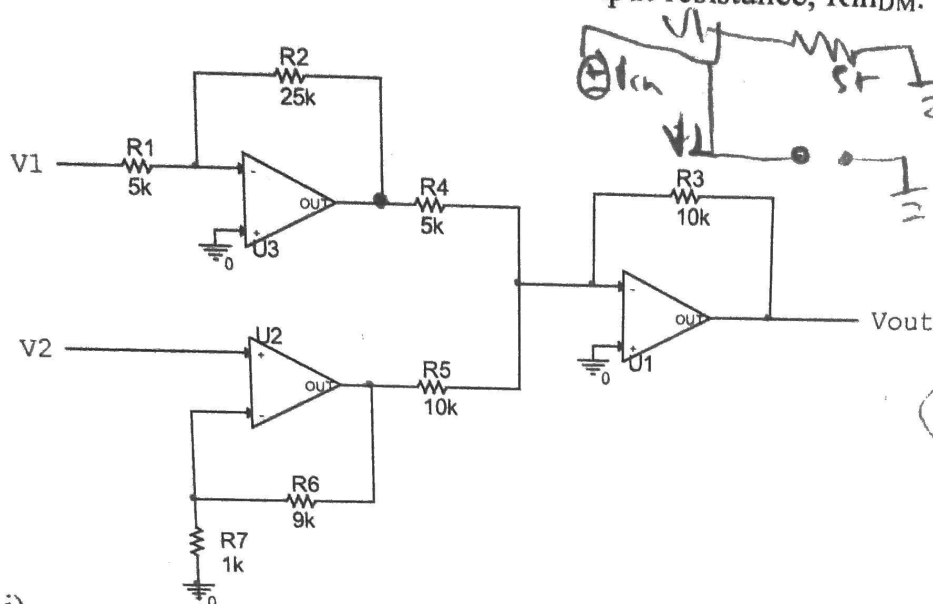
a) For the two opamp circuits from Homework 2, using methods similar to those used with the difference amplifier, determine the common mode input resistance, R_{inCM} , and the differential mode input resistance, R_{inDM} .




i)

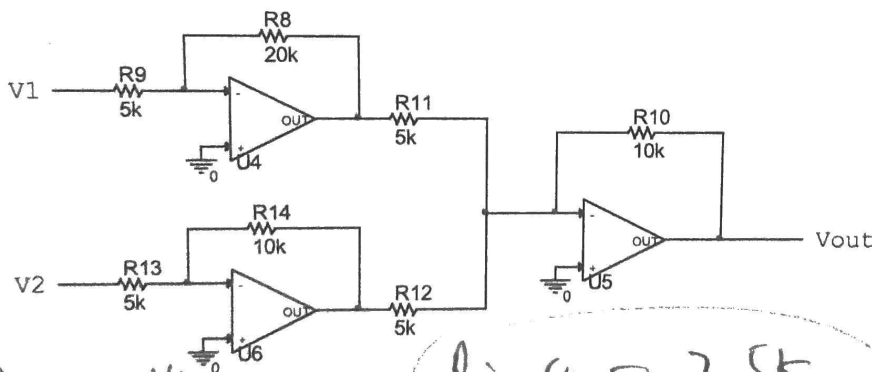

ii)

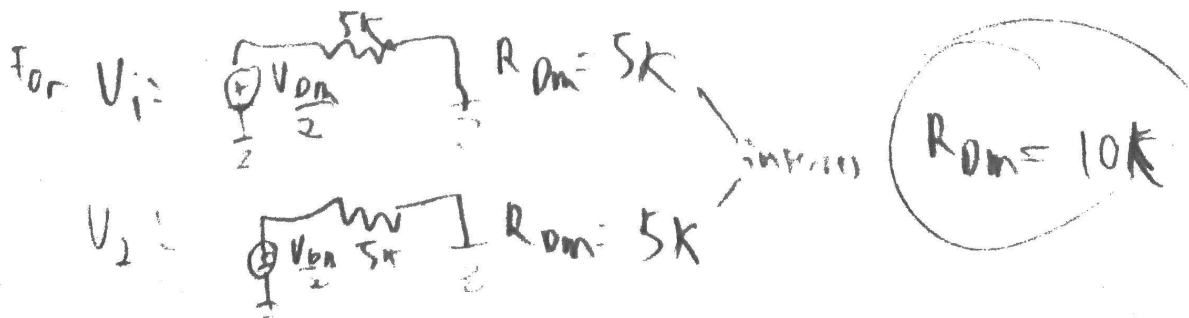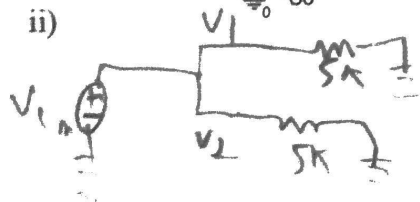

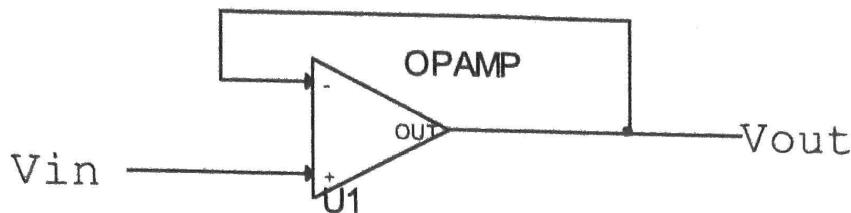2) Gain Bandwidth Product – Voltage follower transfer function




- a) For the voltage follower amplifier, the op-amp has a passband internal gain of 10^5 and a break frequency of 10 [rad/s]. Use circuit analysis and the op-amp frequency dependent gain expression, $A(s) = A_{\text{internal}} \frac{\omega_B}{s + \omega_B}$, to derive the transfer function for the voltage follower, $H(s) = V_{\text{out}}(s)/V_{\text{in}}(s)$. (You derived the relationship between V_{out} and V_{in} for constant finite gain in the last homework.). Make any reasonable simplifications to the transfer function.
- b) Based on your transfer function, determine the amplitude of the output voltage when

a. $V_{\text{in}}(t) = 10\sin(100t)$ \rightarrow 10V

b. $V_{\text{in}}(t) = 10\sin(10^5 t)$ \rightarrow 10V

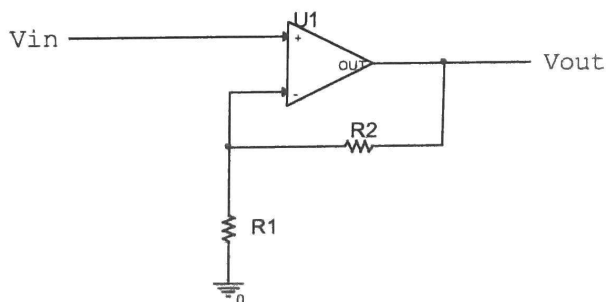c. $V_{\text{in}}(t) = 10\sin(10^7 t)$ \rightarrow 1V

(pay attention to the amplitude of the input voltage, 10V)



- c) Using your problem 1 expression, substitute the frequency dependent expression for op-amp gain, $A(s) = A_{\text{opamp}} \frac{\omega_B}{s + \omega_B}$, and determine the low pass filter transfer function for the non-inverting amplifier.
- d) For $R1 = 1\text{k}\Omega$, $R2 = 9\text{k}\Omega$, and the same op-amp characteristics as part a, make reasonable simplifications to the transfer function and determine the cutoff frequency of the non-inverting amplifier.

$$A = \frac{A_{\text{int}} \omega_B}{s + \omega_B} \rightarrow H(s) = \frac{A_{\text{int}} \omega_B}{A_{\text{int}} \omega_B + s + \omega_B} = \frac{10^6}{10^6 + 10 + s} = \frac{10^6}{10^6 + s}$$

$$3c: \frac{V_{out}}{V_{in}} = \frac{A(R_1 + R_2)}{R_1 + R_2 + AR_1} = \frac{A_{WB}(R_1 + R_2)}{R_1 + R_2 + \frac{A_{WB}}{s + \omega_B} R_1}$$

$$H(s) = \frac{A_{WB}(R_1 + R_2)}{R_1(s + \omega_B) + R_2(s + \omega_B) + AR_1 \omega_B}$$

$$p: H(s) = \frac{10^{10}}{10^3 s + 10^4 + 9 \times 10^3 s + 9 \times 10^4 + 10^9}$$

$$= \frac{10^{10}}{10^4 s + 10^9} = \frac{10^{16}}{10^4 (9 \times 10^5)} = \frac{10^6}{s + 10^5} = H(s)$$