



(You can assume that the power supply has infinite voltage.)

Determine the transfer function,  $H(s) = V_{out}(s)/V_{in}(s) = N(s)/D(s)$ , where  $N(s)$  and  $D(s)$  are polynomials. (3 pts)

Non Inverting terminal =  $V_{in}$  (no drop across resistor)

Ideal op amp: Non-Inverting = Inverting =  $V_{in}$

KCL at Inverting Terminal in S domain:

$$\frac{V_{in}}{10k} + \frac{V_{in} - V_{out}}{0.001s} = 0$$

$$\frac{V_{in}}{10k} + \frac{V_{in}}{0.001s} - \frac{V_{out}}{0.001s} = 0$$

$$V_{in} \left( \frac{1}{10k} + \frac{1}{0.001s} \right) = \frac{V_{out}}{0.001s}$$

$$\frac{V_{out}}{V_{in}} = H(s) = \frac{s + 10^7}{10^7}$$

In the limit as  $s \rightarrow 0$ , what common type of amplifier circuit does this circuit become? (2 pts)

As  $s \rightarrow 0 : H(0) = 1$ . It becomes a voltage follower.

In the limit as  $s \rightarrow \infty$ , what common type of amplifier circuit does this circuit become? (2 pts)

As  $s \rightarrow \infty : H(\infty) = \text{arbitrary gain}$ . It becomes a non-inverting amplifier.

