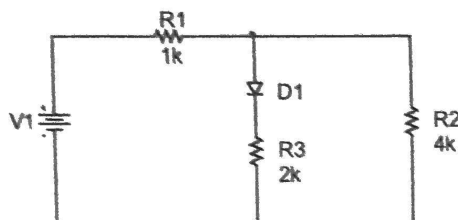



Homework 6

Reading: 2.7-8, (Chapter 3 concepts), 4.1-3


Problem 1) Ideal diodes, on/off conditions



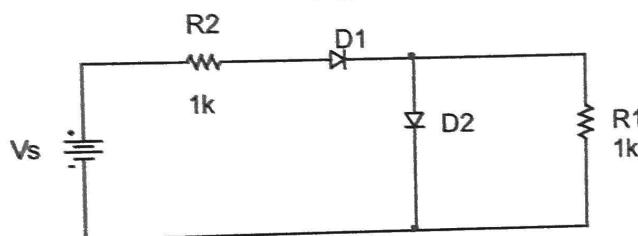- a) Determine the range of voltages for which the above diode is 'on' when the turn-on voltage of the diode is 0V. *Diode = "on" for $V_1 > 0V$*
- b) Determine the range of voltages for which the above diode is 'on' when the turn-on voltage of the diode is 1V. *$V_1(4k) / (1k + 4k) \geq 1 = 1.25V$*



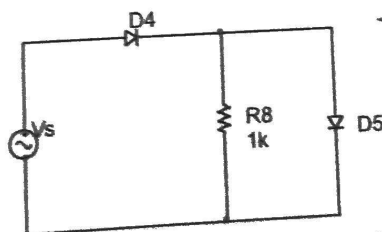
- c) For $V_s = 1V$ and ideal diodes with a turn-on voltage of 0V, determine the voltage across and current through each diode. *$V_{D1} = V_{D2} = 0V$ $I_{D1} = I_{D2} = 1mA$*
- d) For $V_s = 1V$ and ideal diodes with a turn-on voltage of 0.7V, determine the voltage across and current through each diode. *$V_{D1} = .7V$ $V_{D2} = .3V$*




- e) If the diodes in the above circuit are ideal, why is the circuit problematic? (The turn-on voltage is not necessary for this question.)

if the diodes are ideal this is just a short circuit for V_s .


Problem 2) Sinusoidal sources

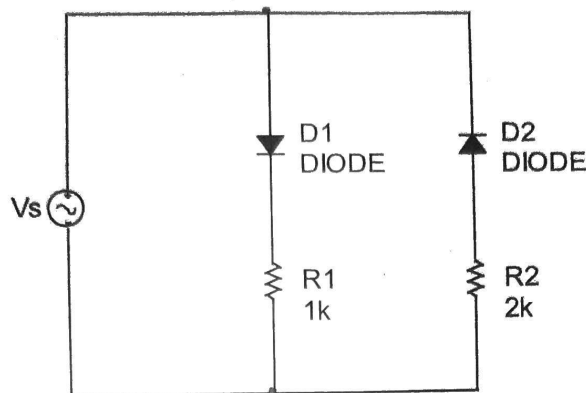

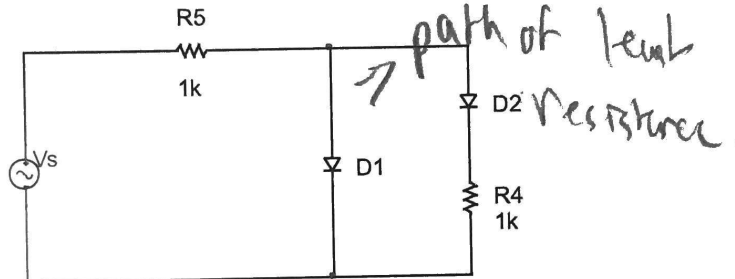- a) For ideal diodes with turn-on voltages, 1V, plot the current through each diode as a function of time. The source voltage is $V_s = 2\sin(\omega t)$. Include a plot of V_s for reference.





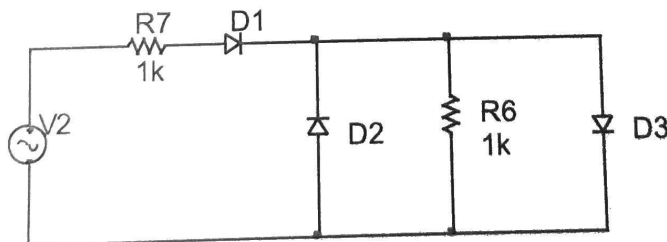- b) For ideal diodes with turn-on voltages, 1V, plot the current through both diodes (separate plots for I_{D1} and I_{D2}) as a function of time. The source voltage is $V_s = 4\sin(\omega t)$. Include a plot of V_s for reference.




- c) For ideal diodes with turn-on voltages, 1V, plot the voltage across $R6$ as a function of time. The source voltage is $V_s = 4\sin(\omega t)$. Include a plot of V_s for reference.




2A:

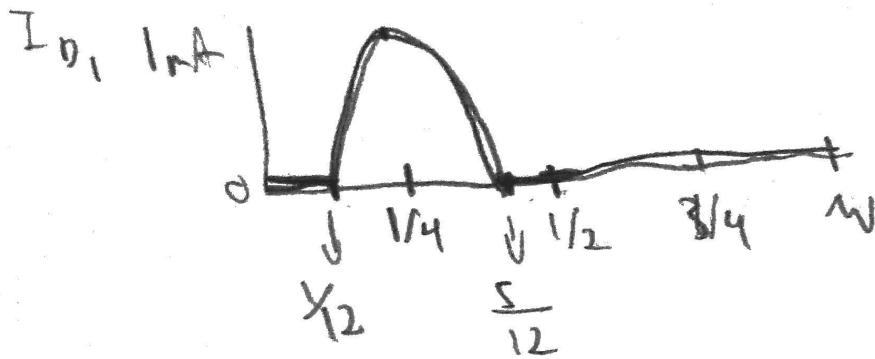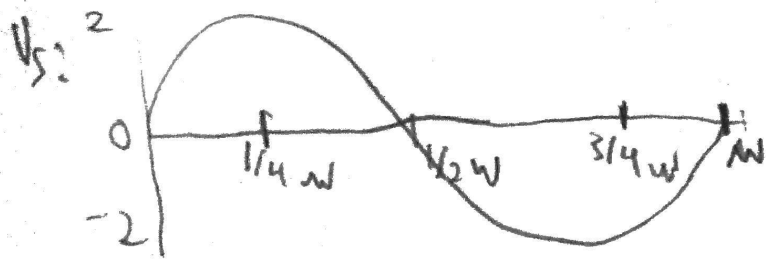

I_{D2}

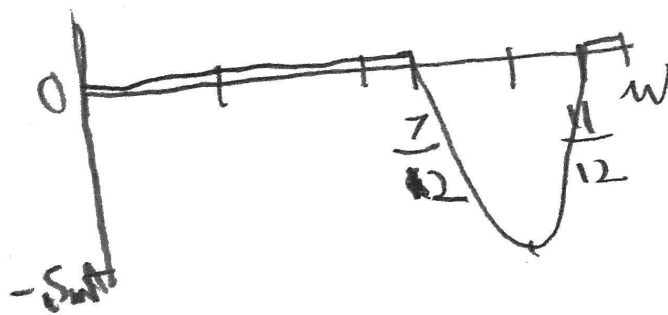

2B:

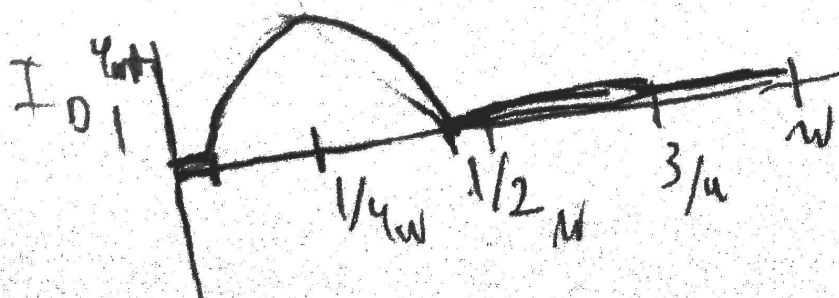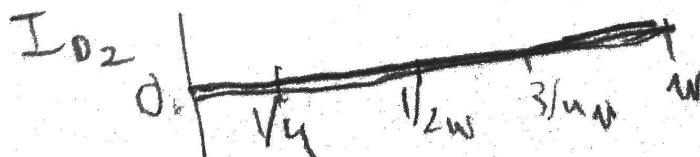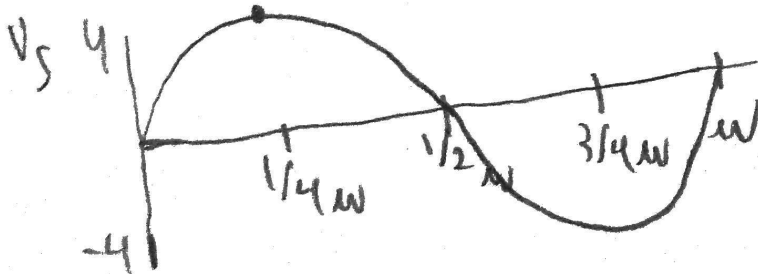


20.

D_1 on for $V_s > 1$


ignore D_2 because current can't flow

$$V_{RG} = V_{D3}$$

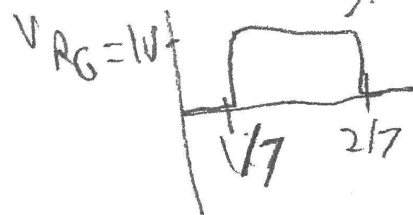
$$V_{RG} = (V_s - V_{D1}) \frac{1k}{2k} = 0.5(V_s - 1) = V_{D3}$$




clipped because diode

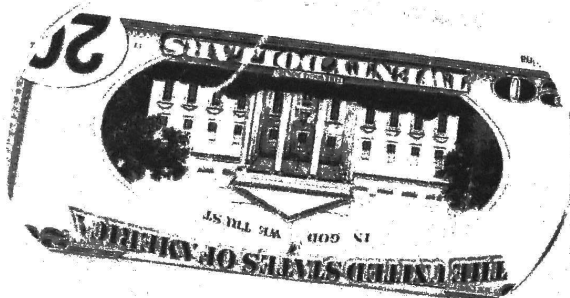


Problem 3) Guessing

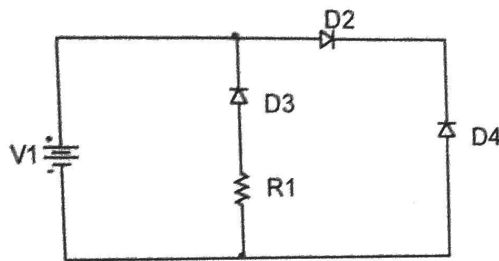

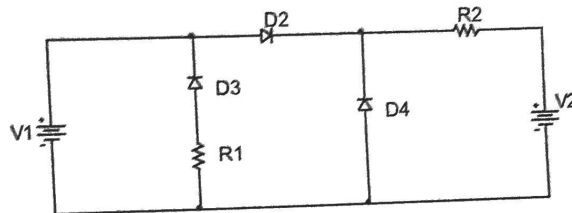- a) For some V_1 , which rows in the on/off 'truth table' can be ignored when analyzing the circuit?



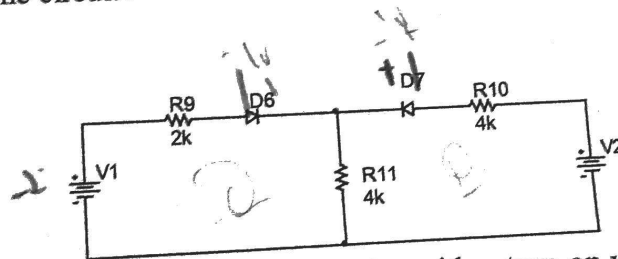- b) For some V_1 and V_2 , which rows in the on/off 'truth table' can be ignored when analyzing the circuit?



- c) For $V_1 = 2V$, $V_2 = 6V$ and ideal diodes with a turn-on voltage of $1V$, determine the voltage across and current through each diode.
 d) For $V_1 = -2V$, $V_2 = -2V$ and ideal diodes with a turn-on voltage of $1V$, determine the voltage across and current through each diode.

A: D_2 D_3 D_4

0 0 0 → ignore

0 0 1 → ignore

0 1 0

0 1 1 → ignore

1 0 0 → ignore

1 0 1 → ignore

1 1 0 → ignore

1 1 1 → ignore

B: D_2 D_3 D_4

0 0 0 → ignore

0 0 1

0 1 0

0 1 1


1 0 0

1 0 1

1 1 0

1 1 1

3C:

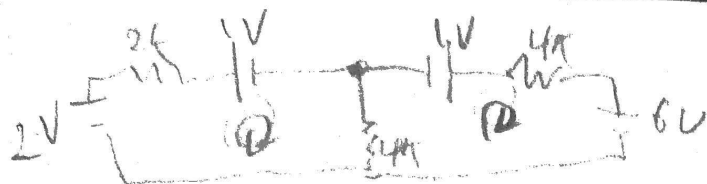


$$i_1 6k - i_2 4k = 1V \quad i_1 = 3nA \rightarrow \text{invalid}$$

$$i_2 8k - i_1 4k = -5V \quad i_2 = -8.125 \times 10^{-4} A$$

must be one off and one on

Try d7 on d6 off

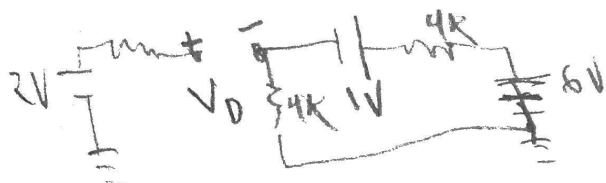

$$V_{D6} = -0.5V \quad I_{D6} = 0A$$

$$V_{D7} = 1V \quad I_{D7} = 6.25 \times 10^{-4} A$$

D:

both off is invalid. One on and one off is impossible because current flows other way. Try both on

$$i_1 6k - i_2 4k = -3 \quad i_1 = -0.01 \rightarrow \text{invalid}$$

$$i_2 8k - i_1 4k = -3 \quad i_2 = -9.3 \times 10^{-4}$$

Thus both diodes are off: $V_{D1} = -2V \quad I_{D1} = 0A$
 $V_{D2} = -2V \quad I_{D2} = 0A$