

Sacif Ahmed  
ahmeds7

9/16/19


66425946

(Colo HW#)

(1) 3.5: False. A NAND produces the opposite of an AND gate. In order an OR gate to become its dual, the inputs and outputs must be inverted. Because only the inputs are inverted this statement is false.

(2) 3.13:

Circuit:

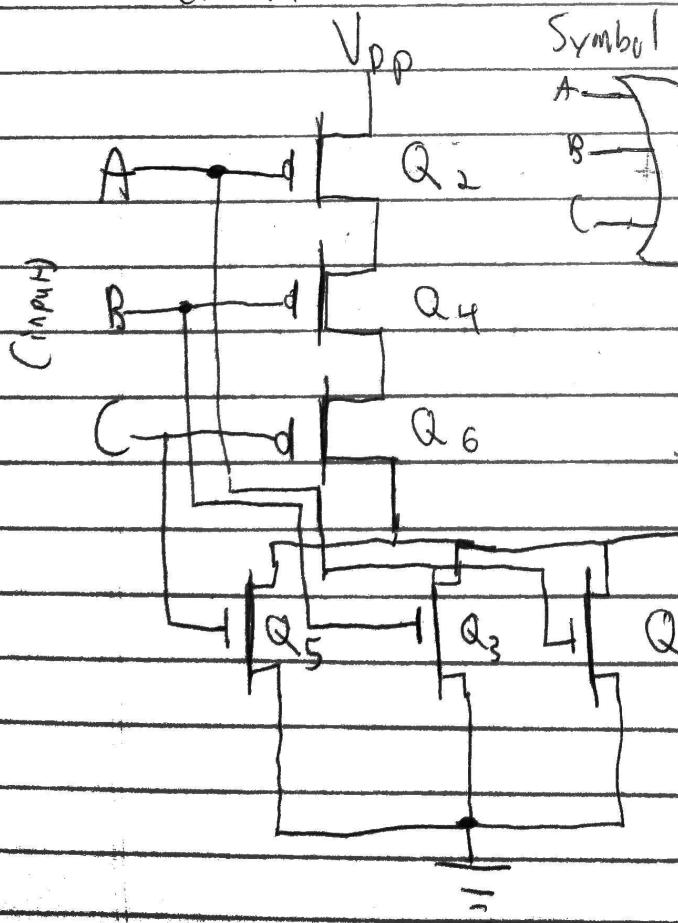

Function table:

ignore this

A	B	C	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>	Z
0	0	0	0	0	0	0
0	0	1	1	0	0	1
0	1	0	0	1	0	1
0	1	1	1	1	0	1
1	0	0	0	0	1	1
1	0	1	1	0	1	1
1	1	0	0	1	1	1
1	1	1	1	1	1	1



function Table:

A	B	C	$Q_1$	$Q_2$	$Q_3$	$Q_4$	$Q_5$	$Q_6$	Z
L	L	L	L	H	L	H	L	H	H
L	L	H	L	H	L	H	H	L	L
L	H	L	L	H	H	L	L	H	L
L	H	H	L	H	H	L	H	L	L
H	L	L	H	L	L	H	L	H	L
H	L	H	H	L	L	H	H	L	L
H	H	L	H	L	H	L	L	H	L
H	H	H	H	L	H	L	H	L	L

Q. 4.5: De Morgan's theorem holds so something is wrong in the boolean logic. If the expression is  $(W \cdot X + Y \cdot Z)$ , then the counter from De Morgan's theorem is  ~~$(\bar{W} + \bar{X} \cdot \bar{Y} + \bar{Z})$~~ . The question seemed to group the terms as  $\bar{W} + (\bar{X} \cdot \bar{Y}) + \bar{Z}$  which would give a 1. However the proper group is  $(\bar{W} + \bar{X}) \cdot (\bar{Y} + \bar{Z})$  according to De Morgan's theorem. This expression will give a 0.

$$(4) \text{ 4.6 A: } F = W \cdot X \cdot Y \cdot Z \cdot (W \cdot X \cdot Y \cdot Z' + W \cdot X' \cdot Y \cdot Z + W' \cdot X \cdot Y \cdot Z + W \cdot X \cdot Y \cdot Z)$$

$$F = W \cdot X \cdot Y \cdot (W \cdot X \cdot Y \cdot 0 + W \cdot X \cdot Y \cdot Z + W' \cdot X \cdot Y \cdot Z + W \cdot X \cdot Y \cdot Z)$$

$$F = W \cdot X \cdot (0 + W \cdot X \cdot Y \cdot Z + W' \cdot X \cdot Y \cdot Z + W \cdot X \cdot 0 \cdot Z)$$

$$F = W \cdot (W \cdot 0 \cdot Y \cdot Z + W' \cdot X \cdot Y \cdot Z + 0)$$

$$F = 0 + 0 \cdot X \cdot Y \cdot Z$$

$$\boxed{F = 0}$$

$$B: F = A \cdot B + A \cdot B \cdot C' \cdot D + A \cdot B \cdot D \cdot E' + A' \cdot B \cdot C' \cdot E + A' \cdot B' \cdot C' \cdot E$$

$$F = B \cdot (A + A \cdot C' \cdot D + A \cdot D \cdot E' + A' \cdot C' \cdot D) + (A' \cdot B \cdot C' \cdot E)$$

$$F = B \cdot (A \cdot (1 + C' \cdot D + D \cdot E')) + A' \cdot C' \cdot E + (A' \cdot B \cdot C' \cdot E)$$

$$F = B \cdot (A \cdot (1) + A' \cdot C' \cdot E) + (A' \cdot B' \cdot C' \cdot E)$$

$$\boxed{F = B \cdot (A + A' \cdot C' \cdot E) + (A' \cdot B' \cdot C' \cdot E)}$$

Ans

~~ANSWER~~

(5) 4.7 F:

→ continued

A	B	C	D	E	Z
1	0	1	1	1	1
1		0	0	0	0
1		0	0	1	0
1		0	1	0	0
1		0	1	1	0
1		1	0	0	6
1		1	0	1	8
1		1	1	0	0
1		1	1	1	0

4.7 H:

A	B	C	D	Z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

$$\begin{aligned}F &= (((A+B')''+C)'+D)' \\&= (((\bar{A} \cdot B + C)'+D)')' \\&= (((A+\bar{B} \cdot \bar{C})+D)')' \\&= (\bar{A} \cdot B) + (C \cdot \bar{D})\end{aligned}$$

4.7 I:

A	B	C	D	Z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

4.10 ( $\because F = \sum_{m,n,p} C_{j_2, j_5, j_6}$ )

$$F = \bar{A} \bar{B} ( + A \bar{B} \bar{C} + A \bar{B} C + A B C )$$

~~D:  $F = \prod_{m,n,p} C_{j_1, j_3, j_7}$~~

$$F = (M+N+P)(N+P+\bar{P})(M+\bar{M}+\bar{P})(\bar{M}+\bar{N}+P)(\bar{M}+\bar{N}+\bar{P})$$

$$Q) 4.10 \text{ C: } F = \sum_{A,B,C,D} (1, 2, 5, 6)$$

$$F = \sum_{A,B,C,D} (1, 2, 5, 6) \quad \blacksquare$$

$$= \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}D + \bar{A}B\bar{C}\bar{D}$$

$$F = \prod_{A,B,C,D} (0, 3, 4, 7, 8, 9, 11, 12, 13, 14, 15)$$

$$= (A+B+C+D)(A+B+\bar{C}+\bar{D})(A+\bar{B}+C+\bar{D})(A+\bar{B}+\bar{C}+\bar{D}) \bullet$$

$$(\bar{A}+B+C+\bar{D})(\bar{A}+B+C+\bar{D})(\bar{A}+B+\bar{C}+\bar{D}) (\bar{A}+B+\bar{C}+\bar{D}) \bullet$$

$$(\bar{A}+\bar{B}+C+\bar{D})(\bar{A}+\bar{B}+C+\bar{D})(\bar{A}+\bar{B}+\bar{C}+\bar{D}) (\bar{A}+\bar{B}+\bar{C}+\bar{D})$$

$$D: F = \prod_{MNP} (0, 1, 3, 5, 7)$$

$$= (M+N+P)(M'+N+\bar{P})(M+\bar{N}+\bar{P})(\bar{M}+\bar{N}+P) \bullet$$

$$(\bar{M}+\bar{N}+\bar{P})$$

$$F = \sum_{MNP} (2, 4, 6)$$

$$= \bar{M}N\bar{P} + M\bar{N}P + M\bar{N}P$$

$$F: F = x' + Y \cdot Z' + Y \cdot Z'$$

$$= x' + Y \cdot Z'$$

$$= x'(y+y')(z+z') + yz'(x+x')$$

$$= x'yz + x'y'z' + x'y'z + x'y'z + xyz' + x'yz' \quad \boxed{\text{Answer}}$$

$$= x'y'z + x'y'z + x'yz' + x'y'z + xyz' \quad \boxed{\text{Answer}}$$

$$= \sum_{xyz} (0, 1, 2, 4, 5, 6)$$

$$F = \prod_{xyz} (4, 5, 7)$$

$$= (\bar{x}+Y+Z)(\bar{x}+Y+\bar{Z})(\bar{x}+\bar{Y}+\bar{Z}) \quad \boxed{\text{Answer}}$$

# HW #2 Re-Submission

4.7 F:

→ continued

4.7 H:

A	B	C	D	Z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

Represent as SOP

$$\Sigma(2, 4, 6, 10, 14)$$

4.7 I:

A	B	C	D	Z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	1	1
0	1	0	0	0
0	1	1	0	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

Represent as SOP

$$\Sigma(2, 3, 4, 5, 6, 7, 8, 13, 15)$$

4.6 B:  $F = A \cdot B + A \cdot B \cdot C \cdot D + A \cdot B \cdot D \cdot E' + A' \cdot B \cdot C' \cdot E + A' \cdot B' \cdot C' \cdot E$

$$F = A \cdot B (1 + C \cdot D + D \cdot E' + A \cdot B \cdot C \cdot E \text{ pull out the } A \cdot B + A' \cdot B \cdot C \cdot E)$$

$$F = A \cdot B + A' \cdot B \cdot C \cdot E + A' \cdot B \cdot C \cdot E \text{ simplify and re-distribute}$$

$$F = A \cdot B + A' \cdot C' \cdot E$$