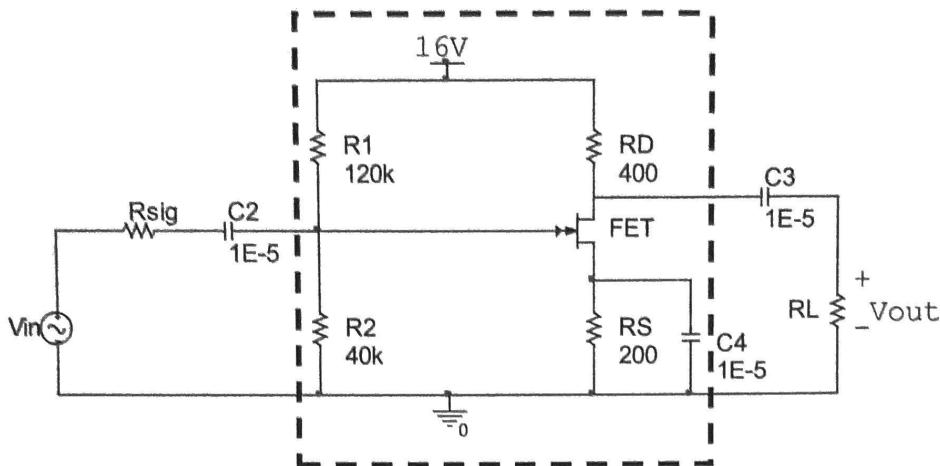


Homework 14

Reading: Chapters 10.1-6 (FET discussion)

Problem 1) Common Source with Cs and the Miller Theorem



The NMOSFET in the above circuit has characteristics $V_{TN} = 2.2V$, and $K_n = 400 \text{ mA/V}^2$


(DC bias characteristics from previous homework, you have calculated the DC bias characteristics and sketched the small signal model. The g_m value is 0.08 A/V .)

$$R_{sig} = 100\Omega$$


$$R_L = 1k\Omega$$

- For each external capacitor, determine the equivalent resistance seen by that capacitor when all other external capacitors are short circuited.
- Determine the approximate pole associated with each external capacitor.
- Estimate the low frequency 3dB cutoff.

$A_{overall}$

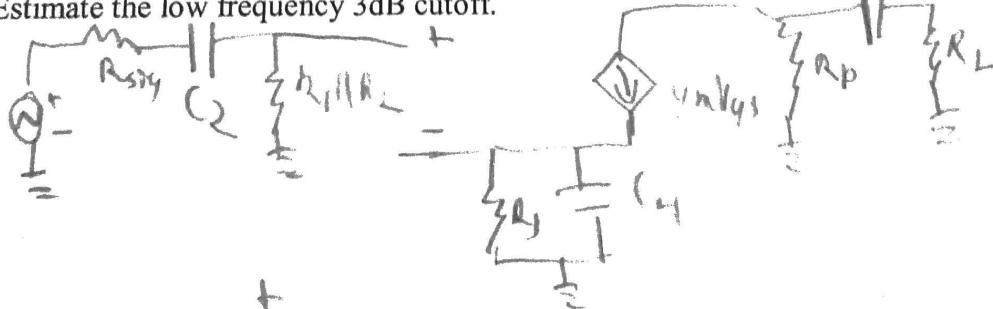

For C_2 :

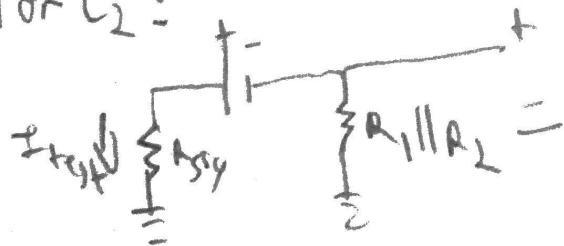


$$R_{seen} = R_{sig} + R_1 || R_2 = 30.1k \text{ } \cancel{\text{SC}}$$


$$\text{Pole} = \frac{1}{RC} = 3.322 \text{ rad/s}$$

Part B \rightarrow

For C_3 :

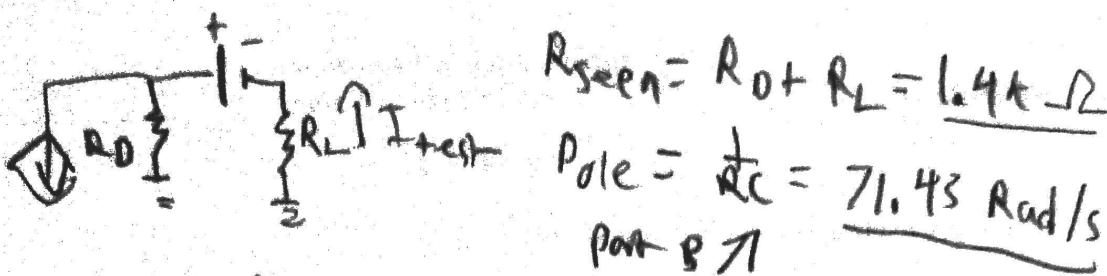

For C_4 :

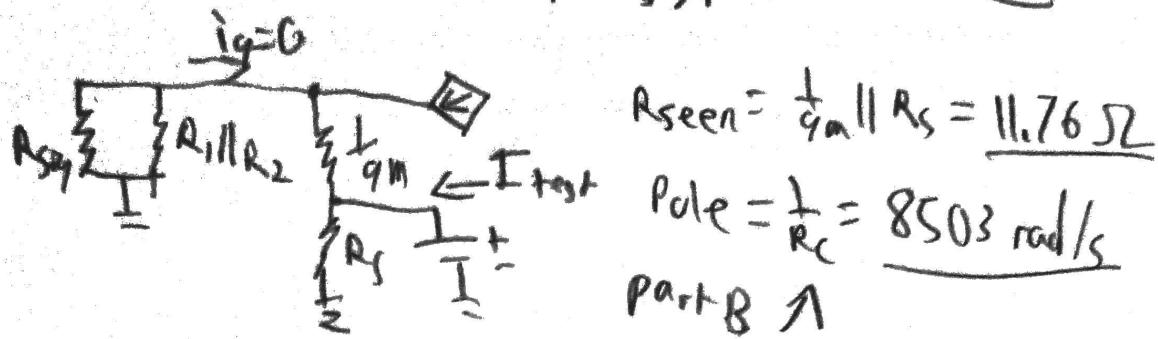

C:


$$Z_{C_2} \& Z_{C_3} \rightarrow 0 \quad Z_{C_4} \rightarrow \infty$$

$$R_{\text{seen}} = \frac{1}{R_m} \parallel R_g = 11.76 \Omega$$

$$\text{pole} = 8503 \text{ rad/s}$$

dominant pole $\rightarrow \underline{\omega_3 d B = 8503 \text{ rad/s}}$

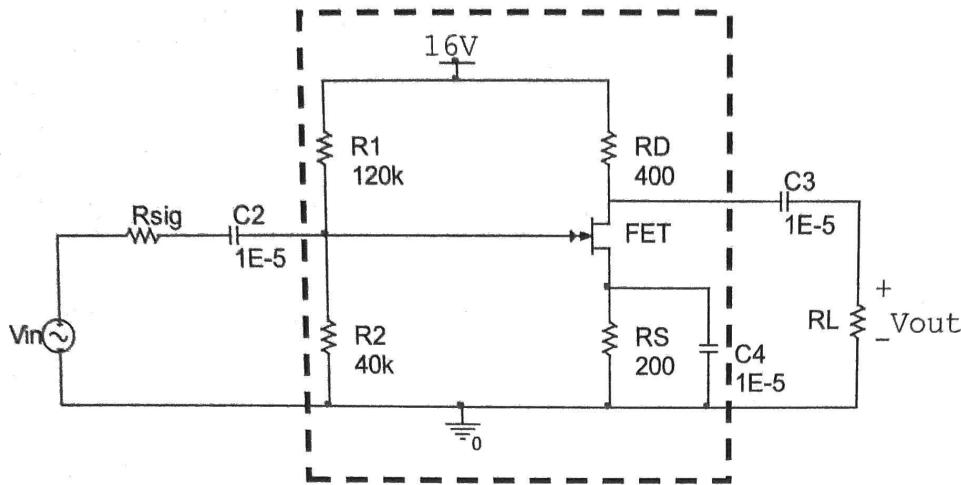Problem 2) Miller Theorem and CGD pole approximation




The NMOSFET in the above circuit has characteristics $V_{TN} = 2.2V$, and $K_n = 400\text{mA/V}^2$


(DC bias characteristics from previous homework, you have calculated the DC bias characteristics and sketched the small signal model. The g_m value is 0.08 A/V.)

$$\begin{aligned} C_{gs} &= 50\text{pF} \\ C_{gd} &= 20\text{pF} \end{aligned}$$
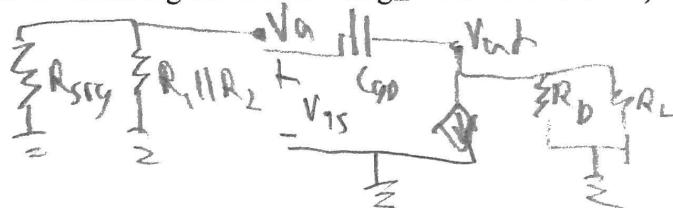
$$\begin{aligned} R_{sig} &= 100\Omega \\ R_L &= 1\text{k}\Omega \end{aligned}$$



- Only considering C_{GD} (C_{GS} open circuited) draw the small signal and identify the two nodes associated with the feedback capacitor, C_{GD} .
- Determine the Miller gain, A_M , associated with those two nodes.
- Redraw the circuit, representing the feedback capacitor as an input side and an output side capacitance.
- Approximate the pole associated with the input side of the circuit and the pole associated with the output side of the circuit.
- For those two poles, approximately determine the high frequency 3dB point.
- Repeat the C_{GD} pole calculation without using the Miller Theorem, replacing the capacitor with a test voltage and finding R_{EQ} using circuit analysis. Does the result after applying the Miller Theorem compare to the result obtained in part e?

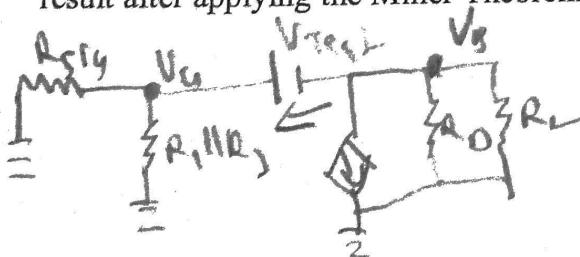


$$V_A = V_{TB} + V_B \left| \frac{V_B + 1}{R_{sig}(R_1 || R_2)} + g_m(V_B + 1) + \frac{V_B - 0}{R_D || R_L} \right|$$

$$V_B \approx -0.96V$$

$$V_A = 0.037V$$

B:
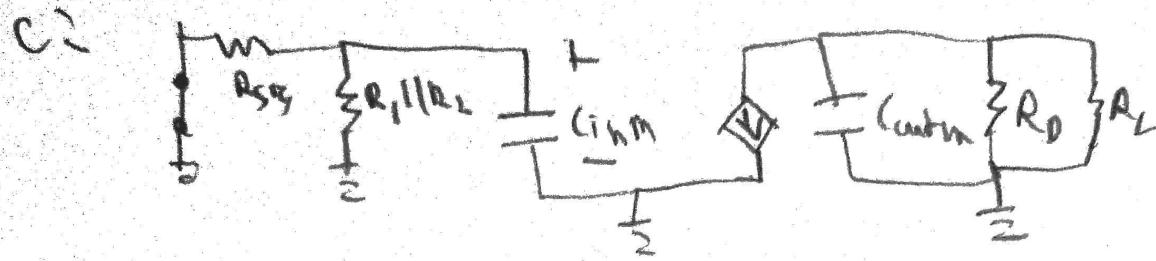
$$A_{v2} = \frac{V_{out}}{V_{in}} = -25.72$$



D:

$$P_{in} = \frac{1}{R_{S2} || R_1 || R_2 \cdot C_{in}}$$

$$= \underline{2 \cdot 103 \cdot 10^7}$$

$$C_{in} = (g_D(1 + g_m(R_0 || R_L)))$$

$$= 4.77 \cdot 10^{-10}$$

$$P_{out} = \frac{1}{R_{0 || R_L} \cdot C_{out}}$$

$$= \underline{1.68 \cdot 10^7}$$

$$C_{out} = (g_D(1 + g_m(R_0 || R_L)))$$

$$= 21.1 \cdot 10^{-11}$$

E:

$$\frac{P_{cm}}{P_{out}} = P_{3dB} = \underline{1.87 \cdot 10^7}$$


F:

$$R_{Sce} = R_{S2} || R_1 || R_2 + R_D || R_L = 385.37$$

$$P = \frac{1}{385.37 \cdot 20 \cdot 10^{-12}} = \underline{1.3 \cdot 10^8}$$


If does not compare well

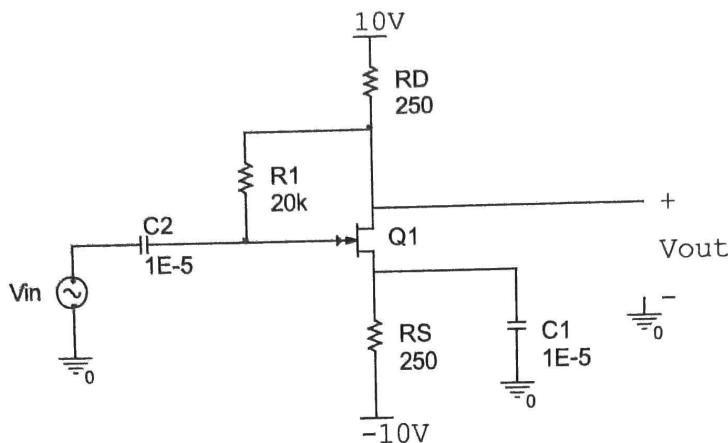Problem 3) Common Source with Cs and the Miller Theorem




The NMOSFET in the above circuit has characteristics $V_{TN} = 2.2V$, and $K_n = 40\text{mA/V}^2$
(DC bias characteristics from previous homework)

- Apply the Miller Theorem to the resistor R_1 , representing it as an equivalent input side and output side resistance in the small signal model.
- Using this equivalent circuit, for each external capacitor, determine the equivalent resistance seen by that capacitor when all other external capacitors are short circuited.
- Determine the approximate pole associated with each external capacitor.
- Estimate the low frequency 3dB cutoff.

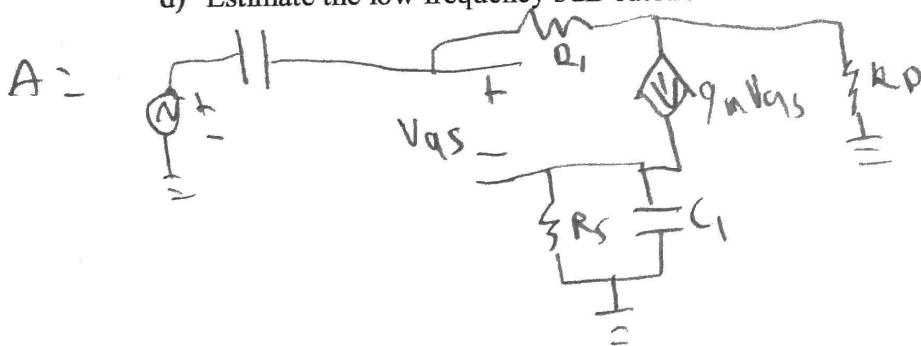

B: For short C_1 :
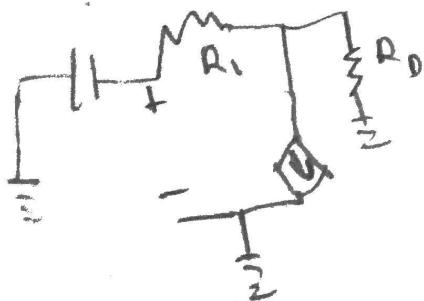
$$R_{\text{seen}} = R_1 + R_d = 20250 \Omega$$



For short C_2 :

$$R_{\text{seen}} = \frac{1}{g_m} \| R_s = 30.96 \Omega$$

$$C_2 = P_{\text{short } Q_1} = \frac{1}{R_C} = \underline{4,938}$$

$$P_{\text{short } Q_2} = \frac{1}{R_C} = \underline{3229,974}$$

D₂: lower pole $\omega_{3dB} = \underline{4,938 \text{ rad/s}}$