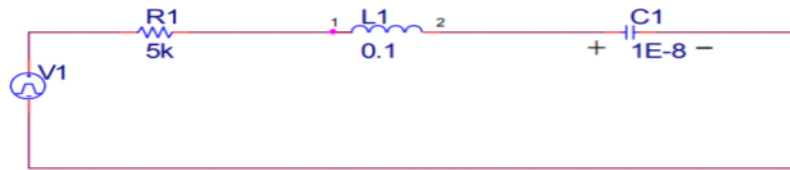



Circuits HW #5

Friday, February 21, 2020 11:59 AM

1 A:



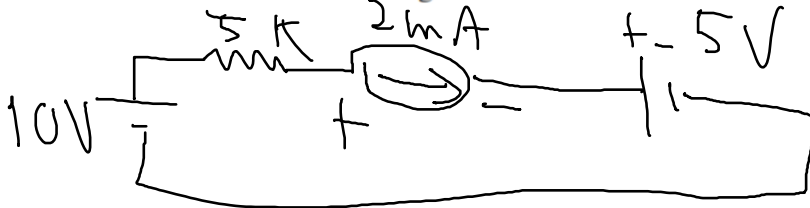At $t = 0^-$, the voltage across the capacitor is 5V (polarity shown), the current through the inductor is 2mA to the 'right' and the source is 10V. At $t = 0^+$, the voltage source becomes 5V and doesn't change for $t > 0$.



	Current	Voltage
R1	2mA	10V
C1	2mA	5V
L1	2mA	-5V
V1	2mA	10V

Mesh Analysis Constrained Node

Take KVL to solve for V_{L1}

$$\begin{aligned} -V_1 + V_{R1} + V_{L1} + V_{C1} &= 0 \\ -10V + 10V + V_{L1} + 5V &= 0 \\ V_{L1} &= -5V \end{aligned}$$

1 B:




	Current	Voltage
R1	2mA	10V
C1	2mA	5V
L1	2mA	-10V
V1	2mA	5V

Mesh Analysis Constrained Node

$$\begin{aligned} \text{Take KVL to solve for } V_{L1} \\ -5V + 10V + V_{L1} + 5V &= 0 \\ V_{L1} &= -10V \end{aligned}$$


1 C:

DC steady state

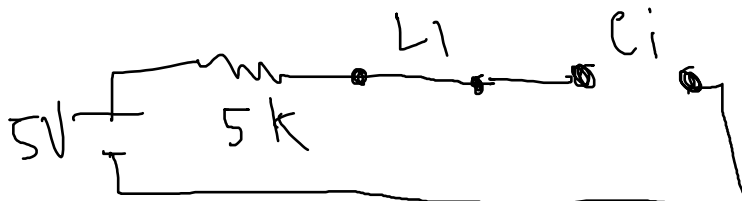

	Current	Voltage
R1	0mA	0V
L1	0mA	0V
C1	0mA	5V
V1	0mA	5V

1 D:

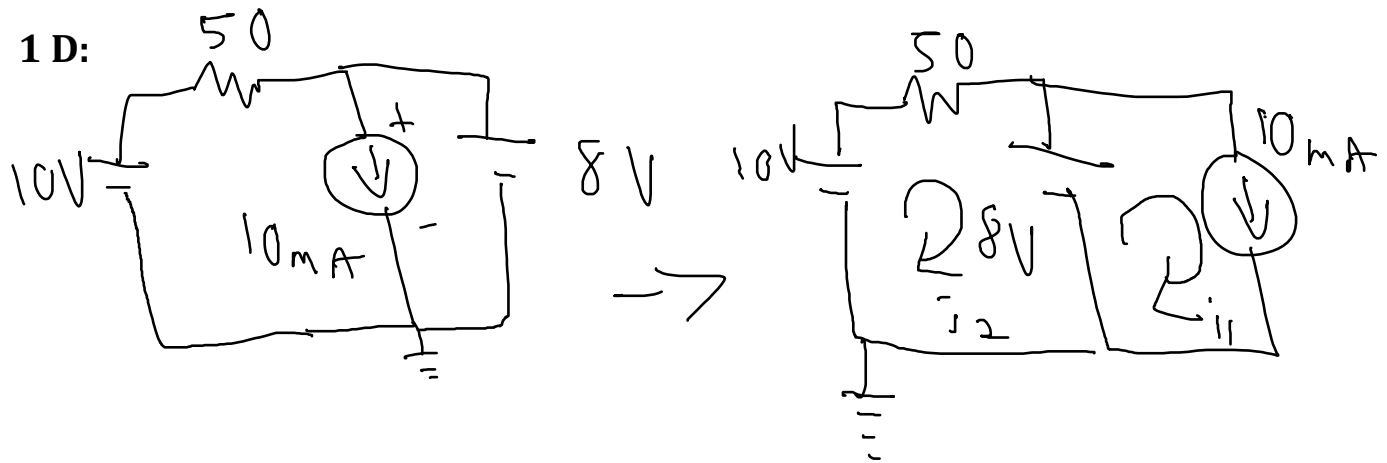

Mesh Analysis Constrained Node:

Use KVL to solve for V_{R1}

$$-10V + V_{R1} + 8V = 0$$

$$V_{R1} = 2V$$

$$i_2 = \frac{V_{R1}}{R_1} = 40mA$$

Use KVL to solve V_{L1}


$$-8V + V_{L1} = 0$$

$$V_{L1} = 8V$$

$$I_{C1} = i_2 - i_1 = 30mA$$

	Current	Voltage
R1	40mA	2V
L1	10mA	8V
C1	30mA	8V
V1	40mA	10V

1 E:

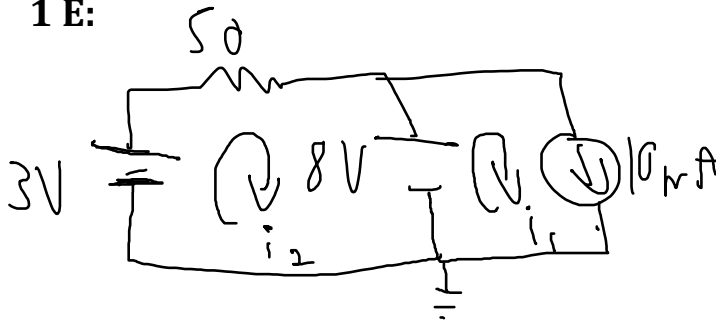

Mesh Analysis Constrained Node:

Use KVL to solve for V_{R1}

$$-3V + V_{R1} + 8V = 0$$


$$V_{R1} = -5V$$

$$i_2 = \frac{V_{R1}}{R1} = -100mA$$

$$I_{C1} = i_2 - i_1 = -110mA$$

	Current	Voltage
R1	-100mA	-5V
L1	10mA	8V
C1	-110mA	8V
V1	-100mA	3V

1 F:

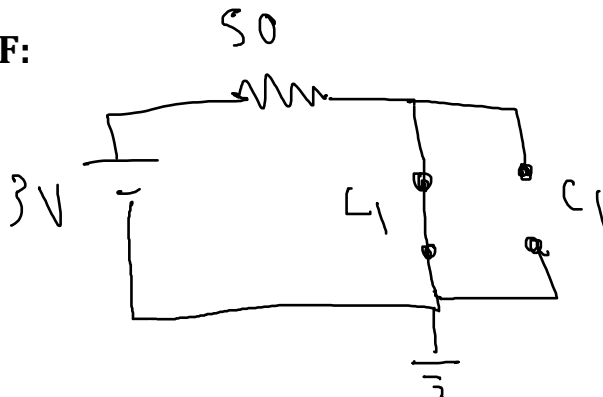

	Current	Voltage
R1	60mA	3V
L1	60mA	0V
C1	0A	0V
V1	60mA	3V

2 A:



Take KCL at the node V_a

$$\frac{V_a - V_s}{R} + I_L + I_C = 0$$

$$\frac{V_a - V_s}{R} + \frac{1}{L} \int V_C(t) + C \frac{dV_C}{dt} = 0$$

$\int V_C(t) = L \left(-C \frac{dV_C}{dt} - \frac{V_C - V_s}{R} \right)$ take derivative of both sides


$$V_C(t) = -LC \frac{d^2 V_C}{dt^2} - \frac{L}{R} \left(\frac{dV_C}{dt} - \frac{dV_s}{dt} \right)$$

2 B: From the equation solved in 2A we divide out $-LC$ from each term.

$$\alpha = \frac{1}{RC} ; \omega = \sqrt{\frac{1}{LC}}$$


2 C:

3 A:

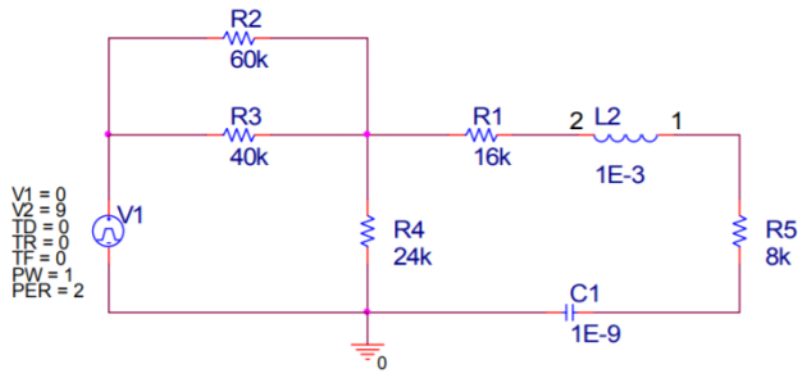

In the above circuit, the initial conditions are zero and the source can be considered a step function, $9u(t)$.

Find the Thevenin Circuit

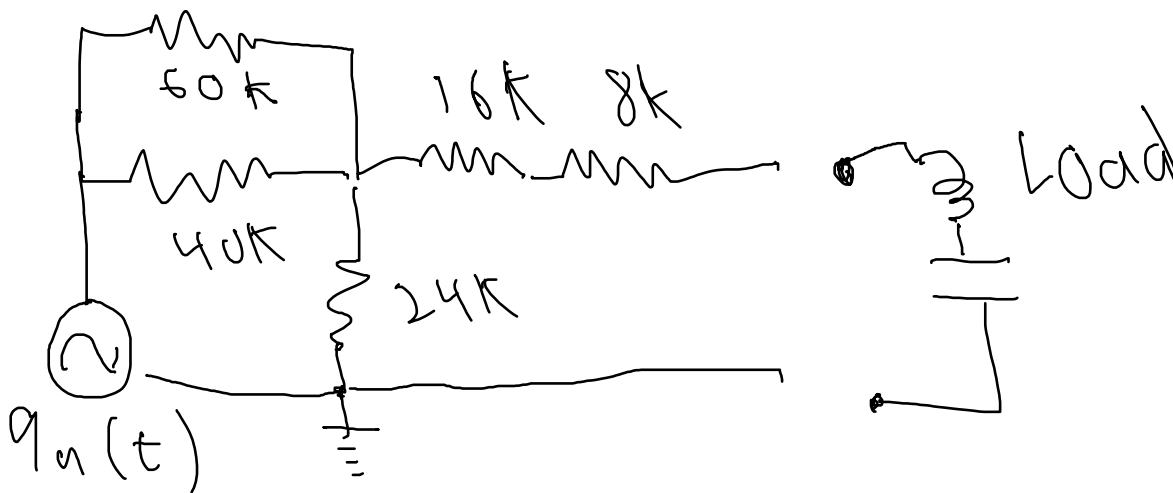


$$V_{TH} = V_{24K} \text{ Use Voltage Divider. } V_{24K} = 9u(t) * \frac{(24k)}{\left(\frac{1}{60k} + \frac{1}{40k}\right)^{-1} + 24k} = 4.5u(t)$$

Short across open load and find R_{TH}

$$R_{TH} = \left(\frac{1}{60k} + \frac{1}{40k}\right)^{-1} + \left(\frac{1}{24k} + \frac{1}{16k + 8k}\right)^{-1} = 36k$$


Simplified Circuit:

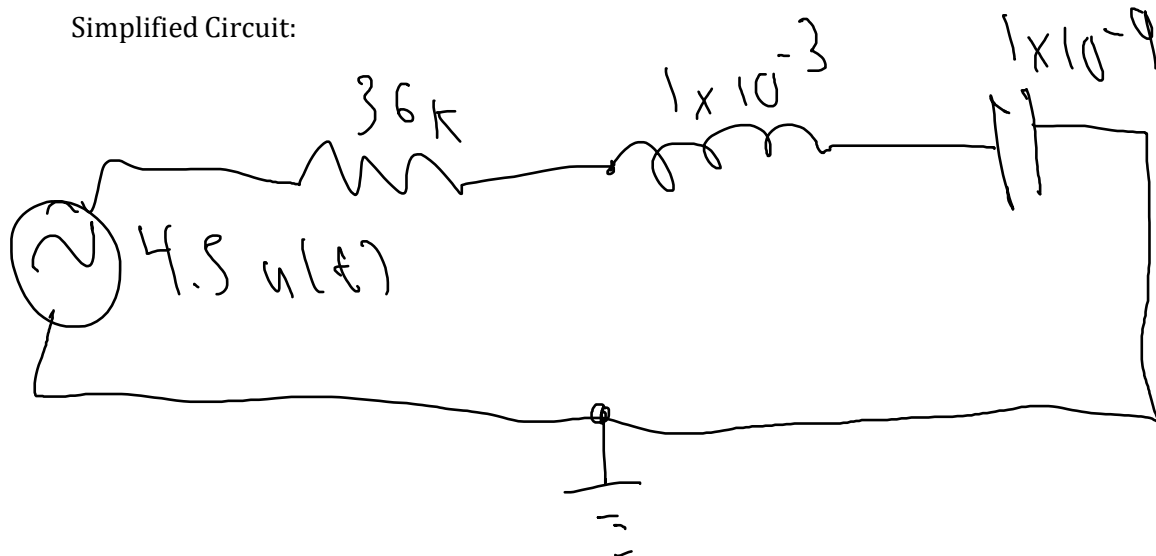



Because the inductor had no current through it at $t(0^-)$, the cap will have current 0A at $t(0^+)$. Voltage of cap will also be 0V.

At $t(0^+)$: $I_c = 0A$; $V_c = 0V$

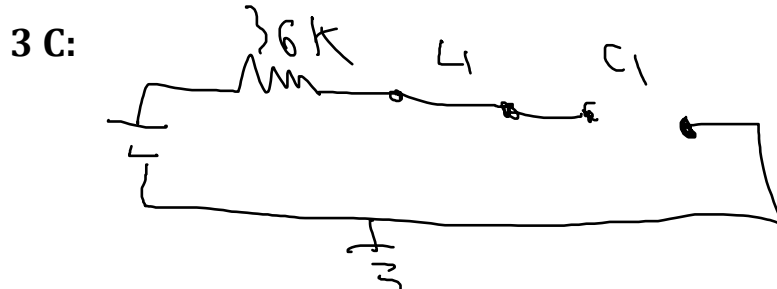

The DC SS of a cap is open circuit so the current is at $t(\infty) = 0A = I_c$

3 D:

$$V_c(t) = \frac{d^2 v_{cn}}{dt^2} + 2\alpha \frac{dv_{cn}}{dt} + \omega^2 v_{cn} = 0 \rightarrow s^2 + 2\alpha s + \omega^2 = 0 \rightarrow s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega^2}$$

$$s_1 = -27799.24 ; s_2 = -35972200.76$$

$$V_{cn} = A_1 e^{-27799.24t} + A_2 e^{-35972200.76t} + A_3$$

$$V_{cn}(0^-) = A_1 + A_2 + A_3 = 0$$

$$\frac{dv_{cn}}{dt} = \frac{i_l(0^-)}{C} = -27799.24A_1 - 35972200.76A_2 = 0$$

$$V(\infty) = 4.5V = A_3 \rightarrow A_1 + A_2 = -4.5V$$

$$\text{Solve the system: } A_1 = -4.503 ; A_2 = 0.00348$$

$$V_{cn}(t) = (-4.503)e^{-27799.24t} + (0.00348)e^{-35972200.76t} + 4.5V$$

$$\frac{dv_{cn}(t)}{dt} * C = (125180e^{-27799.24t} - 125183.26e^{-35972200.76t})10^{-9} = \frac{di_c(t)}{dt}$$

3 E:

$$\text{Characteristic S polynomial: } s^2 + 2\alpha s + \omega_0^2 = 0 \quad \text{Our equation: } s^2 + 2(1.8 * 10^7) + (10^{12}) = 0$$

3 F:

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega^2} \rightarrow s_1 = -27799.24, s_2 = -35972200.76$$

3 G:


2 Real unequal roots: **System is Overdamped**

3 H:

$$\text{For Overdamped systems: } V_c(t) = A_1 e^{-s_1 t} + A_2 e^{-s_2 t} + A_3$$

Problem 4: RLC series Circuits

A:

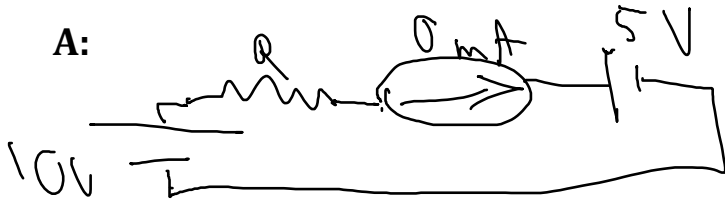

$$I_L = 0A$$

Take KVL, no voltage across resistor: $V_L = 5V$

B: In DCC steady state the cap is open circuit so no current through loop $I_L = 0A$

C: KVL: $V_s = IR + L \frac{di}{dt} + V_{c0} + \frac{1}{C} \int i dt$

$$V_s - \left(\frac{d^2 V_c}{dt^2} + \frac{R}{L} \frac{dV_c}{dt} + v_c \right) - RC \frac{dV_c}{dt} = V_L$$

D:

We first solve for $V_c(t)$

$$s^2 + 2\alpha s + \omega^2 = 0 ; \alpha^2 > \omega^2$$

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega^2} ; s_1 = -399749.84 ; s_2 = -250.16$$

$$V_c(0^-) = A + B + C = 5$$

$$\frac{dV_c}{dt}(0^-) = -399749.84A - 250.16B = 0$$

$$V_c(\infty) = 10 = C$$

Solving the system we get: $A = 0.00313 ; B = -5.003$

Thus

$$V_L(t) = V_s u(t) - (0.00313e^{-399749.84t} - 5.003e^{-250.16t} + 10) - (0.004)(-1251e^{-399749t} + 1251.6e^{-250.16t})$$

E:

$$s^2 + 2\alpha s + \omega^2 = 0 \quad 1 \text{ real roots } s_1, s_2 = -\alpha = -10^4$$

$$V_c(0^-) = Ae^{-10^4 t} + tBe^{-10^4 t} + C = 5$$

$$\frac{dV_c}{dt}(0^-) = -10^4 e^{-10^4 t} A - 10^4 e^{-10^4 t} Bt + Be^{-10^4 t} = 0$$

$$V_c(\infty) = C = 10$$

substitute in t and solve the system: $A = -5 ; B = -50000$

Thus

$$V_L(t) = V_s u(t) - (-5e^{-10^4 t} - 50000te^{-10^4 t} + 10) - (2 * 10^{-4})(50000e^{10^4 t} + 5 * 10^8 te^{-10^4 t} - 50000e^{10^4 t})$$

F:

$$2 \text{ complex roots } \beta = \sqrt{\omega^2 - \alpha^2} = 9683 ; s_1 = -2500 + j9683 ; s_2 = -2500 - j9683$$

$$V_c = e^{-2500t} (A \cos(9683t) + B \sin(9683t)) + C = 5$$

$$\frac{dV_c}{dt} : 9683e^{-2500t} A \sin(9683t) + 9683e^{-2500t} B \cos(9683t) - 2500e^{-2500t} A \cos(9683t) - 2500e^{-2500t} B \sin(9683t)$$

$$V_c(\infty) = C = 10$$

Substitute in $t = 0^+$ and solve the system: $A = -5 ; B = -1.29$

Thus:

$$V_L(t) = V_s u(t) - \left(e^{-2500t} (-5 \cos(9683t) - 1.29 \sin(9683t) + 10) \right) - (-2.26e^{-2500t} \sin(9683t) + 4.47 * 10^{-4} \cos(9683t))$$

Problem 5: RLC series design problem

Circuit is critically damped.


$$\alpha^2 = \omega^2 = -2 * 10^6$$

$$\omega^2 = 2 * 10^6 = \frac{1}{LC} = \frac{1}{L * 2 * 10^{-9}} ; L = 250$$

$$\alpha^2 = \left(\frac{R}{2L}\right)^2 = 2 * 10^6 = \left(\frac{R}{2(250)}\right)^2 ; R = 500000\sqrt{2}$$

The source function is equal to Cap voltage at $t = \infty$ thus source = $10u(t)$

Problem 6:

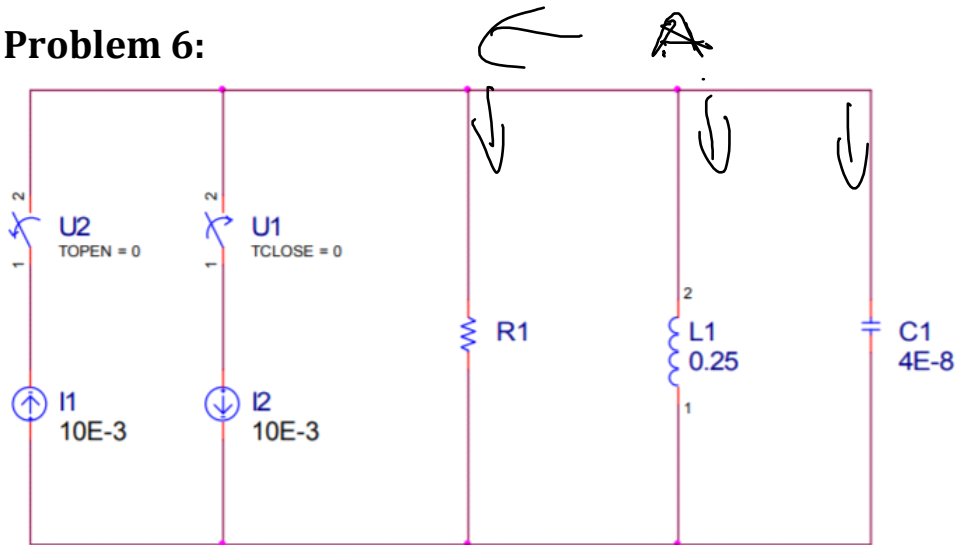

At $t = 0$, U1 closes and U2 opens.

A : Nodal at point A: $I_2 + I_R + I_L + I_C = 0$
 $10mA + 0A + 10mA + I_C = 0 ; I_C = -20mA$

B : $I_C(\infty) = 0A$

C : $I_R + I_L + I_C = -10mA$

$$\frac{1}{R} \frac{dV_C}{dt} + \frac{V}{L} + C \frac{d^2 V_C}{dt^2} = 0$$

$$\frac{1}{RC} \frac{dV_C}{dt} + \frac{V}{LC} + \frac{d^2 V_C}{dt^2} = 0$$

$$s^2 + 2\alpha s + \omega^2 \quad 2 \text{ complex roots } \beta = \sqrt{\omega^2 - \alpha^2} = 9950$$

$$V_C(t) = e^{-1000t} (A \cos(9950t) + B \sin(9950t)) ; V_C(0) = 0 = A$$

$$I_C(t) = (4 * 10^{-8}) (9950 e^{-1000t} B \cos(9950t) - 1000 e^{-1000t} B \sin(9950t)) = -20mA$$

$$B = -50.25$$

$$I_C(t) = (4 * 10^{-8}) (-5 * 10^5 e^{-1000t} \cos(9950t) + 50250 e^{-1000t} \sin(9950t))$$

Problem 6

D :

$$\frac{1}{RC} \frac{dV_c}{dt} + \frac{V}{LC} + \frac{d^2 V_c}{dt^2} = 0$$

$$s^2 + 2\alpha s + \omega^2 = 0 \quad 2 \text{ real roots } s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega^2} \quad s_1 = -1010 ; s_2 = -98989$$

$$V_c(0) = A + B = 0$$

$$I_c(0) = (4 * 10^{-8})(-1010Ae^{-1010t} - 98989Be^{-98989t}) = -20mA$$

Solving the system we get $A = 5.05 ; B = -5.05$

$$I_c(t) = (4 * 10^{-8})(-1010(5.05)e^{-1010t} + 98989(5.05)e^{-98989t})$$