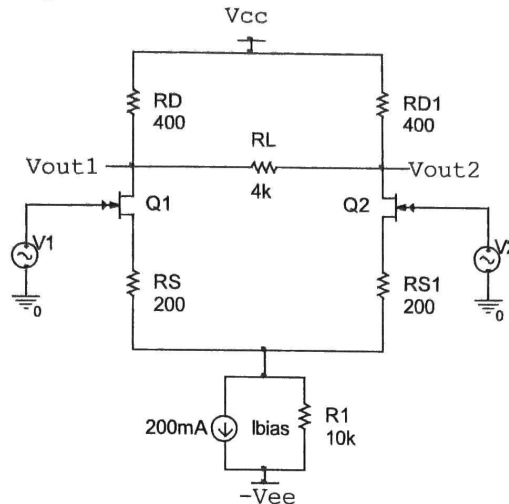


## Homework 19


In all BJT problems, you may assume that  $V_{CEsat} \sim 0.2V$ ,  $V_{BE} \sim 0.7V$  and  $r_o \rightarrow \infty$  when the transistor is in the forward active region. Also, the thermal voltage is  $V_{th} = 26mV$ .
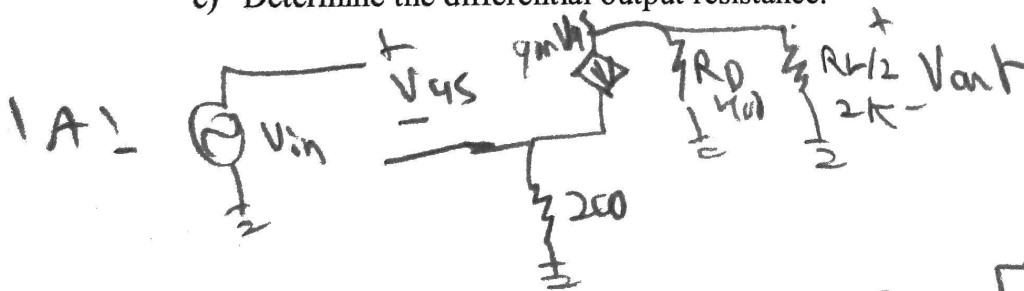
## Problem 1) Differential Amplifier




In the above circuit,  $K_n = 0.1A/V^2$ ,  
(Same differential circuit as problem 3 in HW18)

- Using superposition and the symmetric characteristics for differential inputs ( $V_1 = -V_2$ ), draw the small signal half circuit.
- Determine the half circuit differential mode gain,  $A_{DMHC}$ .
- Determine the input impedance 'seen by' common mode inputs,  $R_{inCM}$ .
- Determine the input impedance 'seen by' differential inputs,  $R_{inDM}$ .  
(The above are kind of 'trick' questions).
- Determine the differential output resistance.



$$B: A_{DMHC} = \frac{-g_m V_{gs} (R_D || 2k)}{V_{gs} + g_m V_{gs} \cdot 200} \rightarrow g_m = \sqrt{2K_n I_{DQ}} = .141 \rightarrow = \frac{-47}{29.2} = \underline{1.610}$$


C1

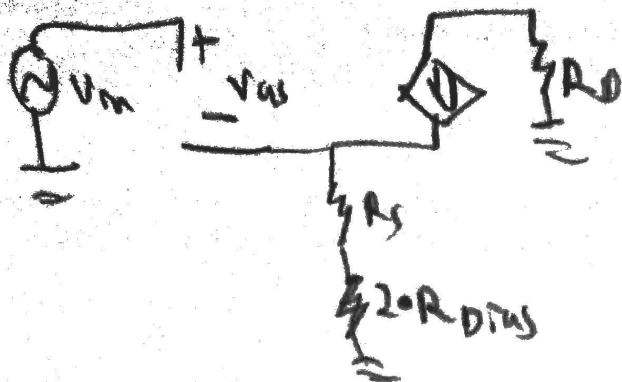

$$R_{in} = \text{open circuit} \\ = \infty$$

D1: retrace the differential circuit:  $R_{in} = \text{open circuit} \\ = \infty$


E1

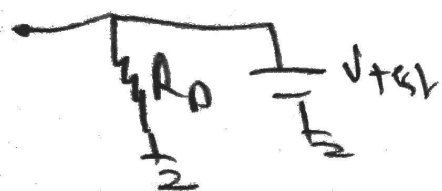

$$R_{out} \text{ on HC} = 400 \\ \downarrow$$


$$R_{out} = 800$$
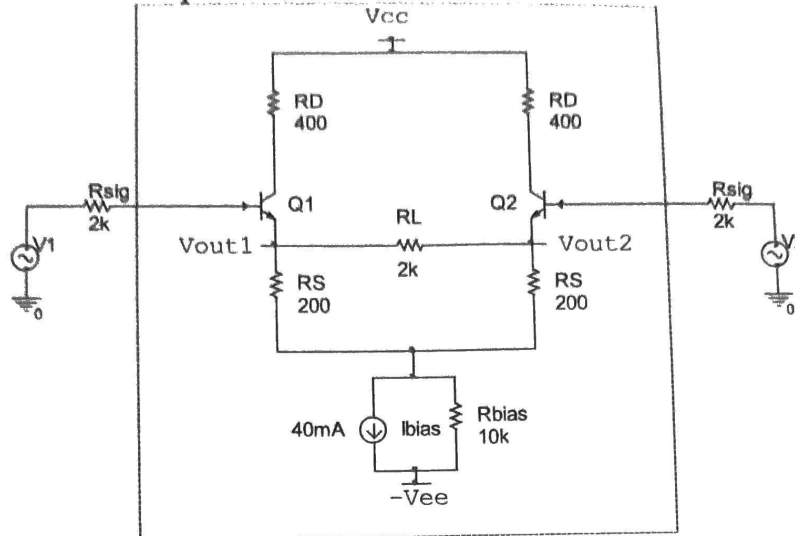
## Problem 2) Differential Amplifier - BJTs




In the above circuit,  $\beta = 100$ ,

- Using superposition and the symmetric characteristics for common mode inputs ( $V_1=V_2$ ), draw the small signal half circuit.
- Using superposition and the symmetric characteristics for differential inputs ( $V_1=-V_2$ ), draw the small signal half circuit.
- For the indicated dashed box, determine the input impedance 'seen by' common mode inputs,  $R_{inCM}$ .
- For the indicated dashed box, determine the input impedance 'seen by' differential inputs,  $R_{inDM}$ .  
(The above are kind of 'trick' questions).
- Determine the differential output resistance.
- Determine the half circuit common mode gain,  $A_{CMHC}$ . Include the contribution from  $R_{sig}$  in your calculation.
- Determine the half circuit differential mode gain,  $A_{DMHC}$ . Include the contribution from  $R_{sig}$  in your calculation.

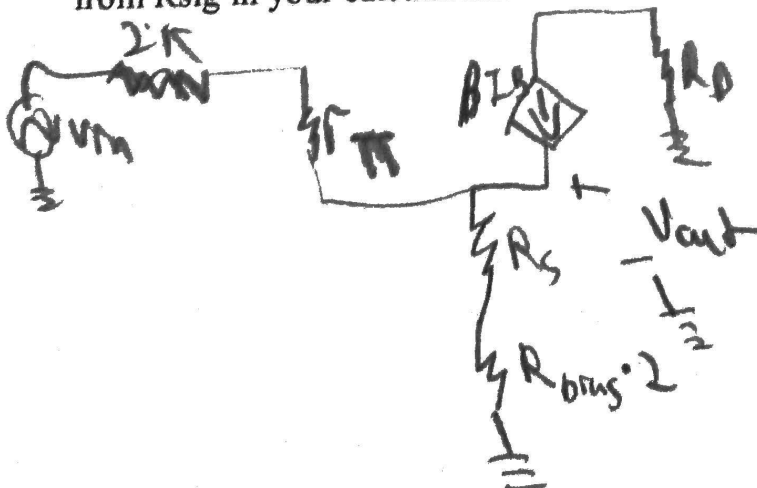

B:

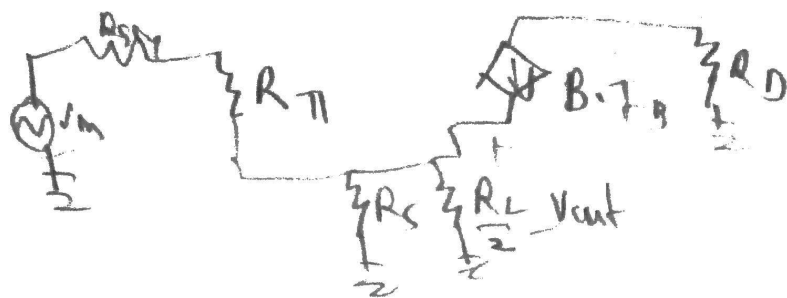

$$C: R_{in_{cm}} = R_{\pi} + (R_s + 2 \cdot R_{base}) (B+1)$$

$$= 2.04 \cdot 10^6$$

$$\downarrow R_{in_{cm}} = \underline{1.02 \times 10^6}$$

$$D: R_{in_{dm}} = R_{\pi} + (B+1) \left( R_s \parallel \frac{R_L}{2} \right) = 18964.63$$

$\downarrow$


$$\underline{R_{in_{dm}} = 33929.26}$$

$$E: R_{out} = R_s \parallel R_{\pi} = 130.45$$

$$F: A_{cm} = \frac{(B+1) (R_s + 2 R_{base})}{R_{sig} + R_{in_{cm}}} = .999$$

$$G: A_{dm} = \frac{(B+1) (R_s \parallel R_L/2)}{R_{sig} + R_{\pi} + (B+1) (R_s \parallel R_L/2)} = .888$$

## Problem 3) Current mirror loads

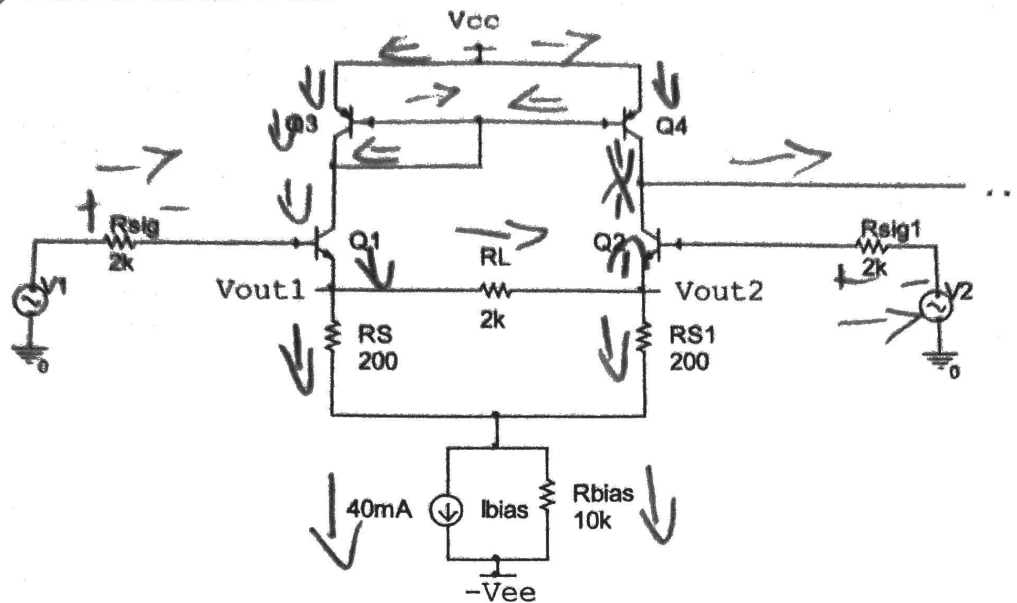

In the above circuit,  $\beta = 100$ ,

- 1) Assuming  $V1$  is a small positive voltage and  $V2$  is an equal and opposite small negative voltage, draw the polarity/direction of the small signal current for each resistor and transistor (base, emitter and collector).