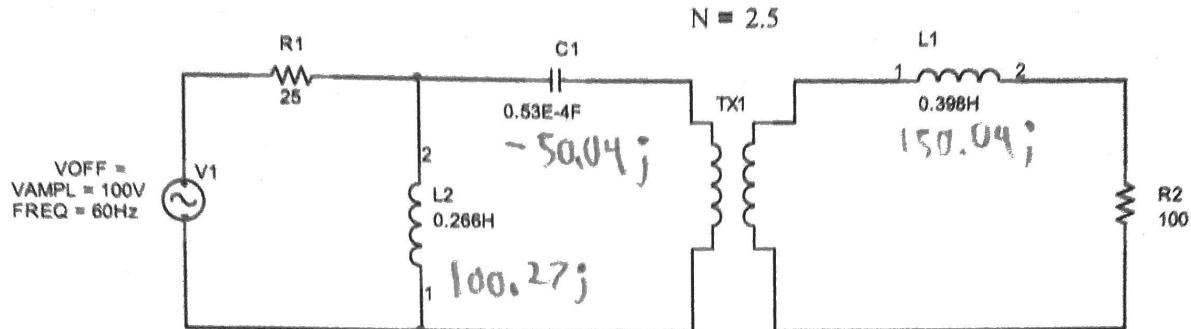


Problem 1) Ideal Transformers



The above circuit has a 100 V, 60 Hz source.


Hint: Draw in impedance form, and find Thevenin Equivalent first

- Determine the equivalent circuit when referring the secondary to the primary (and draw the circuit).
- Determine the equivalent circuit when referring the primary to the secondary (and draw the circuit).
- Determine the total complex power dissipated through the impedance in the primary.
- Determine the total complex power dissipated through the impedance in the secondary.
- Verify that the power dissipated is equal to the power generated by the source.

$$A: V_{TH} = \frac{100(100j)}{100j + 25} = 94.12 + 23.53j; Z_{TH} = \frac{Z_R \cdot Z_{L2}}{Z_R + Z_{L2}} = \frac{2R_1 \cdot 2L_2}{2R_1 + 2L_2} = 23.53 - 49.12j$$

$$Z_{load\,eq} = \frac{Z_{load}}{(N)^2} = \frac{100 + 150j}{(2.5)^2} = 16.24j$$
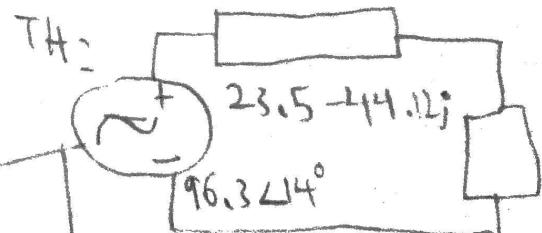
$$\tan^{-1}\left(\frac{23.53}{94.12}\right) = 14^\circ; \sqrt{94.12^2 + 23.53^2} = 96.293$$




$$B: Z_{eq\,p} = (2.5)^2 \cdot Z_{TH} = (147.1 - 275.74j); Z_{load} = 100 + 150j$$

$$V_{STH} = N V_{TH} = 2.5(94.12 + 23.53j) = (235.3 + 58.8j)V$$

$$\sqrt{235.3^2 + 58.8^2} = 242.25$$
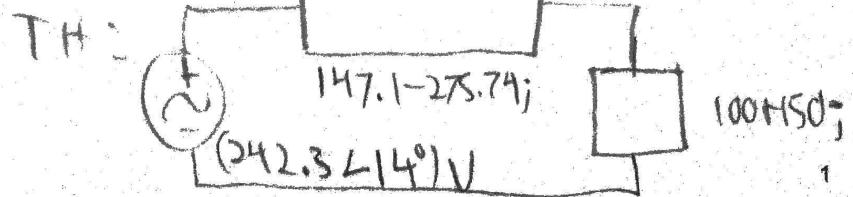
$$\tan^{-1}\left(\frac{58.8}{235.3}\right) = 14^\circ$$



$$C: Z_{eq} = 2, \quad \angle Z_{eq} = 34.53 - 20.12^\circ \quad \sqrt{(20.12)^2 + (34.53)^2} = 44.34 - 27^\circ$$

$$\tan^{-1}\left(\frac{-20.12}{34.53}\right)$$

$$I_{sp} = \frac{V_{sp}}{Z_{eq}} = 2.19 e^{j41^\circ} \quad Z = 23.5^2 + (-44.1)^2 \angle \tan^{-1}\left(\frac{-44.1}{23.5}\right) \\ = 50 \angle -62^\circ$$

$$S = \left(\frac{2.19}{\sqrt{2}}\right)^2 \cdot 50 \cos(-62^\circ) + \left(\frac{2.19}{\sqrt{2}}\right)^2 \cdot 50 \sin(-62^\circ)j = [56.14 - 105.58j]$$

$$D: Z_{eq} = 2, \quad \angle Z_{eq} = 247 - 125.74^\circ; \quad I_{ps} = \frac{235.32 + 58.88j}{247 - 125.74j} \\ \sqrt{235.32^2 + 58.88^2} \angle \tan^{-1}\left(\frac{58.88}{235.32}\right) = 180.32 \angle 56.31^\circ = 187.5 \angle 40.75^\circ$$

$$S = \left(\frac{187.5}{\sqrt{2}}\right)^2 \cdot 180.3 \cdot \cos(56.31^\circ) + \left(\frac{187.5}{\sqrt{2}}\right)^2 \cdot 180.3 \cdot \sin(56.31^\circ) \\ = [35.296 + 57.422j]$$

$$E: Z_{eq} = 44.3 \angle -27^\circ$$

$$S_{eq} = 9.69 e^{j41^\circ}$$

$$S = \frac{\left(\frac{9.69}{\sqrt{2}}\right)^2}{44.3} \cos(-27) + \frac{\left(\frac{9.69}{\sqrt{2}}\right)^2}{44.3} \sin(-27) = 94.42 + (-48.11j);$$

$$\frac{38.296 + 57.422j}{94.42 + (-48.11j)} = S_{source} \text{ checks out.}$$

$$C: Z_{eq} = Z_{s \rightarrow p} + Z_{L_{eq}} = 34.53 - 20.12j$$

$$\sqrt{(20.12)^2 + (34.53)^2} = 44.3 \angle -27^\circ$$

$$\tan^{-1}\left(\frac{-20.12}{34.53}\right)$$

$$I_{s-p} = \frac{V_{s \rightarrow p}}{Z_{eq}} = 2.19 \angle 41^\circ$$

$$Z = \sqrt{23.5^2 + (-44.1)^2} \angle \tan^{-1}\left(\frac{-44.1}{23.5}\right)$$

$$= 50 \angle -62^\circ$$

$$S = \left(\frac{2.19}{\sqrt{2}}\right)^2 \cdot 50 (\cos(-62^\circ) + \left(\frac{2.19}{\sqrt{2}}\right)^2 \cdot 50 \sin(-62^\circ)j) = [56.14 - 105.58j]$$

$$D: Z_{eq} = Z_{p \rightarrow s} + Z_{L_{eq}} = 247 - 125.74j$$

$$I_{p-s} = \frac{235.3 + 58.8j}{247 - 125.74j}$$

$$\sqrt{156^2 + 100^2} \angle \tan^{-1}\left(\frac{156}{100}\right) = 180.3 \angle 56.31^\circ$$

$$= 187.5 \angle 40.75^\circ$$

$$S = \left(\frac{187.5}{\sqrt{2}}\right)^2 \cdot 180.3 \cdot \cos(56.31^\circ) + \left(\frac{187.5}{\sqrt{2}}\right)^2 \cdot 180.3 \cdot \sin(56.31^\circ)$$

$$= [38.296 + 57.422j]$$


$$E: Z_{eq} = 44.3 \angle -27^\circ$$

$$V_s = 96.9 \angle 14^\circ$$


$$S = \frac{\left(\frac{96.9}{\sqrt{2}}\right)^2}{44.3} \cos(-27) + \frac{\left(\frac{96.9}{\sqrt{2}}\right)^2}{44.3} \sin(-27) = 94.42 + (-48.11j)$$

$$\frac{38.296 + 57.422j}{94.4 + (-48.11j)} = S_{\text{source}} \text{ checks out.}$$

Problem 2) Real Transformers

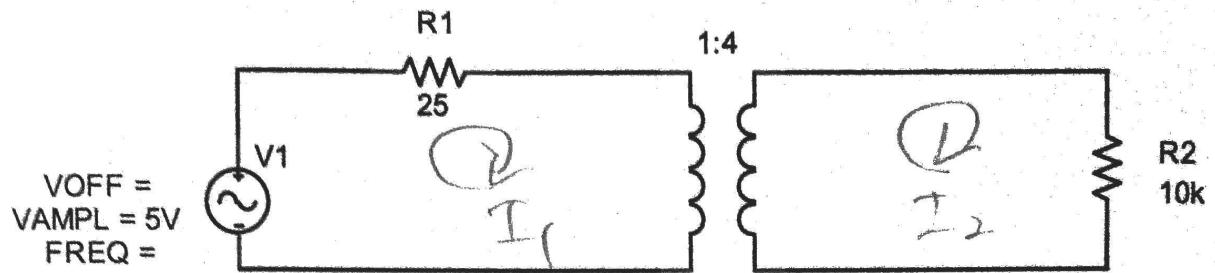

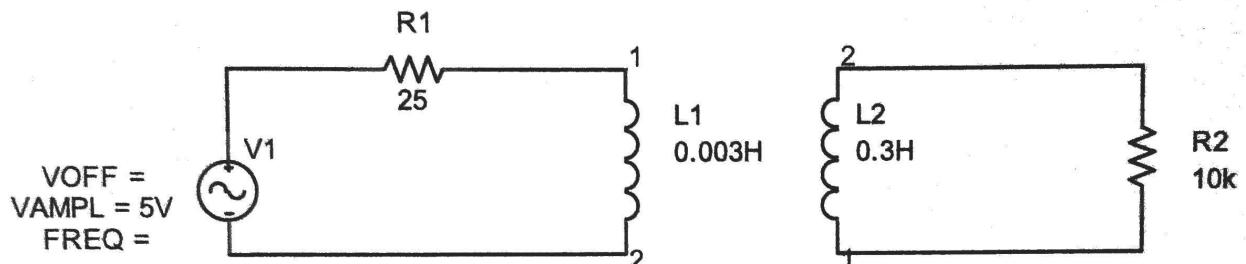a. Determine the voltage across R_2 in phasor form



$$M = k \cdot \sqrt{L_1 \cdot L_2}$$


b. If the real transformer is constructed of two inductors (as show) and the coupling coefficient is $k=0.8$, determine the Tee model of the circuit. Draw your circuit.

$$A: \quad Z_{R2} = \frac{1}{N_2^2} \cdot R_2 = 625 \quad I_1 = \frac{V_1}{625} = 7.69 \text{ mA}$$


$$I_2 = 7.69 / 4 = 1.923 \text{ mA} \quad V_{R2} = I_2 R_2 = 19.23 \text{ V}$$

$V_{R2} = 19.23 \angle 0^\circ$

$$B = .8 \sqrt{0.8 \cdot .3} = .024$$

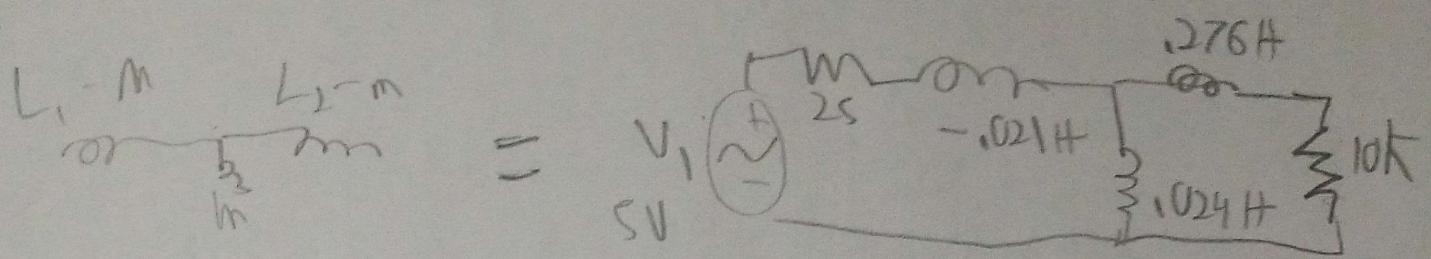

Problem 3) Impedance matching

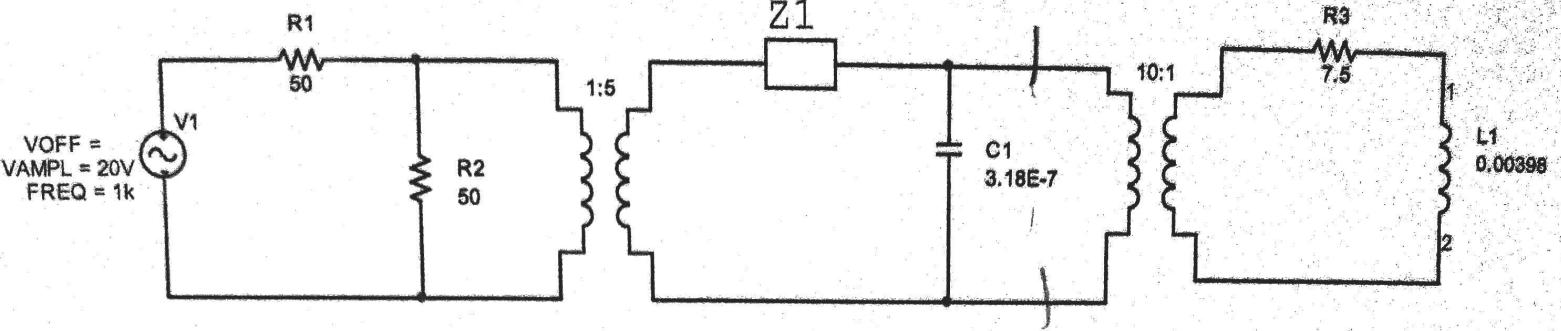

a. For the transformer circuit above, design Z₁ such that the power dissipated across the resistor R₃ is maximized.

$$A = \frac{7.1 + 3.18 \cdot 10^{-7} \cdot 2\pi \cdot 10^3}{10^2 \cdot (7.5 + 0.00398)} \cdot 10^2 \cdot (7.5 + 0.00398)$$

$$Z_1 = \frac{1}{3.18 \cdot 10^{-7} \cdot 2\pi \cdot 10^3} = 750 + j398 \Omega$$


$$Z_1 = 750 + 2000 \angle 22^\circ$$

From referring to primary $Z_1 \rightarrow \frac{Z_1}{s^2}$

So Z_1 will need to be

$$Z_1 = 18750 + 5005.5 \angle$$


Problem 4) Mutual Inductance

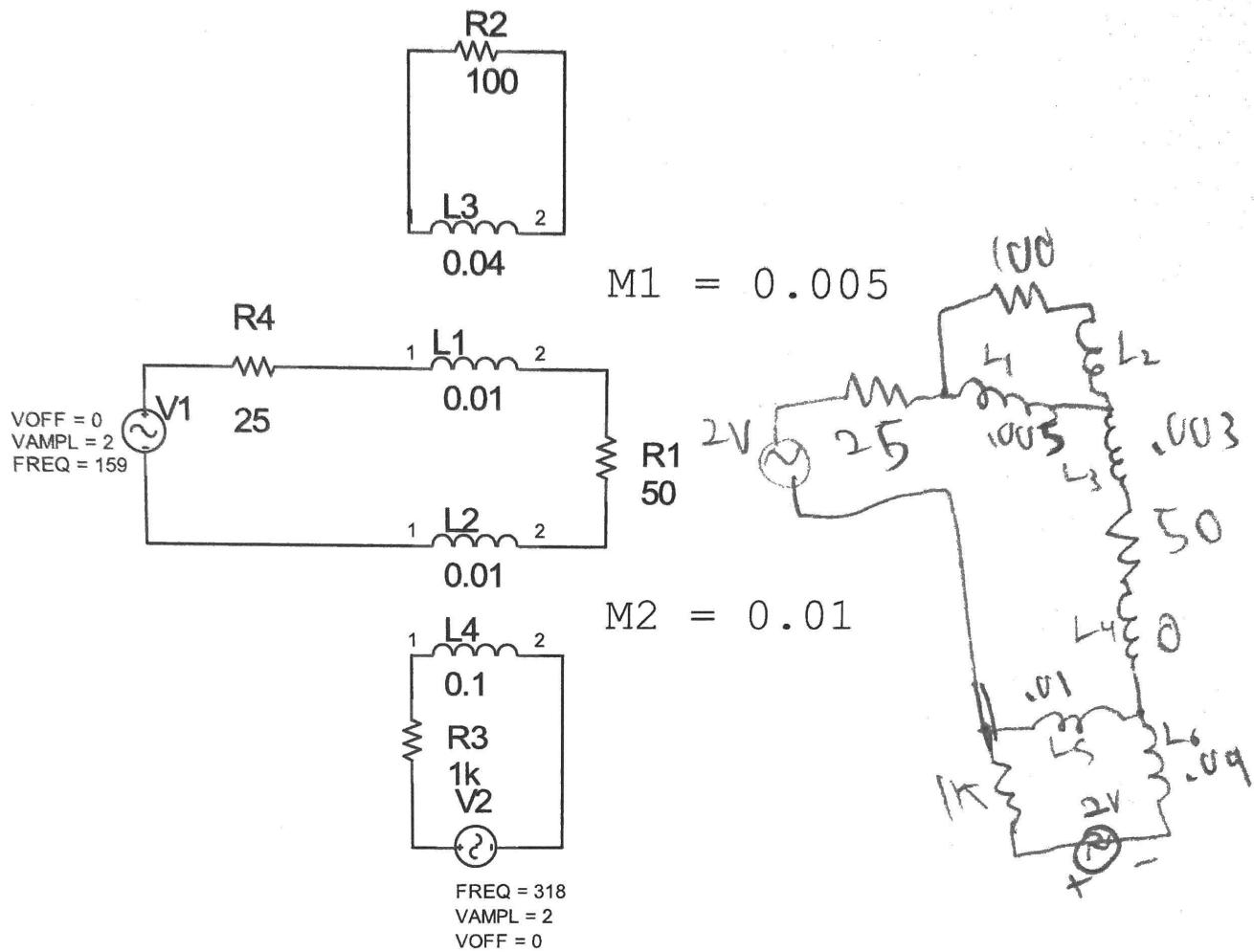

Find the current and voltage through R1 in the above couple circuits. There are two locations with inductive coupling and both sets have additive coupling. Additionally, there are two voltage sources with different excitation frequencies.
 Suggestion, use superposition in your analysis.

$$\begin{aligned}
 \text{For } V_1 & 25 + \left(\frac{1}{5j} + \frac{1}{(0.005+25j)} \right)^{-1} = 5j + 50 + \left(\frac{1}{10j} + \frac{1}{(0.003+100j)} \right)^{-1} \\
 & = 75.32 + 20j \quad I_{R1} = \frac{2}{75.32 + 20j} = .025 - .007j \text{ A}
 \end{aligned}$$

For $V_2 =$

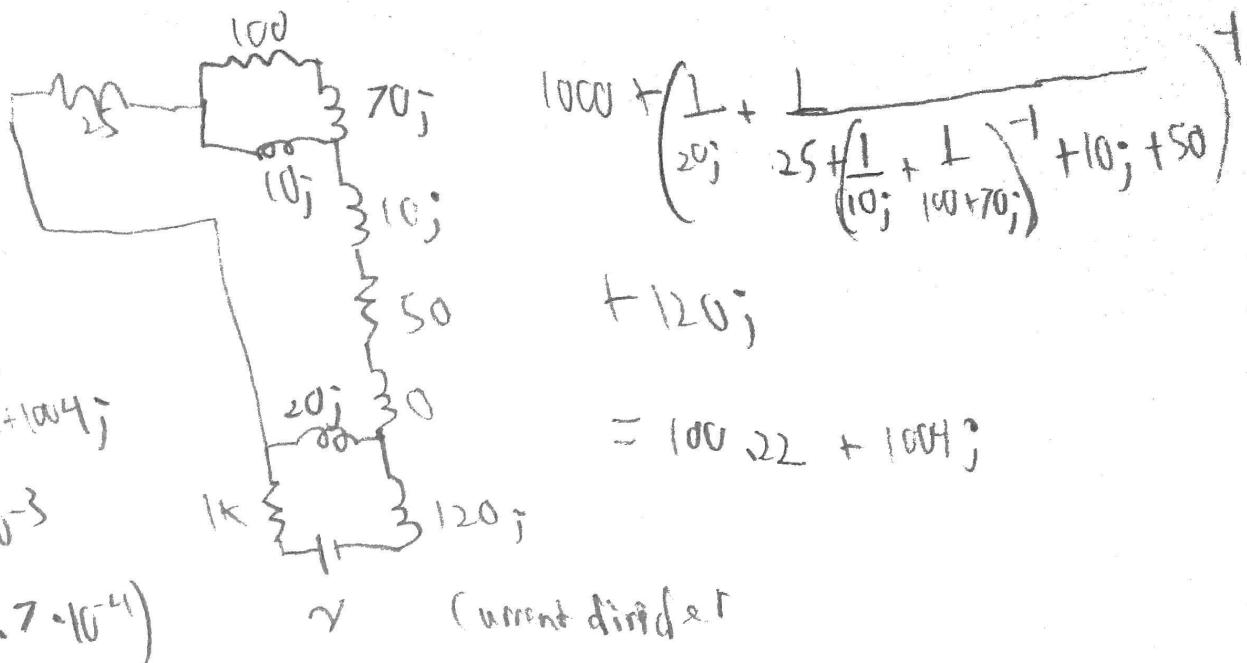

$$100V + \left(\frac{1}{20j} + \frac{1}{25 + \left(\frac{1}{10j} + \frac{1}{100+70j} \right)^{-1}} + 10j + 50 \right) + 120j = 100 \cdot 22 + 1004j$$

$$I_{\text{share}} = \frac{1}{(100 \cdot 22 + 1004j)}$$

$$= 1.9 \times 10^{-3}$$

$$1k \quad \left\{ \begin{array}{l} 20j \\ 30 \\ 120j \end{array} \right\}$$

+ $(2.7 \cdot 10^{-4})$ ✓ current divisor

$$I_{R_1} = 1.9 \times 10^{-3} - 2.7 \times 10^{-4} (20j)$$

$$\frac{20j + \left(\frac{1}{25 + \left(\frac{1}{10j} + \frac{1}{100+70j} \right)^{-1}} + 10j + 50 \right)}{+} = 1.7 \times 10^{-4} + 3.3 \times 10^{-4} j$$

$$I_{R_1} + I_{R_2} V_2 = -0.2517 - 0.08667j \cdot R_1 = 1.28 - 33j$$

$$V_{R_1} = 1.30 \angle -14^\circ$$

$$I_{R_1} = .026 \angle -14^\circ$$