

1) Laplace transforms/Transfer functions

Use Laplace transform tables!!!!

1.1: Find the Laplace transform of

$$f(t) = (\cos(2t) + e^{-4t}) \cdot u(t) \quad (\text{simplify into one ratio})$$

$$f(t) = \cos(2t)u(t) + te^{-4t}u(t) \rightarrow \text{Use a table} \quad \frac{s}{s^2+2^2} + (s+4)^{-1}$$

$$F(s) = \frac{2(s^2-2s+2)}{(s-4)(s^2+4)}$$

1.2: Find the poles and zeros of the following functions. Indicate any repeated poles and complex conjugate poles. Expand the transforms using partial fraction expansion.

1.2.1

$$F(s) = \frac{20}{(s+3)(s^2+8s+25)}$$

Zeros: none

poles: $-3, -4+3i, -4-3i$ complex

$$\frac{-8 \pm \sqrt{64-100}}{2} = -4 \pm 3i$$

$$\frac{A}{(s+3)} + \frac{B}{(s-(-4+3i))} + \frac{C}{(s-(-4-3i))} = \text{pfe } F(s)$$

Continued on another page.

1.2.2

$$F(s) = \frac{2s^2+18s+12}{s^4+9s^3+34s^2+90s+100}$$

$$\text{Zeros: } \frac{-9 \pm \sqrt{33}}{2}, \frac{-9 \pm \sqrt{33}}{2}$$

$$\text{poles: } -2, -5, -1+3i, -1-3i$$

$$\frac{-18 \pm \sqrt{18^2-4(24)}}{4} = \frac{-9 \pm \sqrt{33}}{2}$$

$$\frac{-9 \pm \sqrt{33}}{2}$$

$$s^4+9s^3+34s^2+90s+100$$

↓

$$(s+2)(s+5)(s^2+2s+10)$$

$$\begin{matrix} -2 & -5 & \frac{-2 \pm \sqrt{2^2-40}}{2} & -1 \pm 3i \\ & & & -1-3i \end{matrix}$$

$$\frac{A}{s+2} + \frac{B}{s+5} + \frac{C}{s+1-3i} + \frac{D}{s+1+3i}$$

Continued on another page

Problem 1.2.1

$$\frac{20}{(s+3)(s+4-3i)(s+4+3i)} = \frac{A}{(s+3)} + \frac{B}{(s+4-3i)} + \frac{C}{(s+4+3i)}$$

$$20 = A(s+4-3i)(s+4+3i) + B(s+3)(s+4+3i) + C(s+3)(s+4-3i)$$

For $s = -3$

$$20 = A(1-3i)(1+3i)$$

$$A = 2$$

For $s = -4-3i$

$$20 = C(-1-3i)(-6i)$$

$$C = -1 - \frac{1}{3}i$$

For $s = -4+3i$

$$20 = B(-1+3i)(6i)$$

$$B = -1 + \frac{1}{3}i$$

$$F(s) = \frac{2}{s+3} + \frac{-1+\frac{1}{3}i}{s+4-3i} + \frac{-1-\frac{1}{3}i}{s+4+3i}$$

~~$$F(t) = 2e^{-3t} + (-1+\frac{1}{3}i)e^{(-4+3i)t} + (-1-\frac{1}{3}i)e^{(-4-3i)t}$$~~

$$F(t) = 2e^{-3t} + (-1+\frac{1}{3}i)e^{(-4+3i)t} + (-1-\frac{1}{3}i)e^{(-4-3i)t}$$

Problem 1.2.2

$$2s^2 + 18s + 12 = A(s+5)(s+1-3i)(s+1+3i) + B(s+2)(s+1-3i)(s+1+3i) + C(s+2)(s+5)(s+1+3i) + D(s+2)(s+5)(s+1-3i)$$

For $s = -5$

$$-28 = B(-75) \quad B = \frac{28}{75}$$

For $s = -2$

$$-16 = A(30) \quad A = -\frac{8}{15}$$

For $s = -1 + 3i$


$$-22 + 42j = (-90 - 30j)C \quad C = 0.08 - \frac{37}{75}j$$

For $s = -1 - 3i$

$$-22 + 42j = (-90 + 30j)D \quad D = 0.08 + \frac{37}{75}j$$

$$F(s) = \frac{-8}{15}e^{-2t} + \frac{28}{75}e^{-5t} + (0.08 - \frac{37}{75}j)e^{-(1-3i)t} + (0.08 + \frac{37}{75}j)e^{-(1+3i)t}$$

2) S-domain equivalent

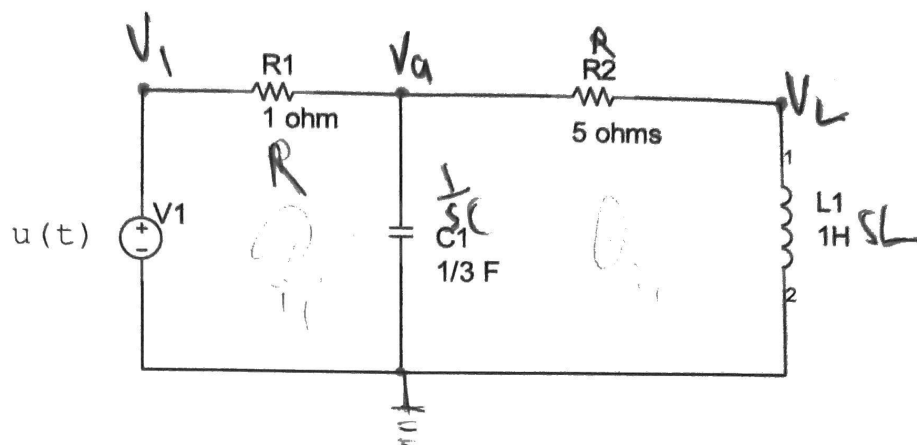

2.1: In the above circuit, the initial conditions are zero. Using s-transforms, find the voltage across the inductor for $t > 0$.

$$i_L = 0 \quad v_C = 0 \quad i_C = 0, \quad v_L = 0$$

$$\frac{V_a - \frac{1}{s}}{R_1} + V_a s C + \frac{V_a - V_L}{R_2} = 0 \quad -\frac{V_L}{sL} = \frac{V_L - V_a}{R_2} \quad V_a = \frac{+R_2 V_L}{sL}$$

$$\frac{V_L}{sL} + \frac{V_L - V_a}{R_2} = 0$$

$$+\frac{R_2 V_L}{sL} + V_L = -V_a$$

$$\frac{5V_L}{s} + V_L - \frac{1}{s} + \left(\frac{5V_L}{s} + V_L\right) \frac{s}{3} + \frac{1}{s} \left(\frac{5V_L}{s} + V_L - V_L\right) = 0$$

$$\frac{5V_L}{s} + V_L - \frac{1}{s} + \frac{5}{3}V_L + \frac{V_L s}{3} + \frac{V_L}{s} = 0 \quad V_L \left(\frac{5}{s} + 1 + \frac{5}{3} + \frac{s}{3} + \frac{1}{s}\right) = \frac{1}{s}$$

$$V_L \left(\frac{s^2 + 8s + 18}{3s}\right) = \frac{1}{s} \quad V_L = \frac{1}{s} \div \frac{s^2 + 8s + 18}{3s} \quad V_L = \frac{3}{s^2 + 8s + 18}$$


$$V_L = \frac{3}{(s+4+j\sqrt{2})(s+4-j\sqrt{2})} = \frac{A}{s+4+j\sqrt{2}} + \frac{B}{s+4-j\sqrt{2}}$$

$$3 = A(s+4-j\sqrt{2}) + B(s+4+j\sqrt{2}) \big|_{s=-4+j\sqrt{2}} \quad 3 = B(2j\sqrt{2}) \quad B = \frac{3}{2j\sqrt{2}}$$

$$3 = A(-2j\sqrt{2}) \big|_{s=-4-j\sqrt{2}} \quad A = -\frac{3}{2j\sqrt{2}}$$

$$V_L(t) = \frac{-3}{2j\sqrt{2}} e^{-(4+j\sqrt{2})t} + \frac{3}{2j\sqrt{2}} e^{-(4-j\sqrt{2})t}$$


3) Circuits and Differential Equations

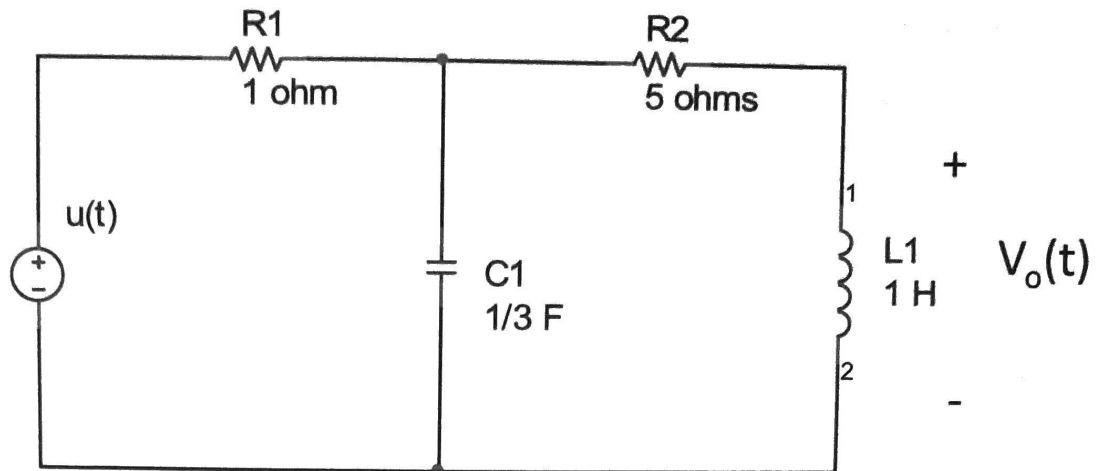

3.1: Draw the s-domain equivalent circuit. Assume all initial conditions are zero and the source is an arbitrary source.

3.2 Using impedances, determine the expression for $V_o(t)$. Consider using mesh analysis. Make one ratio.

3.1

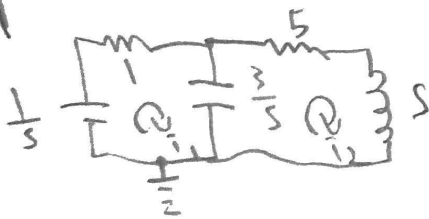

$$3.2: -\frac{1}{s} + i_1 + i_1 \frac{3}{s} - i_2 \frac{3}{s} = 0$$

$$\frac{3}{s} i_2 - \frac{3}{s} i_1 + 5 i_2 + i_2 s = 0$$

$$\frac{1}{s} + i_2 \frac{3}{s} = i_1 + i_1 \frac{3}{s} = i_1 \left(1 + \frac{3}{s}\right)$$

$$i_1 = \left(\frac{1}{s} + i_2 \frac{3}{s}\right) / \left(1 + \frac{3}{s}\right)$$


$$\frac{3}{s} i_2 - \frac{3(1 + 3 i_2)}{s(s+3)} + 5 i_2 + i_2 s = 0$$

$$i_2 = \frac{3}{s(18+8s+s^2)}; V_L = i_2 \cdot s \quad V_L = \frac{3s}{s(18+8s+s^2)} = \frac{3}{(s+4-j\sqrt{2})(s+4+j\sqrt{2})}$$

$$V_L = \frac{A}{s+4+j\sqrt{2}} + \frac{B}{s+4-j\sqrt{2}} \quad | \quad s = -4+j\sqrt{2} \quad B = \frac{3}{2j\sqrt{2}} \quad A = \text{complex conjugate}$$

$$V_L(t) = \frac{-3}{2j\sqrt{2}} e^{-(4+j\sqrt{2})t} + \frac{3}{2j\sqrt{2}} e^{-(4-j\sqrt{2})t}$$

4) RLC and initial conditions

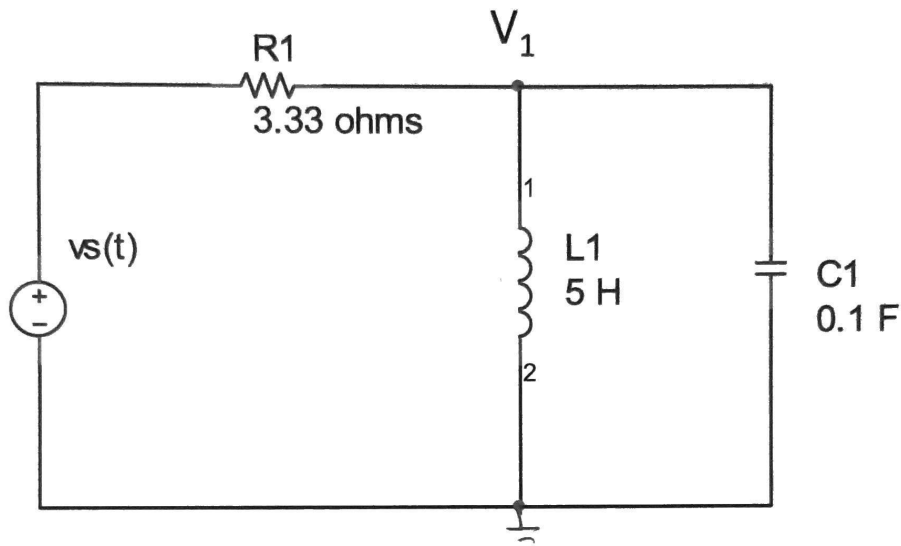

$$v_s(t) = 10u(t)$$

AND assume that -1A flows through the inductor and +5V is across the capacitor at $t=0$...i.e. $v_c(0)=5$ and $i_L(0)=-1$

4.1: Draw the s-domain equivalent with initial conditions.

4.2: Find the value of the voltage across the capacitor, $v_c(t)$, using nodal analysis (at node V1) and laplace.

4.1:

$$\frac{V_1 - \frac{10}{s}}{3.33} + \frac{V_1 + 5}{5s} + \frac{V_1 - \frac{5}{s}}{\frac{10}{s}} = 0$$

$$V_c = V_1 - \frac{5}{s}$$

4.2:

$$\frac{20 + 5s}{s^2 + 3s + 2} = V_1 = \frac{A}{(s+1)} + \frac{B}{(s+2)}$$

$$20 + 5s = A(s+2) + B(s+1)$$

$$s = -2 \mid 10 = B(-1) \quad B = -10 \quad s = -1 \mid 15 = A$$

$$V_1 = \frac{15}{(s+1)} + \frac{-10}{s+2} - \frac{5}{s}$$

$$V_c(t) = 15e^{-t} - 10e^{-2t} - 5$$