

Homework 2


- 1) Design a 4-bit D/A converter, with an output range of 0 to -15V. The digital LO/HI voltages are 0V/3.3V.

Each is 1V $-\frac{R_F}{R_1}(8V_1 + 4V_2 + 2V_3 + 1V_4) = -15$


$$\frac{3.3}{3.3} = 1 \quad -\frac{R_F}{R_1} = -\frac{1}{3.3}$$



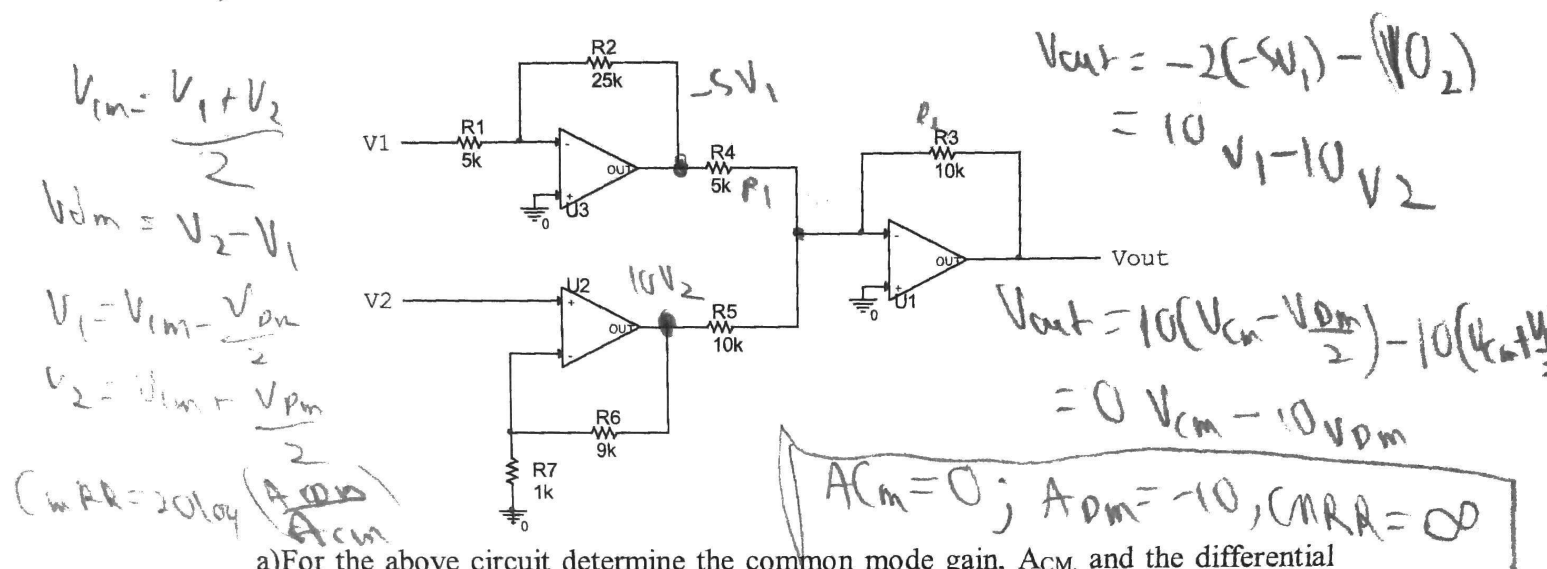2) Common mode and differential mode analysis. Assume the op-amps are ideal.



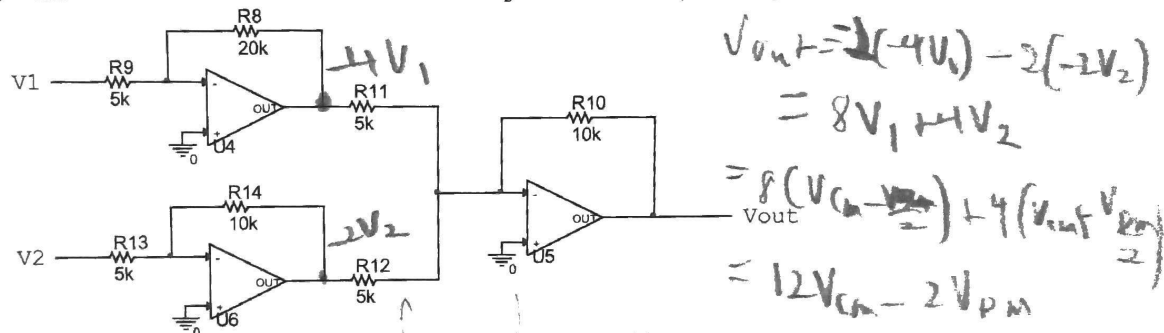a) For the above circuit determine the common mode gain, A_{CM} , and the differential gain, A_{DM} . Determine the Common Mode Rejection Ratio (CMRR).



b) For the above circuit determine the common mode gain, A_{CM} , and the differential gain, A_{DM} . Determine the Common Mode Rejection Ratio (CMRR).

c) For $V_2 = 4V$, $V_1 = 2V$, determine V_{CM} , V_{DM} and V_{out} .

d) For $V_2 = 101V$, $V_1 = 99V$, determine V_{CM} , V_{DM} and V_{out} .

e) Based on your parts c and d results, how would you characterize the above circuit as a difference amplifier (recalling that measuring differences is the important part of a difference amplifier).

Handwritten calculation for part c:

$$V_{out} = 8(2) + 4(4) = 32V$$

Handwritten calculation for V_{cm} in part c:

$$V_{cm} = 4 - \frac{V_{dm}}{2}$$

Handwritten calculation for V_{dm} in part c:

$$32 = 12(4 - \frac{V_{dm}}{2}) - 2V_{dm}$$

Handwritten calculation for V_{dm} in part c:

$$-18 = -V_{dm} \Rightarrow V_{dm} = 18V$$

Handwritten calculation for V_{cm} in part c:

$$V_{cm} = \frac{32 - 2(2)}{12} = 2.33V$$

Handwritten calculation for A_{cm} and A_{dm} in part e:

$$A_{cm} = 12; A_{dm} = -2$$

Handwritten calculation for CMRR in part e:

$$CMRR = 20 \log \left(\frac{-2}{12} \right) = -15.56$$

$$D = 8(aq) + 4(|o|) = V_{out} = 1196V$$

$$aq = V_{cm} - \frac{V_{Dm}}{2}$$

$$|o| = V_{cm} + \frac{V_{Dm}}{2}$$

$$V_{cm} = 100$$


$$V_{Dm} = 2$$

$$E = -4 + 1200 = 1196 \quad \text{from D}$$

$$-4 + 36 = 32 \quad \text{from C}$$

it works as intended

3) Difference amplifier

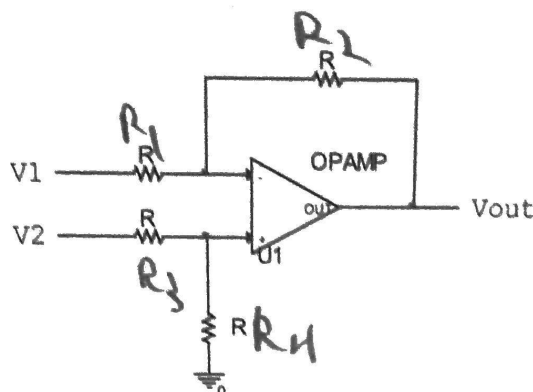

a) When considering gold band resistors (5% tolerance), approximately determine the worst case common mode rejection ratio for the above circuit.

$$V_{cm} = \frac{V_1 + V_2}{2}$$

R_1 and R_2 are
Related from R_3 + R_4

$$A_{cm} = \frac{R_4}{R_3 + R_4} \cdot \frac{1 + R_2}{R_1} - \frac{R_2}{R_1}$$

$$(MRR = -20 \log \left(\frac{A_{cm}}{A_{dm}} \right))$$

meaning A_{cm} and A_{dm}

$$A_{dm} = \frac{1}{2} \left(\frac{R_4}{R_3 + R_4} \cdot \frac{1 + R_2}{R_1} + \frac{R_2}{R_1} \right)$$

need to be as
far apart as
possible


$$A_{cm} = 1 - \frac{1.05}{.95} = -0.105$$

$$A_{dm} = \frac{1}{2} \left(1 + \frac{1.05}{.95} \right) = 1.05$$

$$(MRR = 20 \log \left(\frac{-0.105}{1.05} \right))$$


$$= -20 \text{ dB}$$

4) Differentiators/Integrators

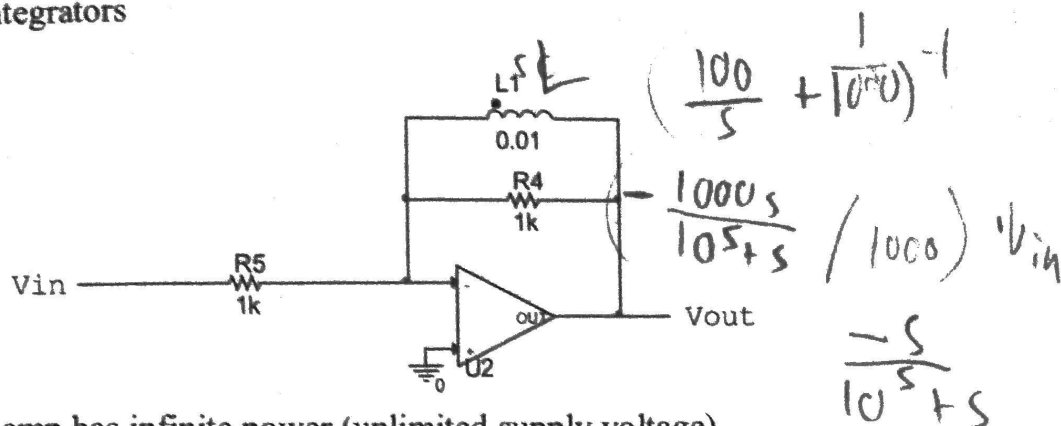

Assume the op-amp has infinite power (unlimited supply voltage)

- As frequency approaches zero (but is still greater than zero), what is the approximate (simplified) transfer function? What type of amplifier circuit corresponds to that transfer function?
- As frequency approaches infinity (large, but finite), what is the approximate (simplified) transfer function? What type of amplifier circuit corresponds to that transfer function?
- For the above circuit, sketch the Bode magnitude plot for $H(s) = V_{out}(s)/V_{in}(s)$. Include dB values in regions where the gain is constant. Indicate the slope of the plot where the gain is not constant. Identify any poles and zeros on the plot. (a log-log plot is provided on the next page.)

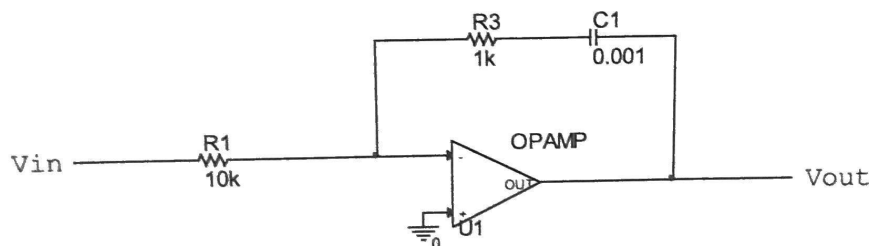

- As frequency approaches zero (but is still greater than zero), what is the approximate (simplified) transfer function? What type of amplifier circuit corresponds to that transfer function?
- As frequency approaches infinity (large, but finite), what is the approximate (simplified) transfer function? What type of amplifier circuit corresponds to that transfer function?
- For the above circuit, sketch the Bode magnitude plot for $H(s) = V_{out}(s)/V_{in}(s)$. Include dB values in regions where the gain is constant. Indicate the slope of the plot where the gain is not constant. Identify any poles and zeros on the plot. (a log-log plot is provided on the next page.)
- If $V_{in}(t) = 10\cos(1E9t) + 5V$, determine the output voltage as a function of time, $V_{out}(t)$.

$$4A: \frac{-s}{10^5 + s} = H(s) \quad s \rightarrow 0$$

$$H(0) = -s \cdot V_{in} \quad \text{Voltage follower}$$

$$B: H(\infty) = \frac{-\infty}{\infty} \cdot V_{in} = -\frac{s}{s} = -1 \quad \text{Inverting amplifier}$$

$$D: \left(1000 + \frac{1000}{s} \right) \div 10^4 = \frac{-(s+1)}{10s} = H(s)$$

$$s \rightarrow 0 \quad -\frac{1}{s \rightarrow 0}$$

$$\text{Inverting amplifier}$$

$$H(0) = -\infty$$

$$E: H(s) \rightarrow H(\infty) = \frac{-\infty}{\infty}$$

$$\text{Inverting Amp}$$

$$G:$$

$$\left(\frac{-1000 - \frac{1}{j10^4(0.001)}}{10k} \right) = A = -1 + j \frac{1}{10^4}$$

$$\sqrt{-1^2 + \left(\frac{1}{10^4}\right)^2} = 1 \rightarrow \text{inverted, } \rightarrow -1$$

$$\text{Thus } V_{out} = (10 \cos(10^4 t) - 5V)$$

