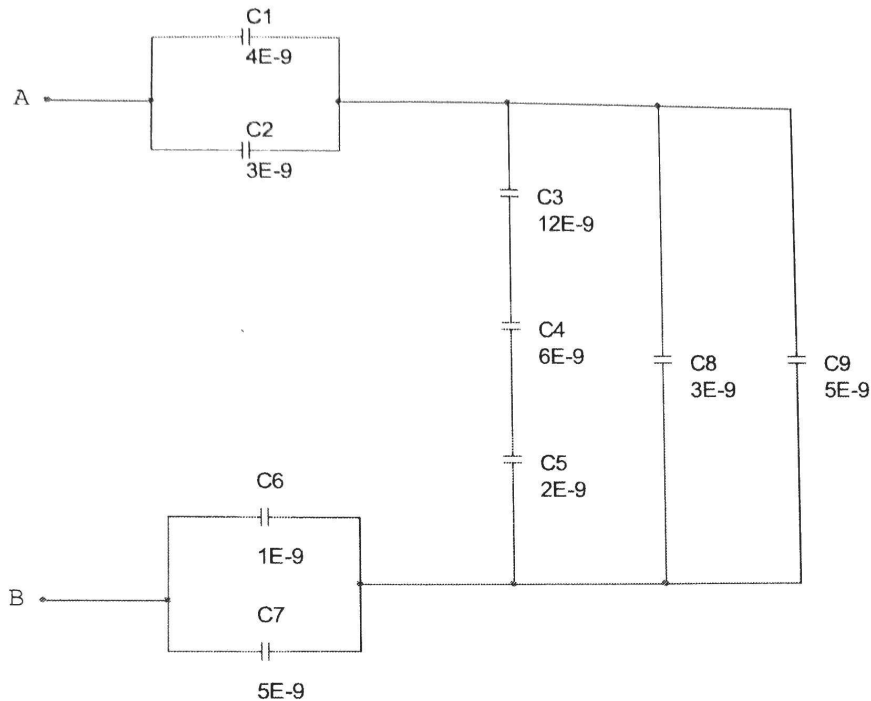


1) Capacitors and Inductors



1.1: For the above circuit, determine the equivalent capacitance between A and B.

$$C_{12} = C_1 + C_2 = 4 \times 10^{-9} + 3 \times 10^{-9} = 7 \times 10^{-9} \text{ F}$$


$$C_{345} = \left(\frac{1}{C_3} + \frac{1}{C_4} + \frac{1}{C_5} \right)^{-1} = 1.33 \times 10^{-9} \text{ F}$$

$$C_{34589} = C_{345} + C_8 + C_9 = 9.33 \times 10^{-9} \text{ F}$$

$$C_{67} = C_6 + C_7 = 6 \times 10^{-9} \text{ F}$$


$$C_{123456789} = \left(\frac{1}{C_{12}} + \frac{1}{C_{34589}} + \frac{1}{C_{67}} \right)^{-1} = 2.4 \times 10^{-9} \text{ F} = C_{AB}$$

2) Amplifier circuits

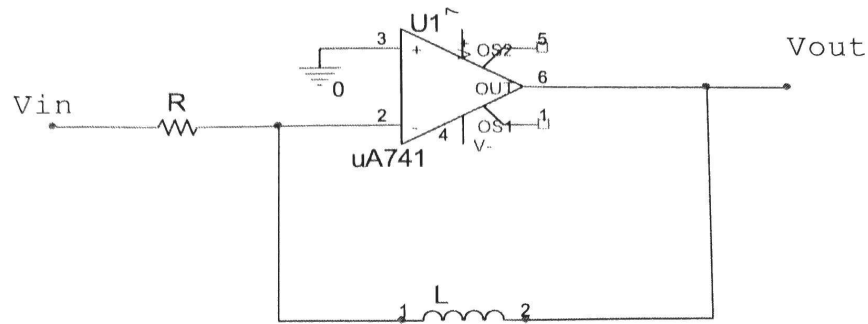

2.1: For the RL amplifier circuit, determine the relationship between V_{out} and V_{in} . As with RC amplifier circuits, KCL is a good starting point. (The power is taken out for simplicity but the op amp is powered).

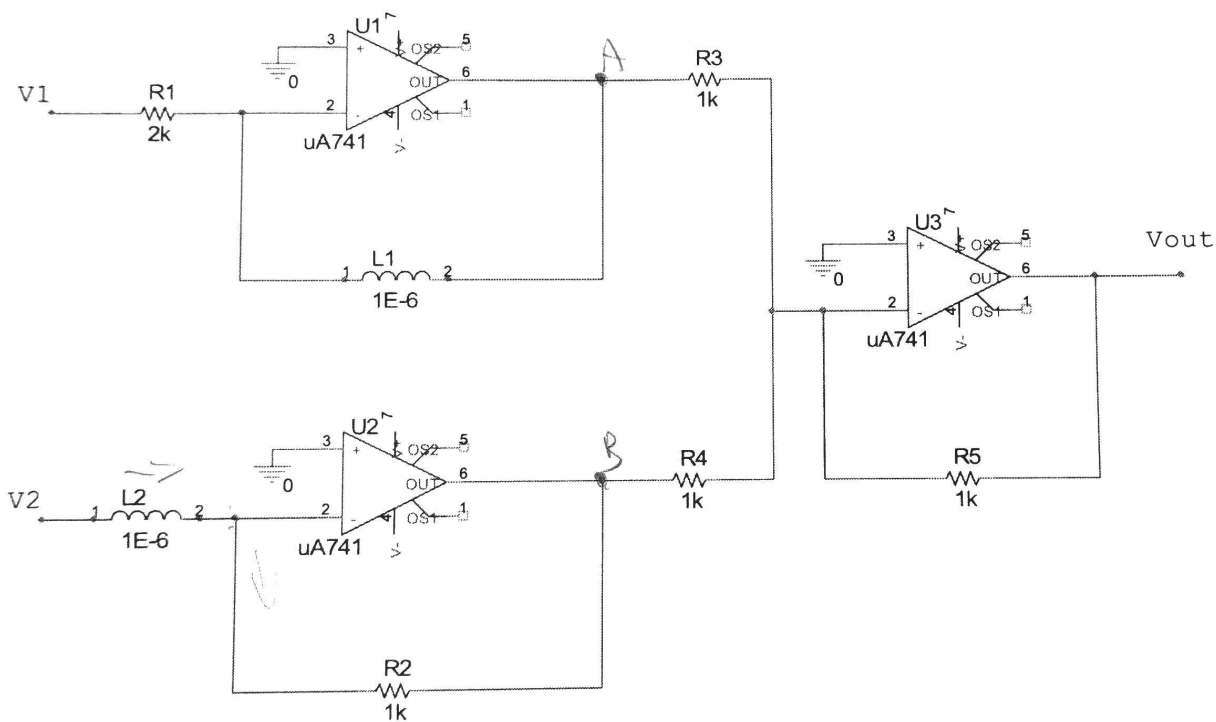2.2: In the circuit below $V_1 = V_2 = 4 \cos(300t)$. Determine V_{out}



2.1: ideal op amp kcl $V_A = 0$

$$\frac{V_{in}}{R} = i_1 \quad V_{out} = 0 - V_L = -L \frac{di}{dt} \quad \text{the } \frac{di}{dt} \text{ refers to } i_1 \quad V_{out} = -L \frac{di}{dt}$$

$$V_{out} = -L \frac{d}{dt} \left(\frac{V_{in}}{R} \right) = \boxed{V_{out} = -\frac{L}{R} \frac{dV_{in}}{dt}}$$

$$2.2: V_{out} = 0 - \frac{V R_2}{R_1} = -I_1 R_2 \quad \text{what is } I_1? \quad V_S = \frac{di}{dt} L$$


$$\frac{1}{L} \int V_S = I_1 \quad V_{out} = -\frac{R_2}{L} \int V_S dt$$

$$A+A: \frac{-1 \times 10^{-6}}{2000} (-\sin(3000t) 1200) = 6 \times 10^{-7} \sin(3000t)$$

$$A+B: \frac{-1000}{1 \times 10^{-6}} \left(\frac{4}{300} \sin(3000t) \right) = -1.33 \times 10^{-7} \sin(3000t)$$

$$V_{out} = -(6 \times 10^{-7} \sin(3000t)) - (-1.33 \times 10^{-7} \sin(3000t)) = \boxed{1.33 \times 10^{-7} \sin(3000t)}$$

3) Voltage/Current continuity

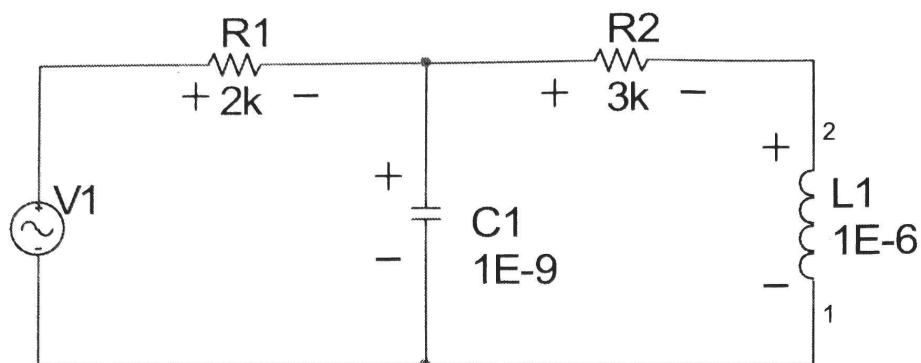

In the above circuit, the voltage is defined as follows:

$$V1 = \begin{cases} 5V & t < 0 \\ 10V & 0 < t \end{cases} \quad (\text{the voltage source turns on at } t = 0)$$

3.1: Determine a mathematical expression for the source. **Meaning use the unit step function $u(t)$ in your expression.**

3.2: At $t = 0^-$ (just before the voltage changes), for the polarities indicated, determine the voltage across each component and the current through each component.


3.3: At $t = 0^+$ (just after the voltage changes), determine the voltage across each component and the current through each component for the polarities indicated in the circuit.

3.1: $V_1(t) = V_a u(t)$ $V_a u(t) = \begin{cases} V_a & t \geq 0 \\ \frac{V_a}{2} & t < 0 \end{cases}$ $V_a = 10V$

3.2:

Component	Voltage	Current
R1	2V	1mA
R2	3V	1mA
C1	3V	0mA
L1	0	1mA

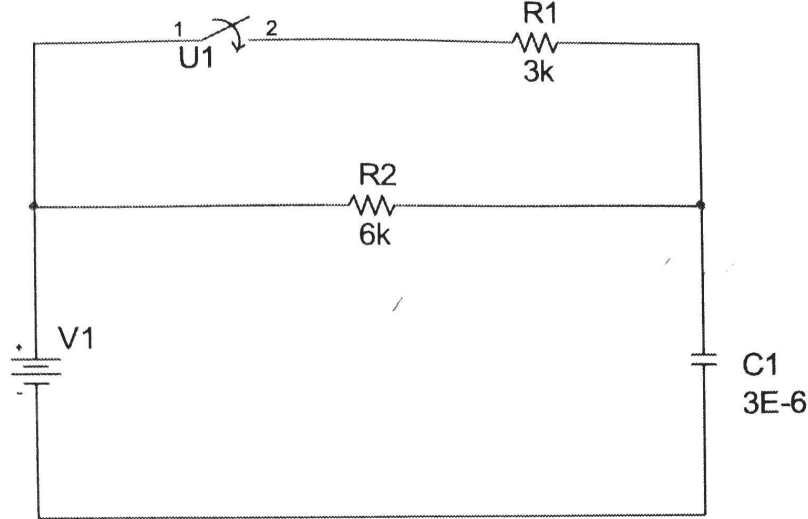Inductor is a short
cap is open.
Simple voltage divider



In the above circuit, the voltage source turns on at $t=0$, $V1 = 15u(t)$. At $t = 1\text{ms}$, switch $U1$ closes.

4.1: Determine the voltage across the capacitor for a function of time for $0 < t < 1\text{ms}$

4.2: Determine the voltage across the capacitor for $t > 1\text{ms}$.

4.1:

$$\frac{dV_c}{dt} + \frac{V_c}{R_{eq}C} = \frac{15}{R_{eq}C}$$

$\tau = R_{eq}C$
 $= 0.001\text{s}$

$$V_c(t) = A_1 e^{-t/\tau} + B_1$$

$$A_1 e^{-55.6t} + B_1$$

τ $0 + B_1 = 15 \rightarrow B_1 = 15$ 0 $A_1 + B_1 = 0 \rightarrow A_1 = -15$

$$V_c(t) = -15e^{-55.6t} + 15$$

4.2 : circuit reduction

$$R_{eq} = 2k$$

$$\frac{dV_C}{dt} R_{eq} C + V_C = 15$$

$$\tau = RC = 0.006$$

$$V_C(t) = A_1 e^{-t/\tau} + B_1 \quad t < 1ms$$
$$= A_1 e^{-167(t-0.001)} + B_1$$

∞

$$0 + B_1 = 15 \quad B_1 = 15$$

0

$$A_1 + B_1 = 0 \rightarrow A_1 = -15$$


$$-15 e^{-35.6(0.001)} + 15 = 0.811$$

$$A_1 + B_1 = 0.811$$

$$A_1 = 0.811 - 15 = -14.189$$

$$V_C(t) = -14.2 e^{-167(t-0.001)} + 15$$

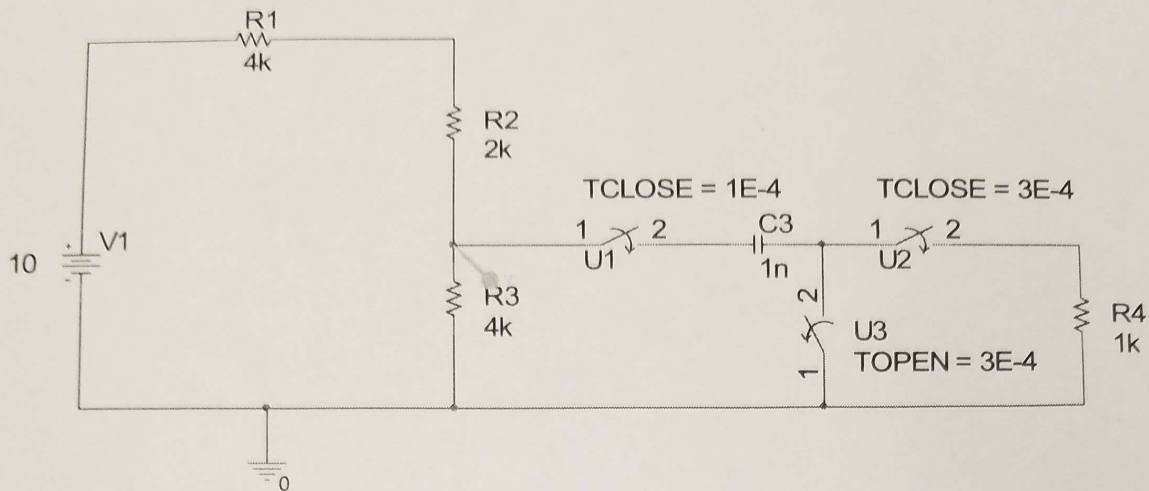5) Thevenin Equivalent and Switching Circuits



In the above circuit, the voltage source turns on at $t = 0$. Switch U1 closes at $t = 0.1 \text{ ms}$. Switch U2 closes and switch U3 opens at $t = 0.3 \text{ ms}$ (effectively putting resistor R3 in series with C3 at $t = 0.3 \text{ ms}$).


5.1: Determine the voltage across R3 as a function of time for $t > 0$.

Three regions of interest

$t < 0.1 \text{ ms}$

$0.1 \text{ ms} < t < 0.3 \text{ ms}$

$0.3 \text{ ms} < t$

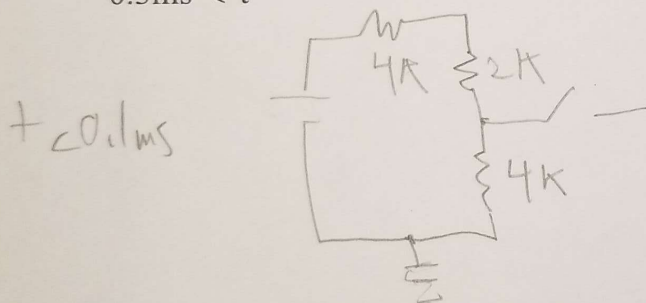

$$V_{R3} = 10 \frac{R3}{R1 + R2 + R3} = 4V \text{ at } t < 0.1 \text{ ms}$$

$0.1 \text{ ms} < t < 0.3 \text{ ms}$

Thevenin:


$$V_{TH} = 4V$$

$$R_{TH} = \frac{4V}{0.0016667A} = 2400 \Omega$$


$$I_{norton} = \frac{10V}{6k} = 0.001666A$$

continued on next page \rightarrow
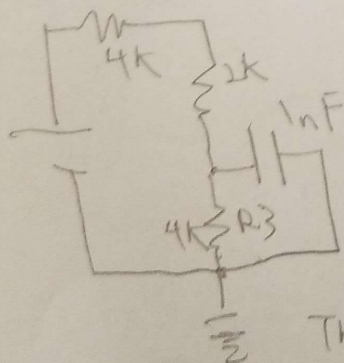
$$\tau = R \cdot C = 2.4 \times 10^{-6}$$



Therm:

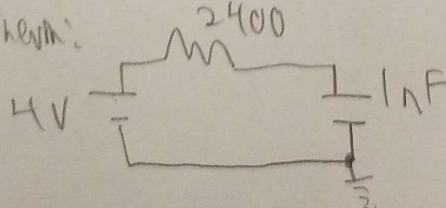

$$0.1 \text{ ms} < t < 0.3 \text{ ms}: V_C(t) = V_{CN} + V_{CF}$$

$$V_{R3} = V_C \quad V_C(t) = A_1 e^{-\frac{(t-0.0001)}{\tau}} + A_2$$

$$V_C(t=0.1 \text{ ms}^-) = V_C(t=0.1 \text{ ms}^+) = 0$$

$$0 = A_1 e^0 + A_2 \quad A_2 = -A_1$$

$$\text{final: } V_C(t) = 4V$$

$$4 = A_1 e^{\frac{(-0.0003-0.0001)}{2.4 \times 10^{-6}}} - A_1$$

↓
ignore

$$4 = -A_1 \quad A_1 = -4 \quad A_2 = 4$$


$$V_C(t) = V_{R3}(t) = -4 e^{-\frac{(t-0.0001)}{2.4 \times 10^{-6}}} + 4$$

$$t > 0.3 \text{ ms}$$



$$\frac{10V(4k)}{4k+2k+4k} = V_{R3} = 4V$$

3.3:

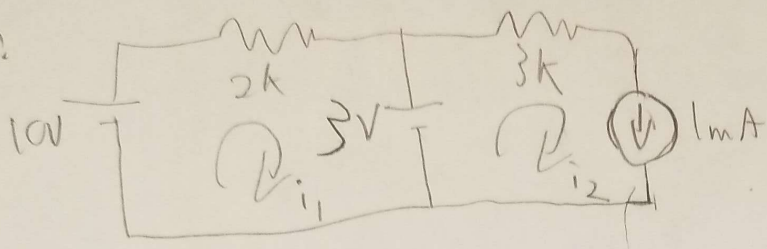

$$i_{12k} = 7V$$

$$i_1 = 0.0065A$$

Component	Current	Voltage
R_1	$3.5mA$	$7V$
R_2	$1mA$	$3V$
$C1$	$2.5mA$	$3V$
$L1$	$-1mA$	$7V$

$$i_1 - i_2 = 2.5mA$$

$$-5V + i_2 3k + V_{L1} = 0$$

$$V_{L1} = 5V + i_2 3k$$

$$=$$