

Laboratory 16: Matlab and Data Analysis

(Edit this document as needed)

Partner 1: _____Saaif Ahmed_____

Partner 2: _____John Gonzalez_____


Partner 3: _____ (if needed)

Part A


Brief description of the Matlab diode plotting experiment:

To delve deeper into Matlab's capabilities of plotting and to determine the difference between a standard diode and an ideal diode and the same for an LED.

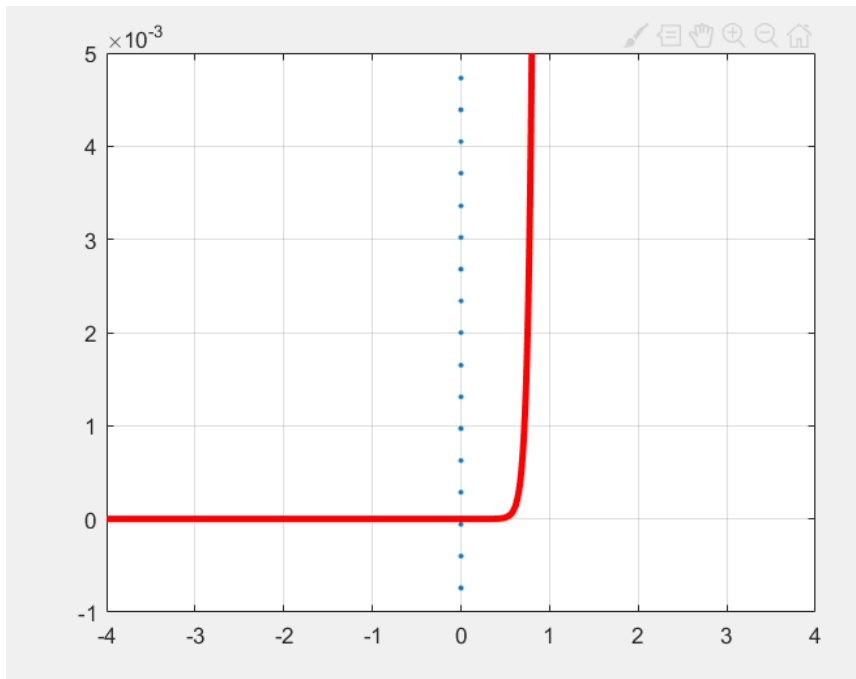Plot of the diode current (I_D) vs. the diode voltage (V_D) for a standard diode. (Matlab)



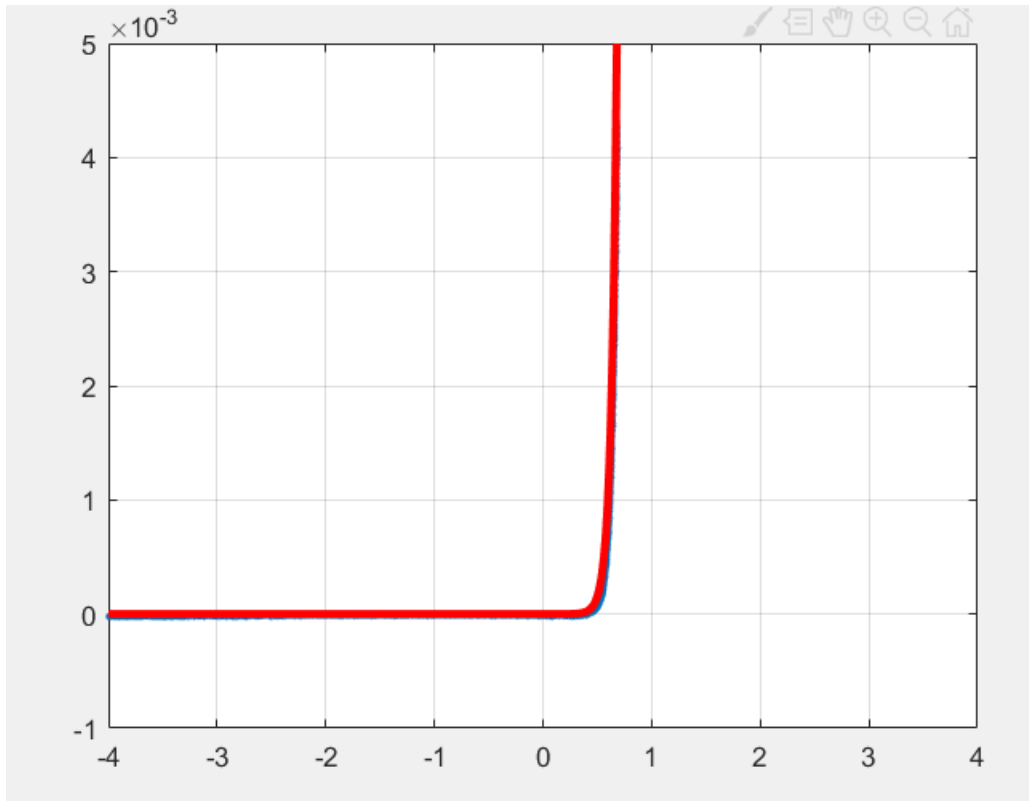
Plot of the experimental I_D - V_D and the calculated I_D using $I_D = I_s \left[\exp\left(\frac{V_D}{nV_T}\right) - 1 \right]$ for a standard diode. (Matlab)




Value of I_S and n in your fitted curve.

I_S	$1e-8[A]$
n	2

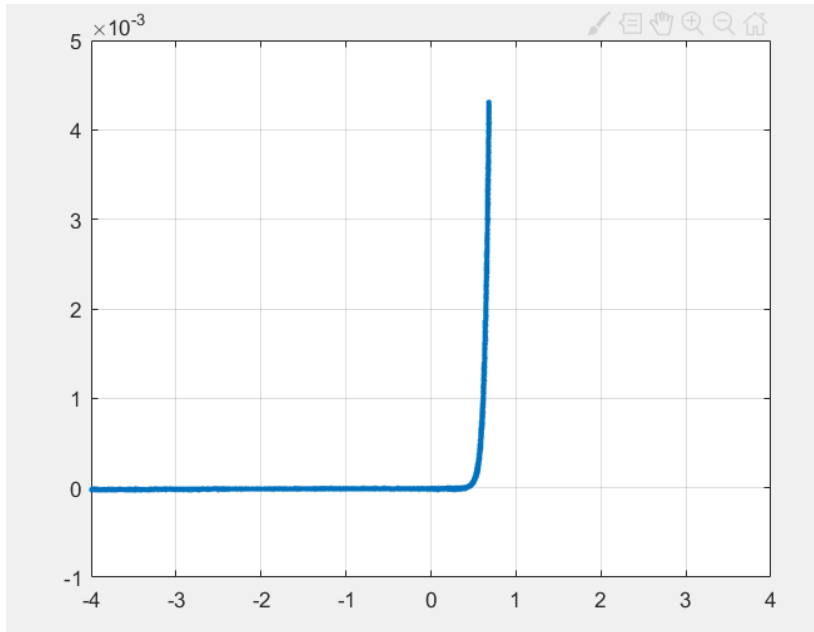Plot of the diode current (I_D) vs. the diode voltage (V_D) for a LED. (Matlab)



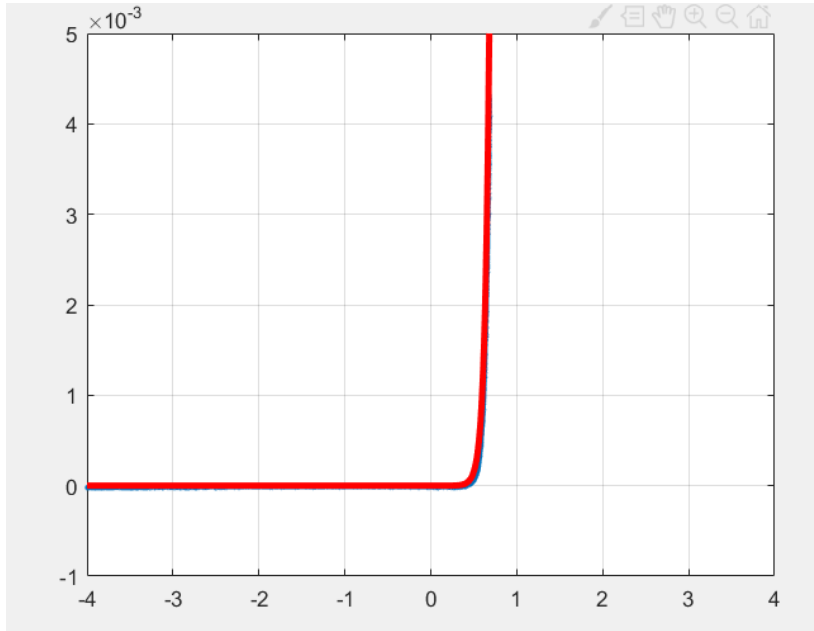Plot of the experimental I_D - V_D and the calculated I_D using $I_D = I_s \left[\exp\left(\frac{V_D}{nV_T}\right) - 1 \right]$ for a LED. Matlab)



Value of I_s and n in your fitted curve.

I_s	$1e-7[A]$
n	2

Experimental and analytical plots verification by TA/Instructor. _____HC_____

Part B


Brief description of the Load Line experiment:

To reference the load of a circuit in the form of $I=AV+B$ and to be able to analyze graphically the operational points of circuit components(diodes).

Mathematical expression for the current through the resistor in terms of the source voltage (V_s) and the resistance, R .

$$I=(-1/R)V+(V_s/R)$$

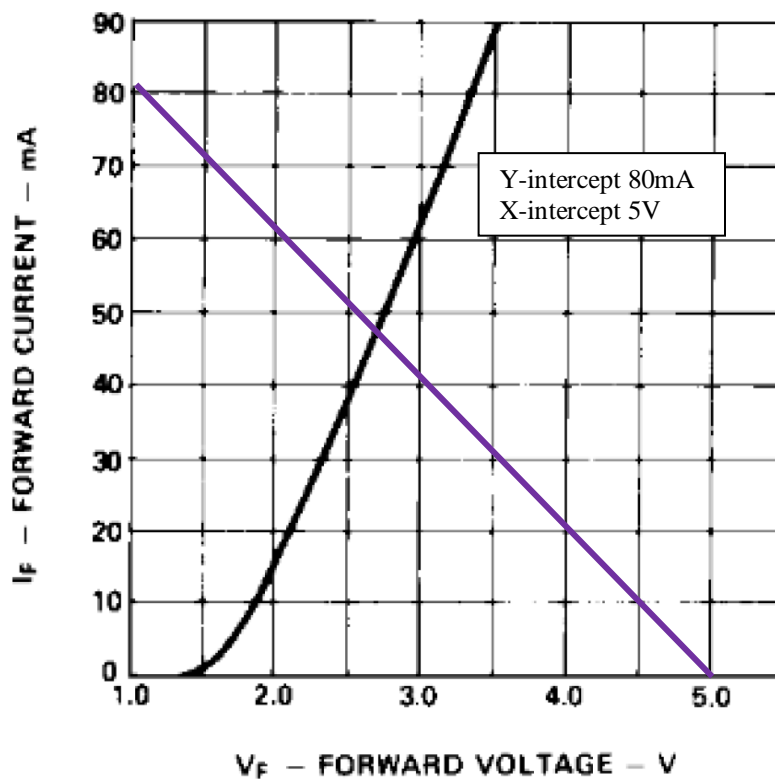Plot of load line on the following experimental curve.




Load line plot verification by TA/Instructor. _____HC_____

Approximate diode (resistor) current and diode voltage using the load line analysis on the above plot.

I_D	0.048[A]
V_D	2.7[V]

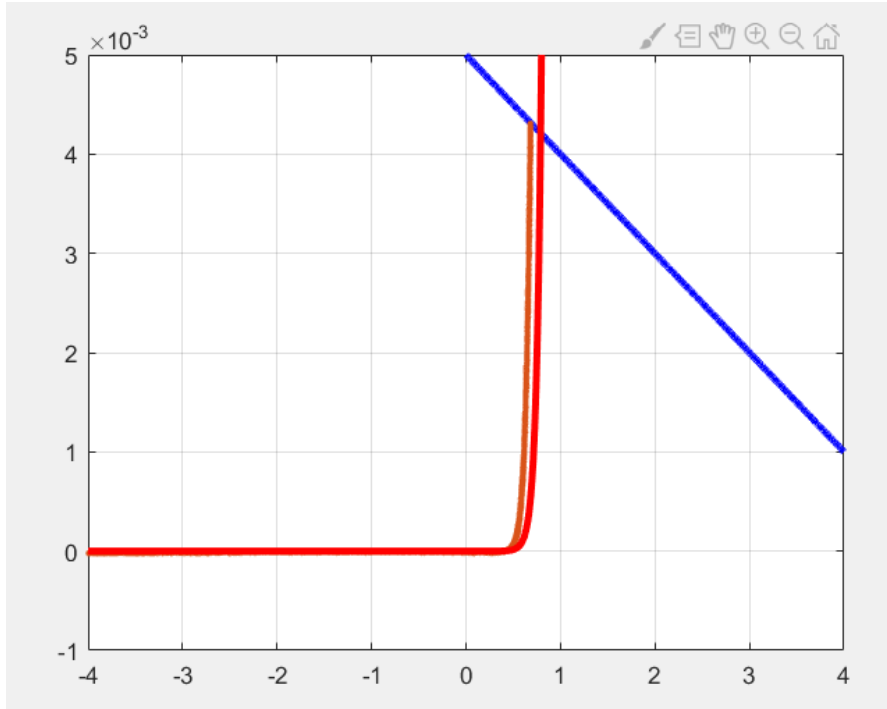
Plot with load line for standard diode using experimental data from part A.



Approximate diode (resistor) current and diode voltage using the load line analysis on the above plot.

I_D	0.005[A]
V_D	0.67[V]

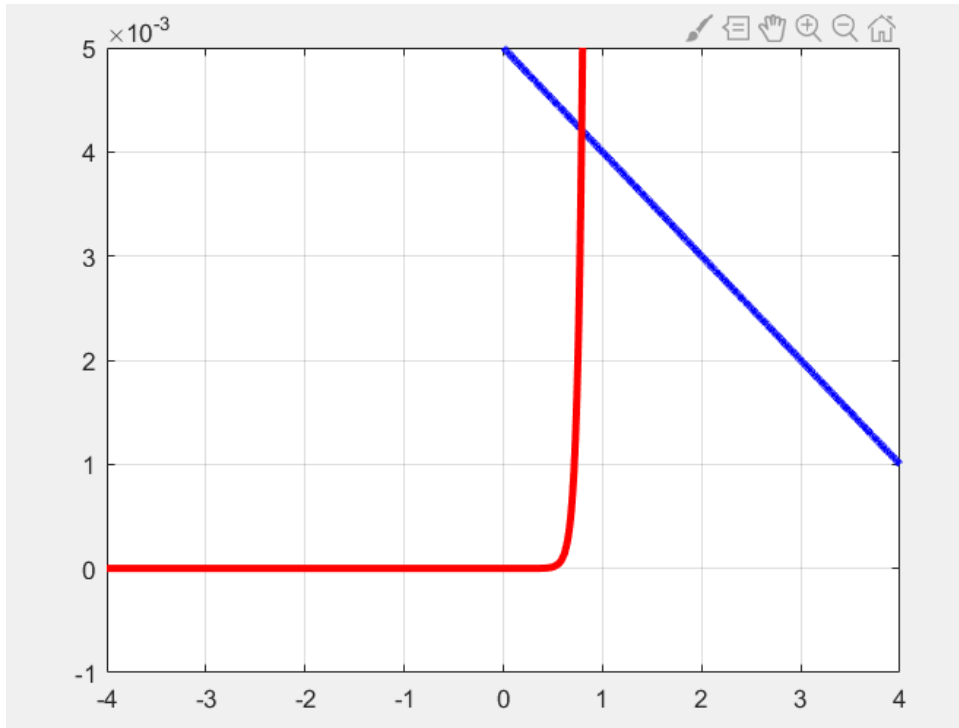Plot with load line for LED using experimental data from part A.



Approximate diode (resistor) current and diode voltage using the load line analysis on the above plot.

I_D	0.004[A]
V_D	0.8[V]