

Circuits

Exam 2

COVID Spring 2020

1.	/25
2.	/25
3.	/25
4.	/25
Total	/100

Name Saif Ahmed


Notes:

- 1) If you are stuck on one part of the problem, choose ‘reasonable’ values on the following parts to receive partial credit.
- 2) You don’t need to simplify all your numerical calculations. For example, you can leave square root terms in radical form.

Name Saqif Ahmed

1) Short Answer - (25 pts)

Derivations in the Time Domain

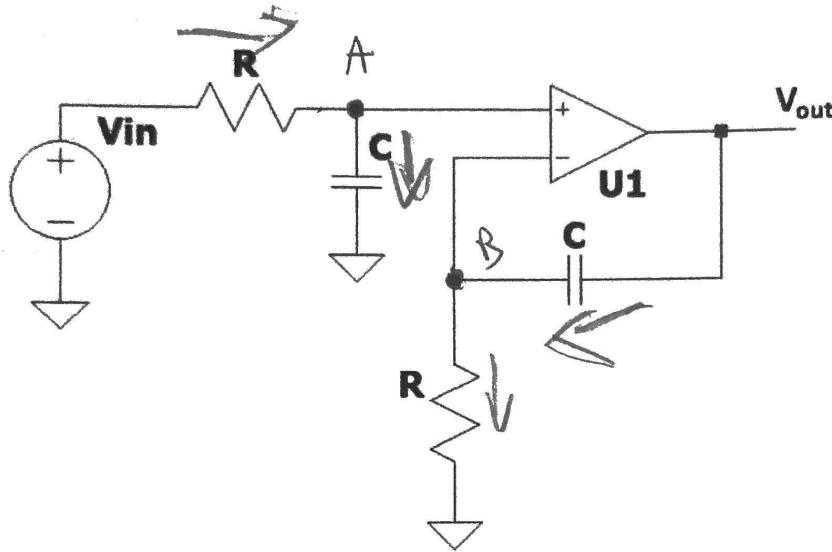

1.1: (10 pts) Derive the relationship between V_{in} and V_{out} . Hint: Use what you know about ideal op amps and KCL at nodes.

Do NOT use impedances, s-domain conversion to solve.

$$\begin{aligned} \text{KCL at } A: \quad & \frac{V_{in} - V_A}{R} = I_{CA} \\ & = C \frac{dV_A}{dt} \end{aligned}$$

KCL at B:

$$I_{CB} = V_B / R$$

$$\frac{V_B}{R} = C \frac{d(V_{out} - V_B)}{dt}$$

$$= \frac{dV_{out}}{dt} - C \frac{dV_B}{dt}$$

$$\text{Knowing that } V_A = V_B \quad C \frac{dV_B}{dt} = \frac{V_{in} - V_A}{R}$$

$$\frac{V_A}{R} = C \frac{dV_{out}}{dt} - \frac{V_{in} - V_A}{R}$$

$$\frac{V_A}{R} = C \frac{dV_{out}}{dt} - \frac{V_{in}}{R} + \frac{V_A}{R}$$

$$\left(\frac{V_{in}}{RC} = \frac{dV_{out}}{dt} \right) \Rightarrow V_{out} = \frac{1}{RC} \int V_{in} dt$$

1.2: (15 pts) Circle all cases where the initial condition must be included in the definition in the s-domain. The diagram below is given as a reference for one of four examples of initial condition source configurations. **Draw and label the other schematics then write equations below each for full credit.**

a. Definition of $V_L(s)$ for initial condition source in series with inductor


Equation: $\underline{V_L(s)} = sL \underline{I_L(s)} - L \underline{I(0^-)}$

b. Definition of $I_L(s)$ for initial condition source in series with inductor

Equation: _____

c. Definition of $V_L(s)$ for initial condition source in parallel with inductor

Equation: _____

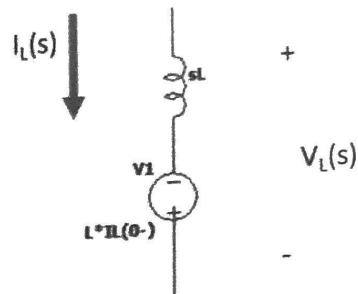

d. Definition of $I_L(s)$ for initial condition source in parallel with inductor

Equation: $\underline{I_L(s)} = \frac{\underline{I(0^+)}}{s} + \frac{\underline{V_L}}{sL}$

e. Definition of $V_C(s)$ for initial condition source in series with capacitor

Equation: $\underline{V_C(s)} = \frac{1}{sC} \underline{I_C(s)} + \frac{\underline{V_C(0^+)}}{s}$

f. Definition of $I_C(s)$ for initial condition source in series with capacitor


Equation: _____

g. Definition of $V_C(s)$ for initial condition source in parallel with capacitor




Equation: _____

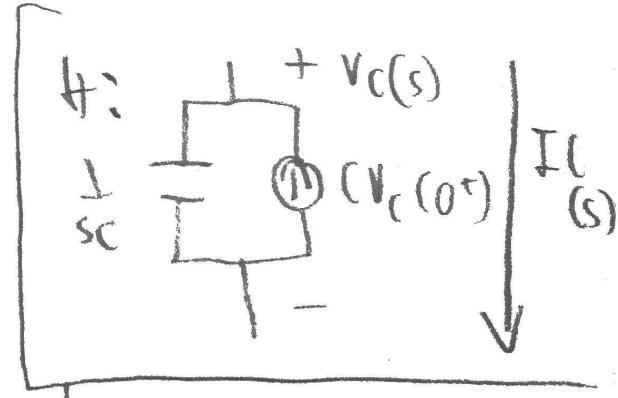h. Definition of $I_C(s)$ for initial condition source in parallel with capacitor


Equation: $\underline{I_C(s)} = \frac{\underline{V_C}}{s} \cdot sC - C \underline{V_C(0^+)}$



Initial condition schematics:

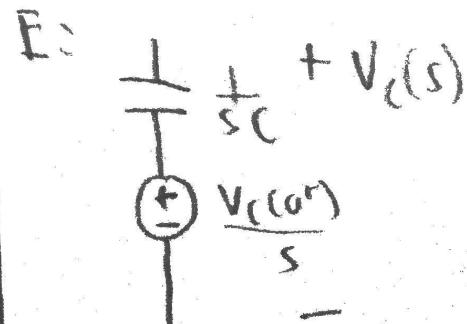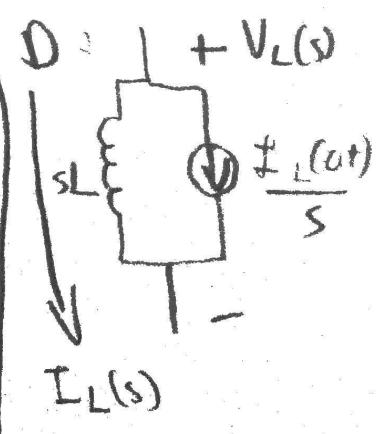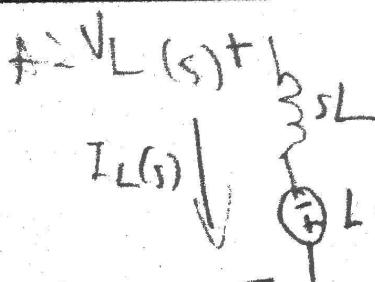

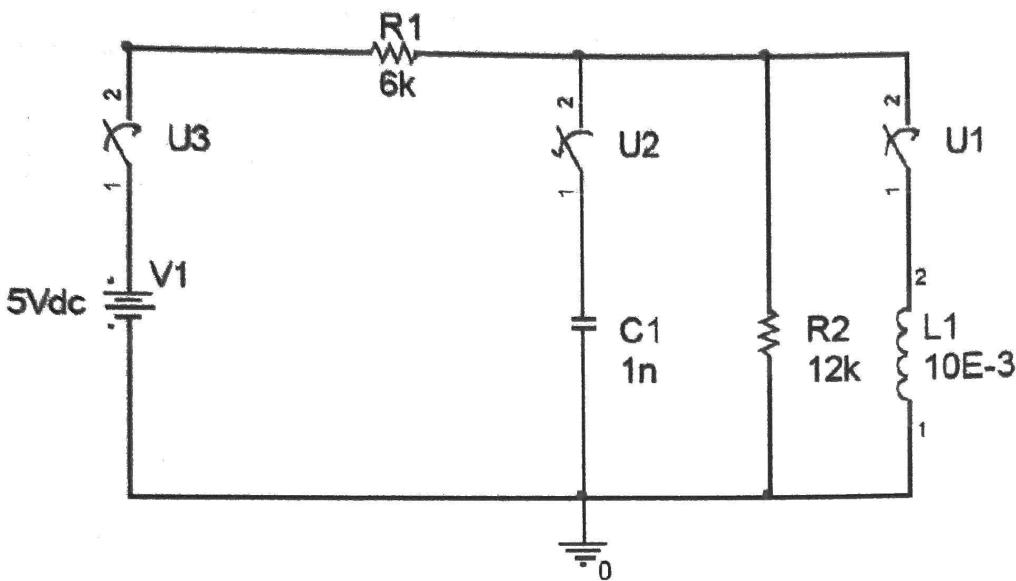2) First Order - Switching Differential Equations (25 pts)



THIS PROBLEM MUST BE DONE BY DIFFERENTIAL EQUATIONS!

In the above circuit,


1. For $t < 0$, switches U1 and U3 are open and U2 is closed.
2. At $t = 0$, U3 closes
3. At $t = 3\mu s$, U2 opens and U1 closes

2.1: Find the current from the source for $t < 0$. (You MUST draw the circuit for this time region!)




$I_s(t < 0)$	0 A
--------------	-----

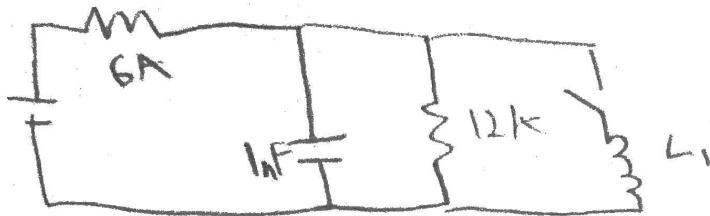2.2: Find the current from the source for $0 < t < 3\mu s$. (You MUST draw the circuit for this time region!)



Theremin

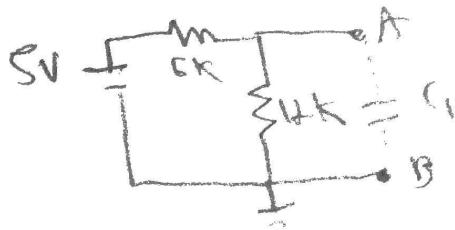


$$V_{TH} = V_{AB}$$

$$= \frac{5(12k)}{18k} = \frac{10}{3}$$



Thevenin:

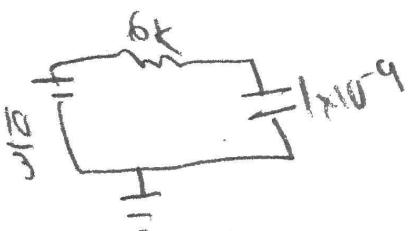

$$R_{TH} = 6k$$

$$V_C(0^+) = 0V$$

$$V_C(\infty) = \frac{10}{3}$$

$$\text{Guess } V_C(t) = Ae^{-\frac{t}{6\mu s}} + B$$

$$Ae^{-\frac{t}{6\mu s}} + B = 0 \quad |t=0^+ \\ A + B = 0$$

$$V_C(t) = -\frac{10}{3} e^{-t/6\mu s} + \frac{10}{3}$$

$$B = \frac{10}{3} \quad |t=\infty \quad A = -\frac{10}{3}$$



$$\frac{dV_C}{dt} \cdot C = I_S = -\frac{1}{6\mu s} \cdot -\frac{10}{3} e^{-\frac{t}{6\mu s}}$$

$$= \left(\frac{5000000}{9} e^{-\frac{1}{6\mu s} t} \right) 10^{-9}$$

$I_S(0 < t < 3\mu s)$	$\left(\frac{5000000}{9} e^{-\frac{1}{6\mu s} t} \right) 10^{-9}$
-----------------------	--

$I_S(0 < t < 3\mu s)$	$\left(\frac{5000000}{9} e^{-\frac{1}{6\mu s} t} \right) 10^{-9}$
-----------------------	--

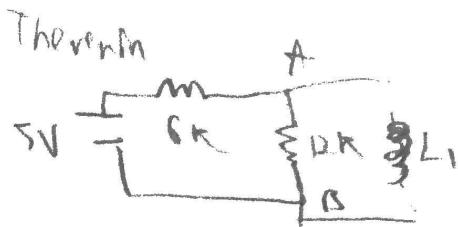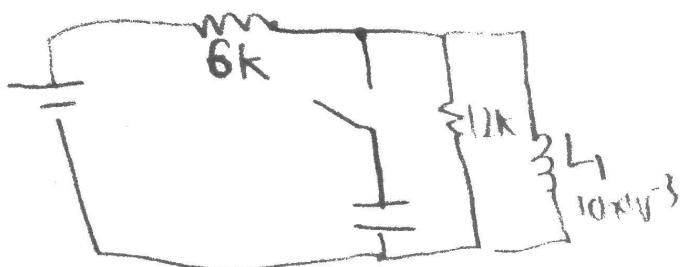2.3: Find the current from the source for $t > 3\mu s$. (You MUST draw the circuit for this time region!)



$$V_{TH} = \frac{5(12k)}{18k}$$

$$R_{TH} = 6k$$



$$I_L = \frac{1}{s}$$

knows that $I_L = A e^{-t/1.66 \times 10^{-6}} + B$ $I_L(3\mu s) = 0A$ $I_L(\infty) = \frac{10}{3} \div 6 = 5A$


$$I_L(0) = A e^0 + B = 0$$

$$I_L(0) = B = \frac{5}{9}$$

$$I_L = I_s = -\frac{5}{9} e^{-t/1.66 \times 10^{-6}}$$

$I_s(t > 3\mu s)$	$I_s = -\frac{5}{9} e^{-60000t} + \frac{5}{9}$
-------------------	--

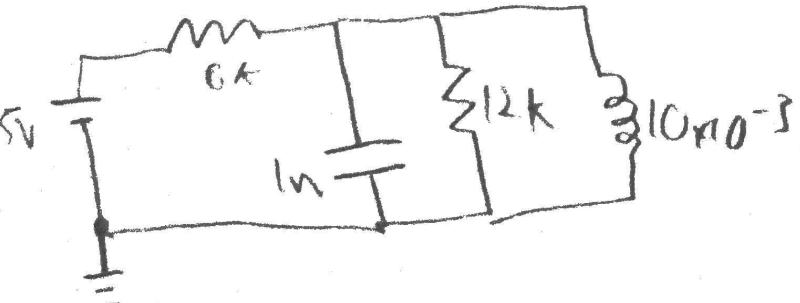2.4: 1 pt If U2 stays closed at $t=3\mu s$ how would you approach finding the current through the inductor $I_L(t)$? Draw the circuit and write the first two major steps to solve the problem quickly. (I understand this may be somewhat subjective to perspective but I am curious...)




Step 1. Source convert to get everything parallel. Simplify

Step 2: calculate new initial conditions.

3) Second Order - Differential Equations (25 pts)

S1 opens at t=0

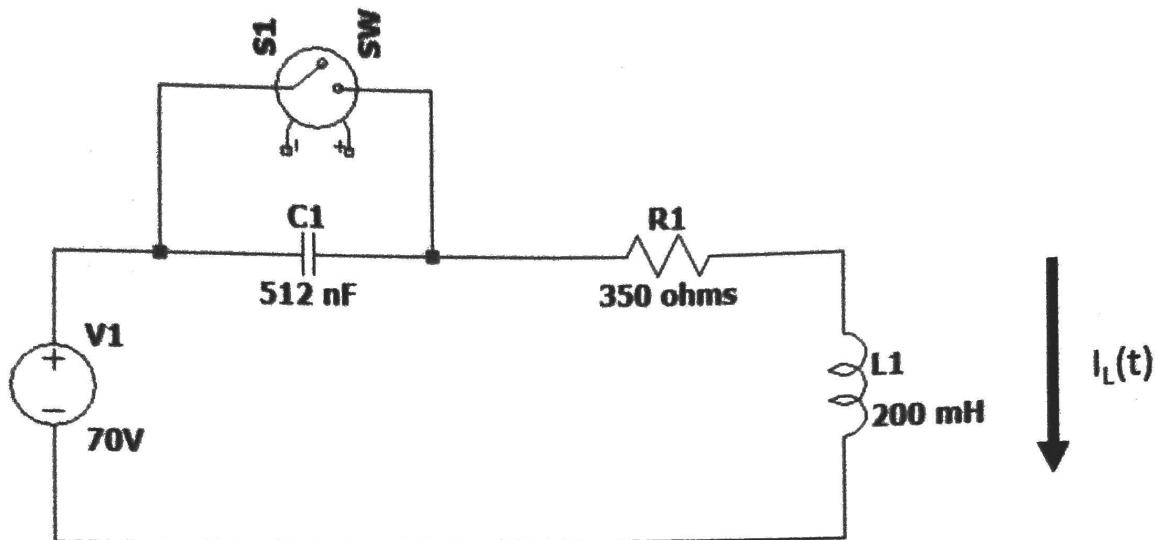

THIS PROBLEM MUST BE DONE BY DIFFERENTIAL EQUATIONS!

3.1: Find $I_L(t)$ for $t > 0$.

(cap is shorted across Series RL for $t < 0$.)

$$I_{L(0^-)} = 0.2 \text{ A} \quad \alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$V_C(0^-) = 0 \text{ V} \quad \omega_0 > \alpha \quad \text{underdamped 2 complex roots}$$

$$V_C(\infty) = 70 \text{ V} \quad \beta = 3000$$

Guess that $V_C(t) = e^{-875t} (A_1 \cos(3000t) + A_2 \sin(3000t)) + A_3$

$$\frac{dV_C}{dt} \cdot (= I_C(0^-) = -3000 e^{-875t} A_1 \sin(3000t) + 30000 e^{-875t} A_2 \cos(3000t)$$

$$- 875 e^{-875t} A_1 \cos(3000t) - 875 e^{-875t} A_2 \sin(3000t)$$

$$V_C(0^+) = 70V = A_3 \cdot 512 \times 10^{-9}$$

$$-3000 e^0 A_1 \sin(0) + 30000 e^0 A_2 \cos(0) - 875 e^0 A_1 \cos(0) - 875 e^0 A_2 \sin(0)$$

$$V_C(0^+) = 0V = 0(A_1 \cos(0) + A_2 \sin(0)) + 16$$

$$A_1 + 70 = 0V$$

$$(30000 A_2 - 875 A_1) \cdot 512 \times 10^{-9} = 16$$

$$A_1 = -70 \quad A_2 = \frac{2635}{24}$$


$$I_L(t) = I_C(t) = \frac{dV_C}{dt} \cdot 512 \times 10^{-9} = (2.1 \times 10^5 e^{-875t} \sin(3000t) + 329375 e^{-875t} \cos(3000t) + 61250 e^{-875t} \cos(3000t) - 96067.7 e^{-875t} \sin(3000t)) \cdot 512 \times 10^{-9}$$

$$I_L(t) = (340625 e^{-875t} \cos(3000t) + 306067.7 e^{-875t} \sin(3000t)) \cdot 512 \times 10^{-9}$$

$I_L(t)$ for $t > 0$	$\frac{1}{5} e^{-875t} \cos(3000t) + 0.16 e^{-875t} \sin(3000t)$
----------------------	--

4) Second Order Laplace (25 pts)

S1 opens at t=0

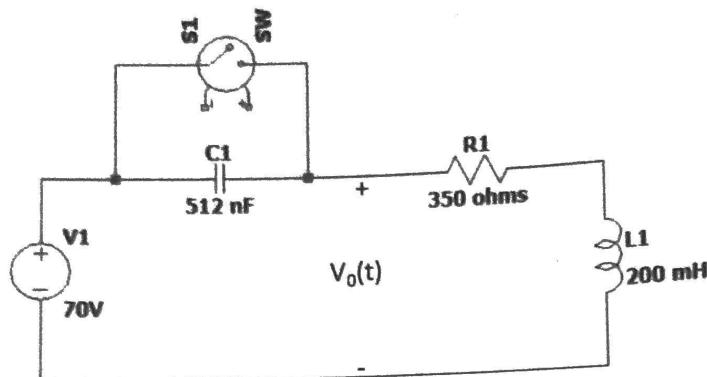


THIS PROBLEM MUST BE DONE BY LAPLACE
 specifically conversion of components into an
 s-domain circuit!

4.1: Find $V_o(t)$ for $t > 0$ using Laplace from the s-domain equivalent circuit. Note: $V_o(t)$ is the voltage across R_1 AND L_1 .

$$L \cdot I(0^+) = 200 \times 10^{-3} \cdot \frac{70}{350}$$

$$= 0.04$$

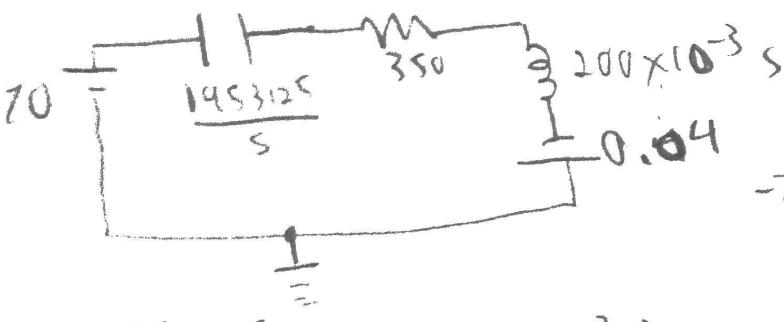

$$-70V + i_1 \frac{1953125}{s} + i_1 350 + i_1 200 \times 10^{-3}s - 0.04 = 0$$

$$i_1 \left(\frac{1953125}{s} + 350 + 200 \times 10^{-3}s \right) = 70.04$$

$$i_1 = 70.04 / \left(\frac{1953125}{s} + 350 + 200 \times 10^{-3}s \right)$$

$V_o(t)$ for $t > 0$

OR Next page & boxed

$$i_1 = \frac{70.04}{\frac{1955125}{s} + \frac{350s}{s} + \frac{.2s^2}{s}} = \frac{70.04 s}{.2s^2 + 350s + 1955125}$$

$$= \frac{-350 \pm \sqrt{350^2 - 4(.2)(1955125)}}{2s+2} = -875 \pm 3000 i$$

$$i_1 = \frac{70.04 s}{(s+875+3000i)(s+875-3000i)} = \frac{A}{s+875+3000i} + \frac{B}{s+875-3000i}$$

$$70.04s = A(s+875-3000i) + B(s+875+3000i)$$

$$\text{for } s = -875 + 3000i \quad A = 70.04(-875 + 3000i)$$

$$B = 70.04(-875 - 3000i)$$

$$\text{For VL: } C = 70.04(-875 + 3000i)^2 \cdot .2$$

$$D = 70.04(-875 + 3000i)^2 \cdot .2$$

$$V_o(s) = i_1 R_1 + i_1 s L - 0.04$$

$$V_o(t) = -6(285 + 210120i)e^{-(875 + 3000i)t} + 6(285 - 210120i)e^{-(875 - 3000i)t}$$

$$-115347125 - 73542000i e^{-(875 + 3000i)t}$$

$$+ 115347125 - 73542000i e^{-(875 - 3000i)t} - 0.04$$

4.2: How would you approach making sure that your answer from Problem 3.1 ($i_L(t)$) corresponds with your answer in Problem 4.1 ($V_o(t)$)?

take $V_o(t)$ and use that in a series RL circuit
 $\int L \frac{dV_o(t)}{dt} = i_L(t)$ in problem 3.1

Extra credit (5 pts): Calculate whether your answers correspond to one another.