 


Saaif Ahmed  
Section 3


10/28/19  
ahmeds7

660 HW 8


7.6:



7.7:

 


 ~~7.10 Yes, The J and K together because it is J-K.~~



7.10: I don't think it is possible. You'd have to alter the metastability states with logic gates external to the device. Logic gates tend to fail in that regard.


7.11: Tie J and R together

 

8.13: It counts multiples of 2 up to the given maximum value.


## HW # 8 resub

7.6.

 

\* I had the correct idea I just messed up the pin labels.

7.7

 

\* I should have realized that the ~~pins~~ inputs should have matched a J-K Flip Flop. I see now that Q relates with J and Q-bar relates to K in order to create the desired Flip Flop.

7.10: In addition to what I said already I forgot to mention that the Flip Flop triggers on an edge which a logic gate cannot perform Combinatorially.

8.3: QD states the up or down counting. Loads occur ~~at~~ at the 0000/1111 case. Analyze from 1000~1111. 8, 9, 10, 11, 12, 13, 14, 15, 7, 6, 5, 4, 3, 2, 1, 0. So it starts from 8 counts up to 1111 then loads in 7 and counts down, then it cycles. Which means if we observe three bits it goes 0, 1, 2, 3, 4, 5, ~~6~~, 7, 7, 6, 5, 4, 3, 2, 1, 0. It counts up to 7 then counts down from 7.