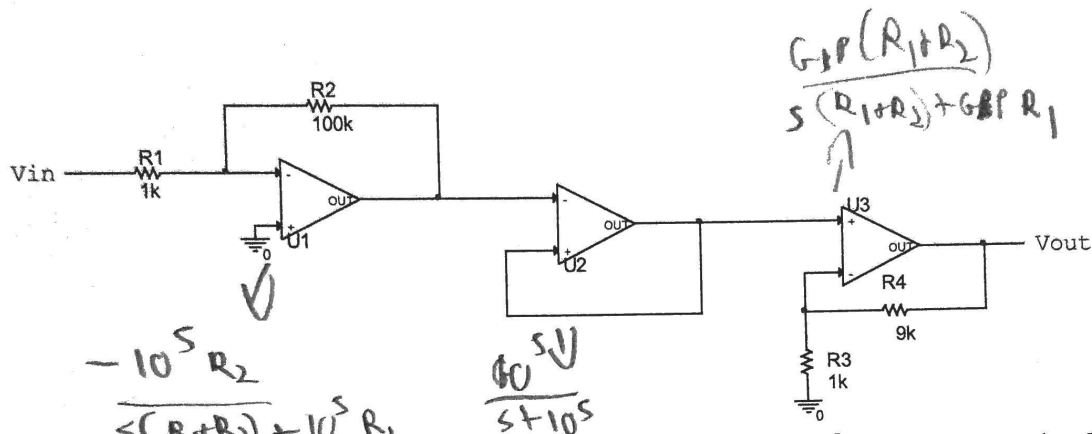


Homework 5

Reading: Chapter 2.5-2.8

1) Gain-Bandwidth Product




- a) For amplifiers with a gain-bandwidth product of 10^5 [rad/s], plot the Bode magnitude for the above circuit. (Be careful, the low pass filter characteristics are associated with the op-amp, not the overall circuit.)


$$\text{Total } H(s) = \frac{-10^5}{s + 10^{-3}} \cdot \frac{10^5}{10^5 + s} \cdot \frac{10^5}{s + 10^4}$$

Bode Plot:

pole

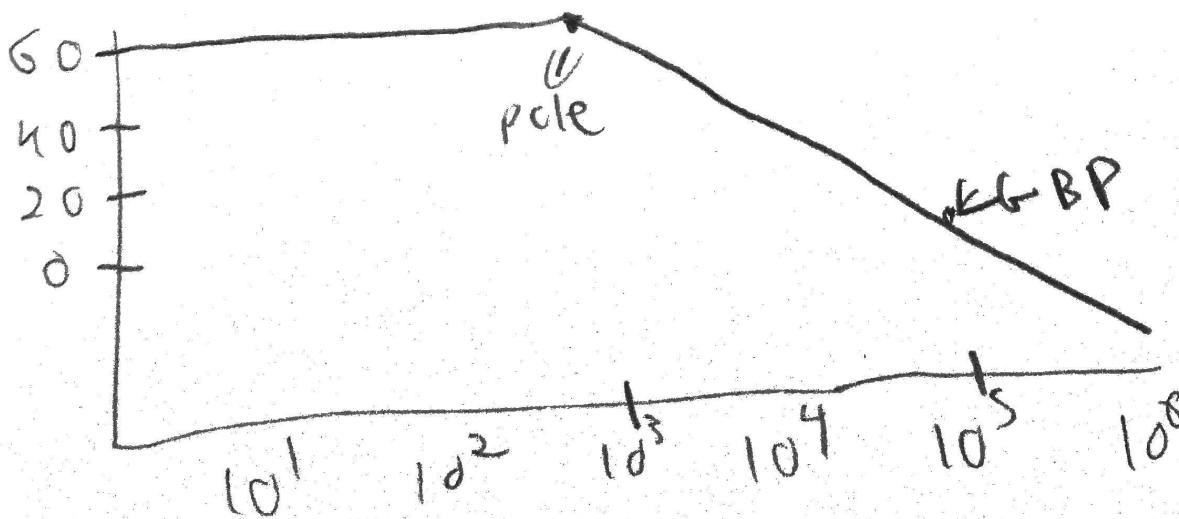

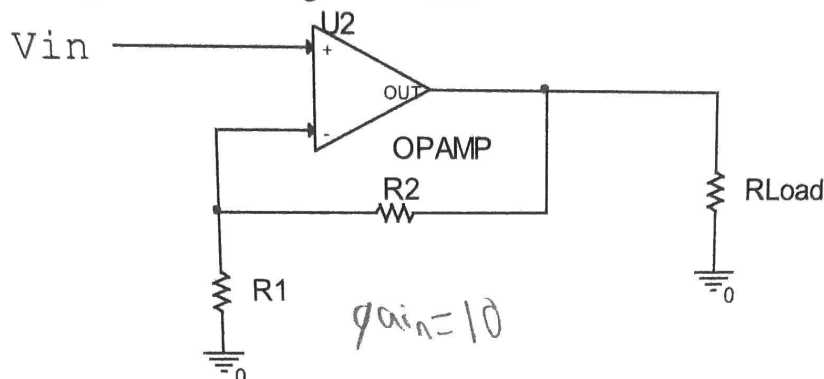2) Op-amp limiting factors – Voltage Saturation




Circuit/Spec sheet parameters


- 1) The saturation voltages for the above op-amp are 15/-15V.
- 2) The saturation output current for the above op-amp is +/- 20mA.
- 3) The slew rate for the above op-amp is 4V/ μ s.

For the following input signals, determine if the output appears as would be expected in an ideal circuit. Include sketches of the output voltage.

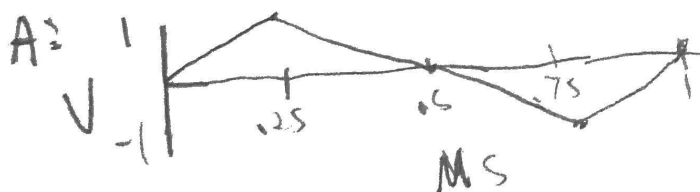
- a) $R1 = 100$, $R2 = 900$, an open circuit load, and V_{in} is 4Vpp triangle wave with zero offset voltage and a period of 1 μ s.
- b) $R1 = 100$, $R2 = 900$, an open circuit load, and V_{in} is 0.2Vpp square wave with zero offset voltage and a period of 4 μ s.
- c) $R1 = 100$, $R2 = 900$, a 1k Ω load, and V_{in} is 2Vpp triangle wave with a 1V offset voltage ($V_{max} = 2V$, $V_{min} = 0V$) and a period of 2ms.
- d) $R1 = 100$, $R2 = 900$, an open circuit load, and V_{in} is 2Vpp triangle wave with a 1V offset voltage ($V_{max} = 2V$, $V_{min} = 0V$) and a period of 2ms.




slew rate affects the amplitude

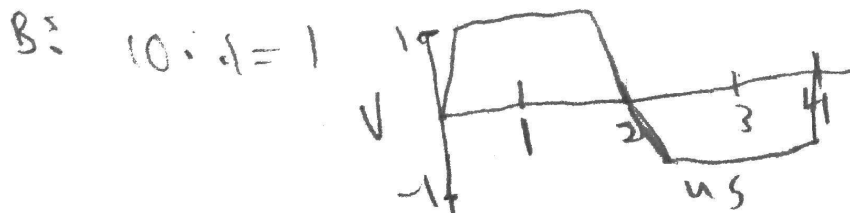

achieves expected value

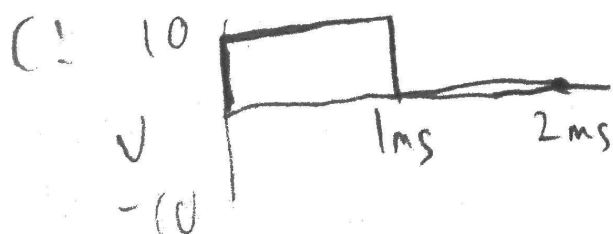

saturation ~~voltage~~ current

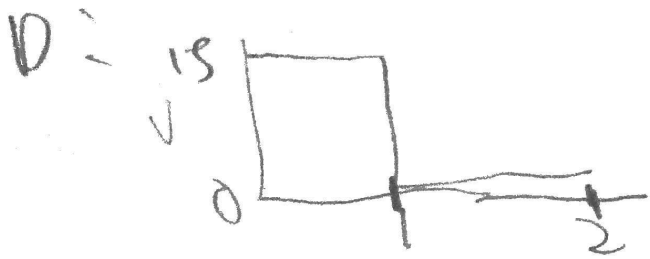

Saturation voltage caps