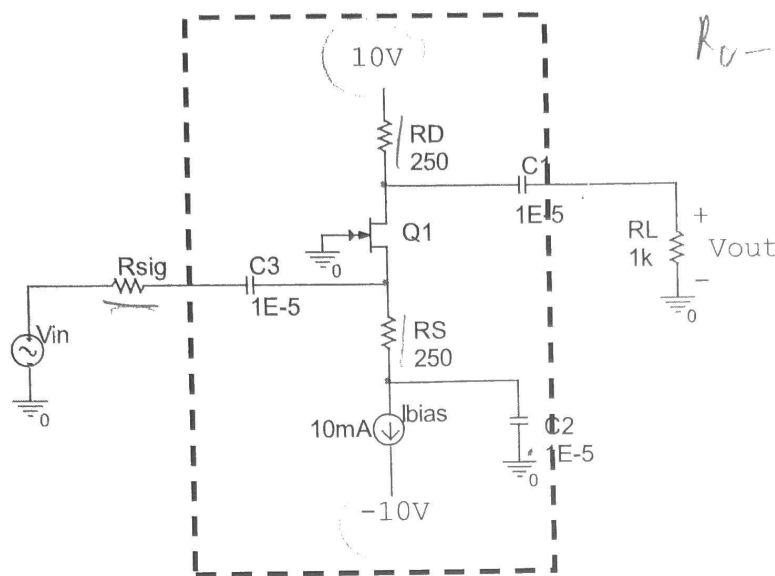


Homework 13


Reading: 7.1, 7.2-5 (FET discussion)
Problem 1) Common Gate



The NMOSFET in the above circuit has characteristics $V_{TN} = 2.2V$, and $K_n = 40 \text{ mA/V}^2$
(If you used $K_n = 400$, you do not need to redo your work.)

(Same DC bias circuit as HW12)

- $I_D = 10 \text{ mA}$ $g_m = 0.02 \text{ S}$
- Sketch the small signal model of the circuit.
 - For $R_{sig} = 0$ and $R_L \rightarrow \infty$, determine the open circuit gain, $A_{vo} = V_{out}/V_{in}$.
 - Using the dashed box to define the input and output impedance, find R_{in} and R_{out} .
 - Redraw the circuit, using the general amplifier model with R_{in} , R_{out} and A_{vo} .
 - What is the maximum value of R_{sig} such that the 'first' parenthesis term ($R_{in}/(R_{in} + R_{sig})$) has a magnitude greater than 0.8.

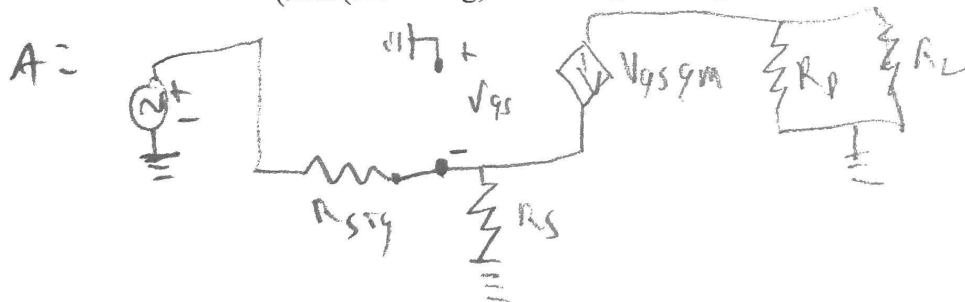

B: $R_{sig} \rightarrow 0 \Rightarrow V_{in} = V_{gs}$


$V_{out} = V_{RD}$

$$\frac{V_{out}}{V_{in}} = \frac{-250 \cdot g_m \cdot (-V_{in})}{V_{in}} = 2.08 = A_{vo}$$


$$C: \quad \underline{R_{in} = 250 \Omega \leq R_s}$$

$$\underline{R_{out} = R_D = 250 \Omega}$$

$$e: \quad \frac{250}{250 + R_{sig}} > 18 \quad \underline{R_{sig} < 62.9}$$

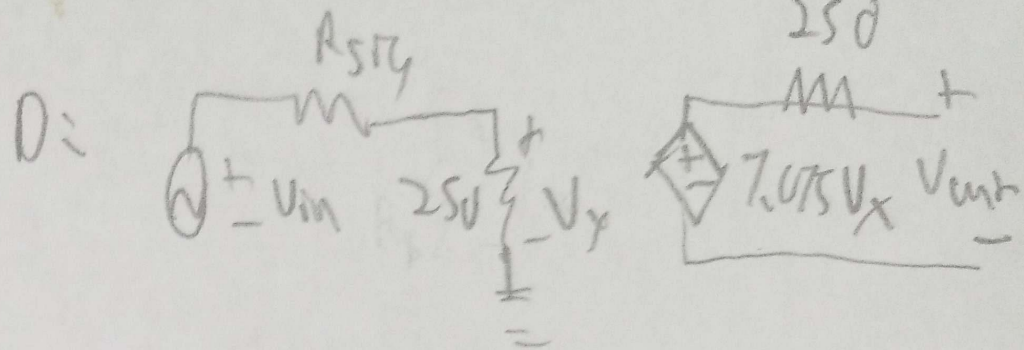


Problem 2) Common Drain

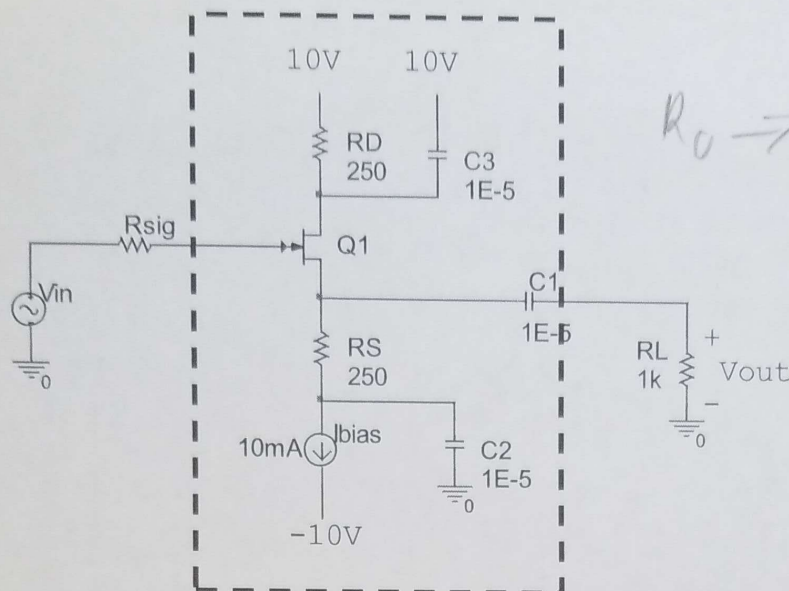

The NMOSFET in the above circuit has characteristics $V_{TN} = 2.2\text{V}$, and $K_n = 40\text{ mA/V}^2$
(If you used $K_n = 400$, you do not need to redo your work.)


(Same DC bias circuit as HW12) $\rightarrow I_D = 10\text{mA}$ $V_{GS} = 2.91\text{V}$ $V_{DS} = 16.4\text{V}$ $g_m = 0.0284$

- Sketch the small signal model of the circuit.
- For $R_{sig} = 0$ and $R_L \rightarrow \infty$, determine the open circuit gain, $A_{vo} = V_{out,o}/V_{in,o}$.
- Using the dashed box to define the input and output impedance, find R_{in} and R_{out} .
- Redraw the circuit, using the general amplifier model with R_{in} , R_{out} and A_{vo} .
- What is the maximum value of R_{sig} such that the 'first' parenthesis term ($R_{in}/(R_{in}+R_{sig})$) has a magnitude greater than 0.8? (This is kind of a trick question.)

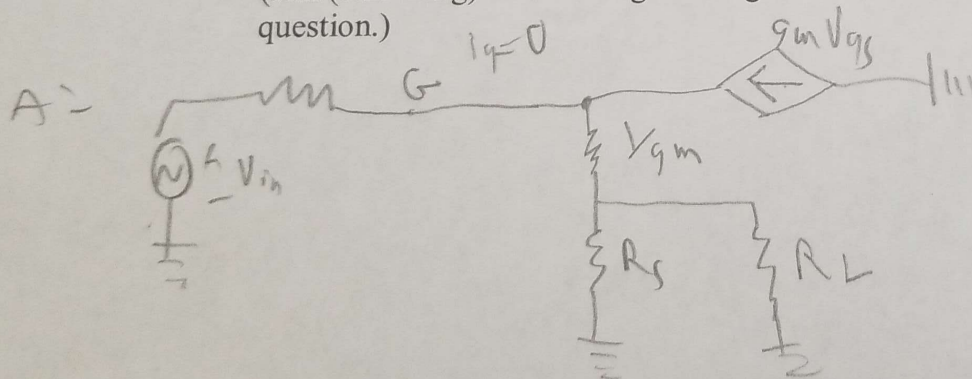


$$B: V_{out} = \frac{R_S}{R_S + \frac{1}{g_m}} \cdot V_{in} \quad A_v = \frac{R_S}{R_S + \frac{1}{g_m}} = 0.88$$

C)

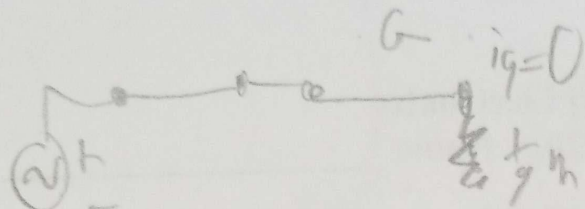


$$\underline{R_{in} = 0}$$

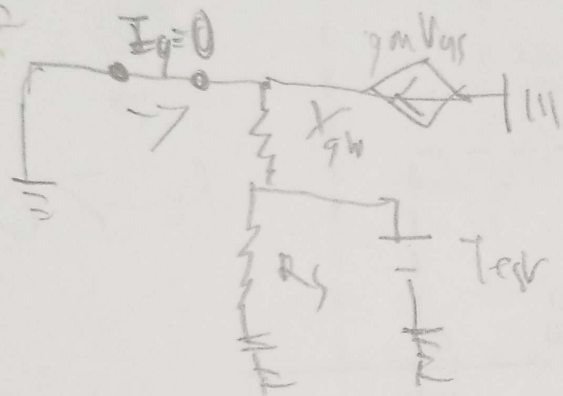

$$I_{test} = \frac{V_t}{R_s} + \frac{V_t - V_{gs}}{\frac{1}{g_m}} \quad V_t = I_{test} R_{out}$$

$$I_{test} = \frac{V_t}{R_s} + \frac{V_t}{\frac{1}{g_m}} \quad \underline{R_{out} = 30.86}$$

D:

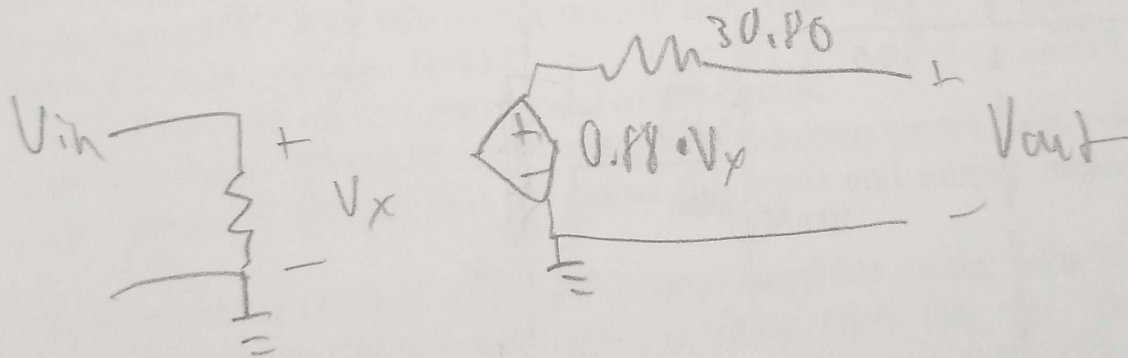

E: There is no term because $R_{in} = 0$.