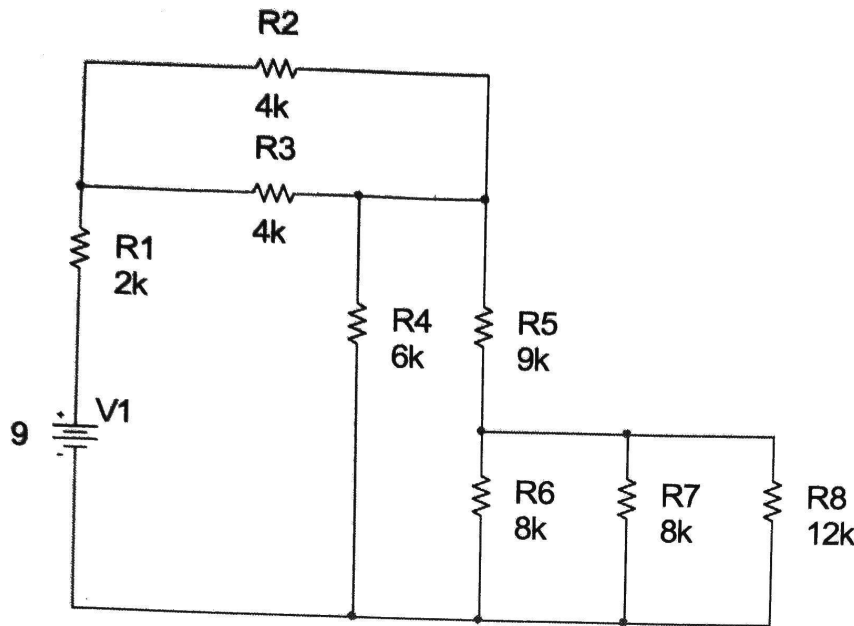


## 1) Equivalent Circuits/Circuit Reduction

Saad Ahmed




In the above circuit determine:

1.1: The equivalent resistance seen by the voltage source.

1.2 Find the current through the voltage source.

1.3 Find the voltage across R8.

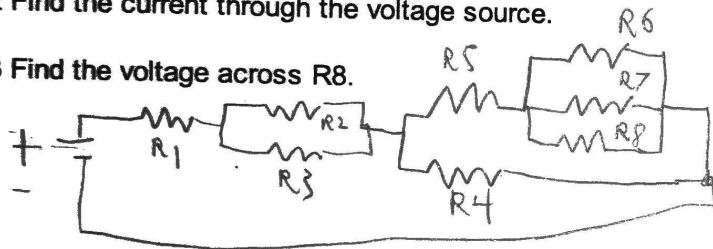

$$\frac{1}{R_{678}} = \frac{1}{R_6} + \frac{1}{R_7} + \frac{1}{R_8} = \frac{1}{8k} + \frac{1}{8k} + \frac{1}{12k} ; R_{678} = 3k\Omega$$

$$R_5 + R_{678} = 12k\Omega \quad \frac{1}{R_{45678}} = \frac{1}{R_{5678}} + \frac{1}{R_4} ; R_{45678} = 4000\Omega$$

$$\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3} ; R_{23} = 2000\Omega ; R_{12345678} = R_1 + R_{23} + R_{45678} = 8000\Omega$$


$$\boxed{1.1: 8000\Omega}$$

$$1.2: V = RI \quad \frac{V}{R} = I \quad \frac{9V}{8000\Omega} = I \quad \boxed{I = 1.125mA}$$

$$1.3: V_{R45678} = \frac{V_1 (4000)}{8000} = \frac{1}{2} V_1 = 4.5V ; V_{678} = \frac{V_{45678} (3k\Omega)}{12k\Omega}$$

$$V_{678} = \frac{1}{4} V_{R45678} = \frac{4.5}{4} = 1.125V \quad V_{678} = V_{R8} \text{ (parallel)} , \quad \boxed{V_{R8} = 1.125V}$$

## 2) Node/Mesh Analysis

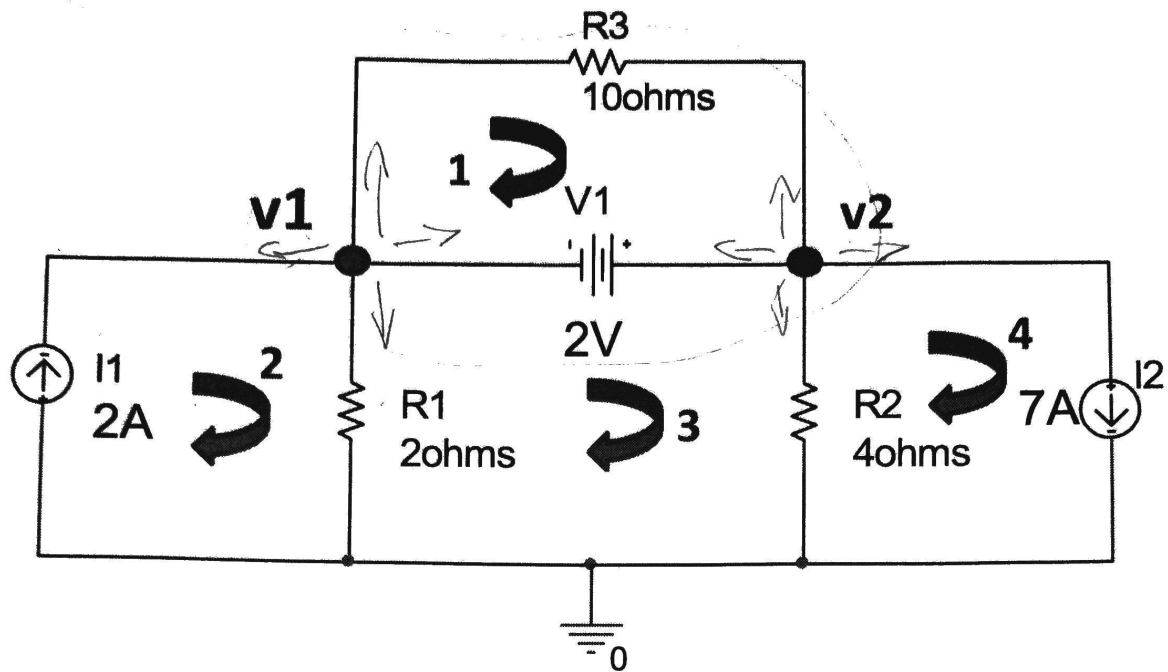

2.1: Find the node voltages  $V_1$  and  $V_2$  using nodal analysis.

2.2: Using Mesh Analysis, find the voltage across  $R_2$ .

$$2.1: V_2 - V_1 = 2V$$

$$\frac{V_1}{R_1} - 2A + \frac{V_2}{R_2} + 7A = 0$$

$$\begin{bmatrix} \frac{1}{2} & \frac{1}{4} \\ -1 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -5 \\ 2 \end{bmatrix}$$

$$\boxed{V_1 = -7.33V}$$

$$\boxed{V_2 = -5.33V}$$

$$A^{-1} \cdot B = X = \begin{bmatrix} -7.33 \\ -5.33 \end{bmatrix}$$

$$2.2: i_1 R_3 + 2V = 0$$

$$i_3 R_1 - 2A - 2V + i_3 R_2 - 7A = 0$$


$$\begin{bmatrix} 10 & 0 \\ 0 & 6 \end{bmatrix} \begin{bmatrix} i_1 \\ i_3 \end{bmatrix} = \begin{bmatrix} -2 \\ 11 \end{bmatrix}$$

$$A^{-1} \cdot B = X = \begin{bmatrix} -0.2 \\ 5.66 \end{bmatrix}$$

$$V_{R_2} = (i_3 - 7A) R_2$$

$$\boxed{V_{R_2} = -5.33V}$$

## 3) Superposition

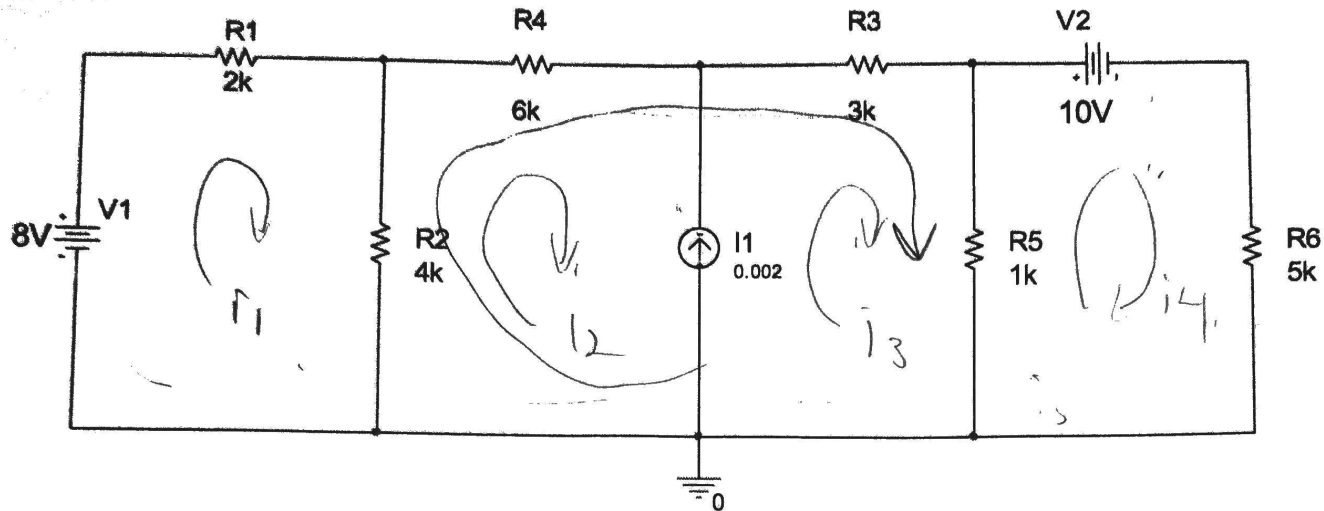

3.1: Use any method in the parentheses to determine the voltage across R2 (node, mesh, circuit reduction, source transformation)

3.2: Find  $V_{R2}$  using superposition. (For each source, draw the schematic).

3.1 Mesh Analysis:  $i_3 - i_2 = 0.002 \text{ A}$

$$i_1 R_2 + (-8\text{V}) + i_1 R_1 - i_2 R_2 = 0$$

$$i_2 R_2 - i_1 R_2 + i_2 R_4 + i_3 R_3 + i_3 R_5 - i_4 R_5$$

$$i_4 R_5 - i_3 R_5 + 10\text{V} + i_4 R_6 = 0$$

$$i_1 6\text{k} - i_2 4\text{k} = 8$$

$$i_2 10\text{k} - i_1 4\text{k} + i_3 4\text{k} - i_4 1\text{k} = 0$$

$$i_4 6\text{k} - i_3 1\text{k} = -10$$

$$i_3 - i_2 = 0.002$$

$$A^{-1} \cdot B = \begin{bmatrix} 0.001 \\ -3.58 \\ 0.0016 \\ -0.0014 \end{bmatrix}$$

$$V_{R2} = (i_1 - i_2) R_2$$

$$V_{R2} = 0.0011 - (-3.58 \times 10^{-4}) R_2$$


$$V_{R2} = \boxed{5.81 \text{ V}}$$

$$\begin{bmatrix} 6000 & -4000 & 0 & 0 \\ -4000 & 10000 & 4000 & -1000 \\ 0 & 0 & -1000 & 6000 \\ 0 & -1 & 1 & 0 \end{bmatrix}$$

$$\begin{bmatrix} 8 \\ 0 \\ 10 \\ 0.002 \end{bmatrix}$$

A


8V source:

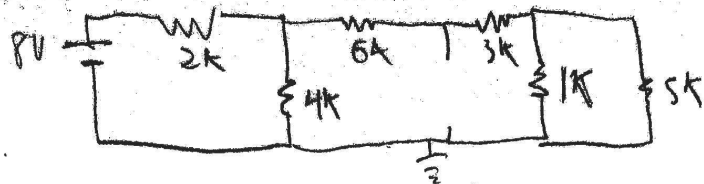


Current reduction:  $\left(\frac{1}{1k} + \frac{1}{5k}\right)^{-1} + 3k + 6k = R_{\text{right hand}} = 9833.33 \Omega$

right hand  $\left(\frac{1}{R_{\text{right hand}}} + \frac{1}{4k}\right)^{-1} = R_{\text{bottom}} = 2843.37 \Omega$

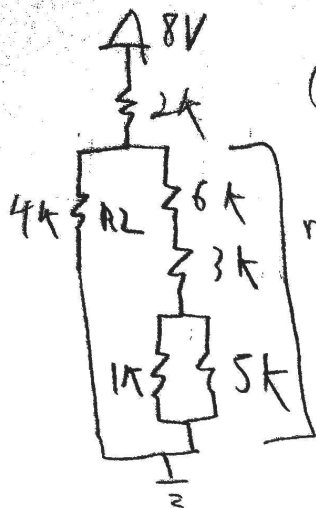$\frac{8V (R_{\text{bottom}})}{R_{\text{bottom}} + 2k} = V_{R2} = 4.70 V$



10V source:

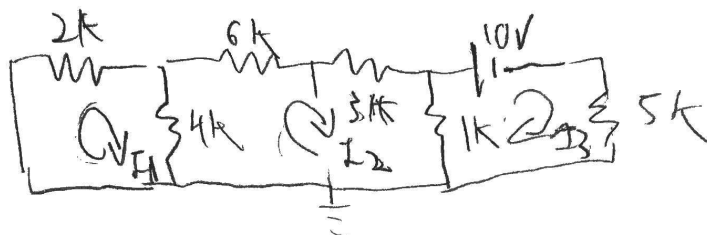

Meth Analysis:

$I_1 2k + I_1 4k - I_2 4k = 0$

$I_2 4k - I_1 4k + I_2 6k + I_2 3k + I_2 1k - I_3 1k = 0$

$I_3 1k - I_2 2k + 10V + I_3 5k = 0$

$\begin{cases} I_1 6k - I_2 4k = 0 \\ I_2 14k - I_1 4k - I_3 1k = 0 \\ I_3 6k - I_2 1k = -10V \end{cases}$


$\begin{bmatrix} 6000 & -4000 & 0 \\ -4000 & 14000 & -1000 \\ 0 & -1000 & 6000 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ -10 \end{bmatrix}$

$A^{-1} \cdot B = \begin{bmatrix} -9.95 \times 10^{-5} \\ -1.49 \times 10^{-4} \\ -0.00169 \end{bmatrix}$

$V_{R2} = (I_1 - I_2) R_2$

$V_{R2} = 0.199 V$

3.2 I, current source:

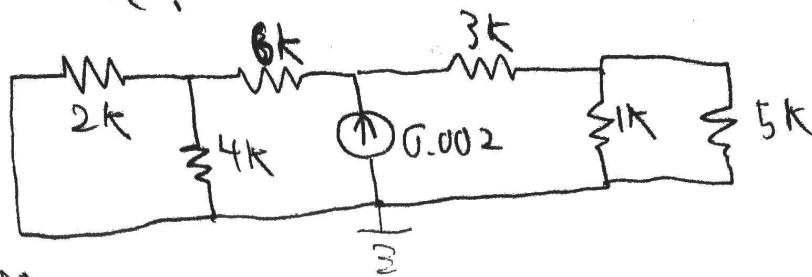

Circuit Reduction



3833.33 Mesh Analysis:

Definition:  $i_3 - i_2 = 0.002 \text{ A}$

$$i_1 6k - i_2 4k = 0$$

$$i_2 10k - i_1 4k + i_3 (3833.33) = 0$$

$$\begin{bmatrix} 6000 & -4000 & 0 \\ -4000 & 10000 & 3833.33 \\ 0 & -1 & 1 \end{bmatrix}$$

$$A^{-1} \cdot B = X = \begin{bmatrix} -4.577 \times 10^{-4} \\ -6.87 \times 10^{-4} \\ 0.0013 \end{bmatrix}$$

$$VR_2 = (i_1 - i_2) R_2$$


$$VR_2 = 0.91544 \text{ V}$$

Final:  $10V_{\text{source}} + 8V_{\text{source}} + 0.002 \text{ A}_{\text{source}} = VR_2$



$$0.199 + 4.700 + 0.91544 = 5.81 \text{ V} = VR_2$$
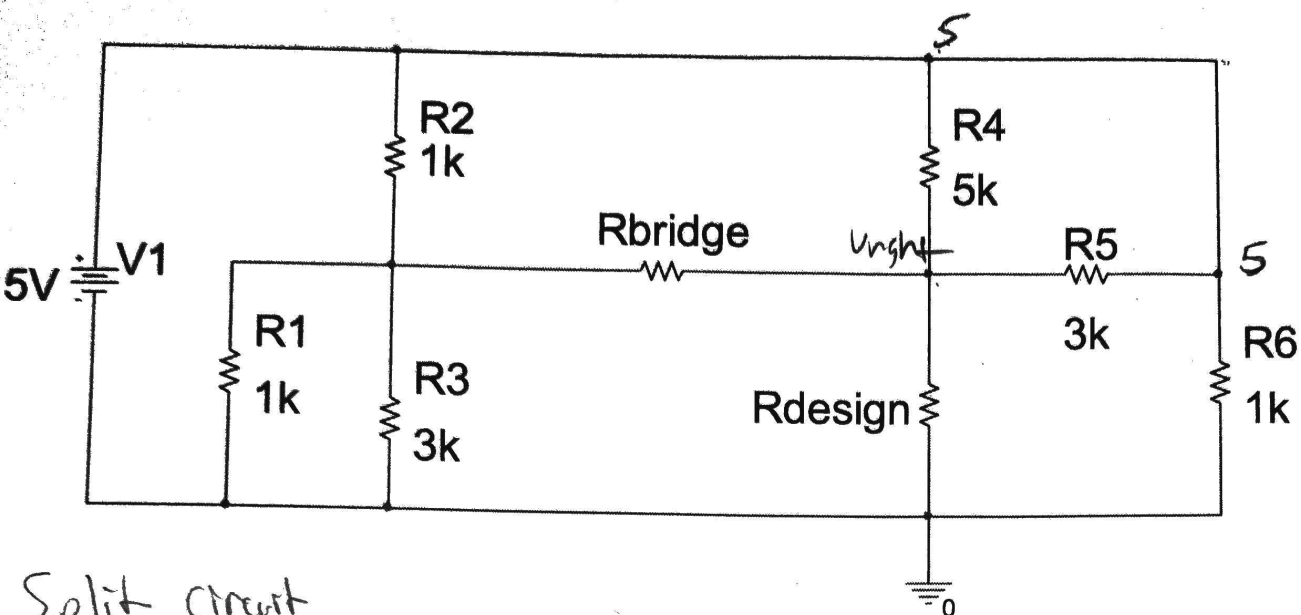
# Bridge Circuit

Find the value of  $R_{design}$  so the bridge is balanced (no current through  $R_{bridge}$ ).




Split circuit

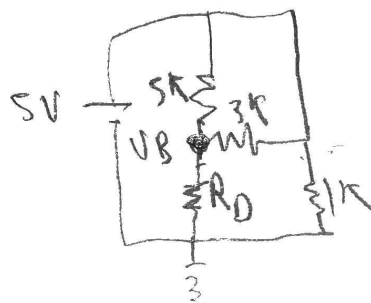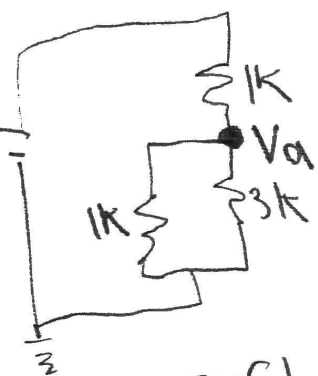

Find  $R_{design}$  for  $V_a = V_B$


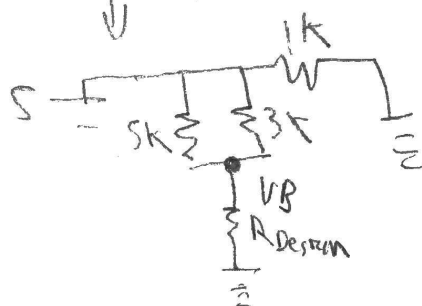
$$V_a = \frac{5V \left( \frac{1}{1000} + \frac{1}{3000} \right)^{-1}}{\left( \frac{1}{1000} + \frac{1}{3000} \right)^{-1} + 1000} = 2.14V$$



$$V_B = \frac{5(R_D)}{\left( \frac{1}{5000} + \frac{1}{3000} \right)^{-1} + R_D}$$

$$2.14 = \frac{5(R_D)}{1875 + R_D}$$

$$2.14 R_D + 4012.5 = 5 R_D$$

$$4012.5 = 2.857 R_D$$

$$R_{design} = 1406.25 \Omega$$