

1) Short Answers (22 points)

Question 1 (5 points)

T / F Ideal diodes consume no power

T / F Minimizing ripple voltage improves efficiency in rectifier circuits

T / F It is possible that the output voltage due to bias terms can be negative

T / F The real (not ideal) input resistance of the OP27 is in the 1-10Meg Ω range

T / F For a Miller Integrator, when the input is DC, the output is zero.

Question 2 (2 points)

During the ‘diode off’ time of a rectifier circuit, the load voltage is $V_L = V_o e^{-\frac{t}{\tau}}$ where $\tau = RC$. What relationship must hold for the ripple voltage to be considered small.


Question 3 (4 points)

For a two input amplifier circuit, two measurements were taken

$V_1 = 1.9\text{V}$ and $V_2 = 2.1\text{V}$, $V_{\text{out}} = 5\text{V}$

$V_1 = 3.9\text{V}$ and $V_2 = 4.1\text{V}$, $V_{\text{out}} = 5.2\text{V}$

Determine the common mode gain and the differential gain.

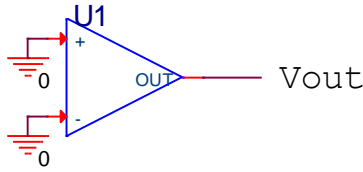Question 4 (2 points)

When considering real amplifiers, briefly describe why the output of the above op-amp is at the saturation voltage ($V_{out} = V_{sat}$) when both the inputs are grounded.

Question 5 (2 points)

Under what conditions is a Taylor's series approximation reasonable in rectifier analysis?

Question 6 (4 points)

For a slew rate of $4 \text{ V}/\mu\text{s}$, what is the maximum frequency of a voltage follower with a triangle wave input $V_{\text{peak-to-peak}} = 10\text{V}$ such that the output appears as expected.

Question 7 (3 points)

When considering ideal balanced difference amplifiers


The common mode gain is ideally, $A_{CM} = \underline{\hspace{2cm}}$

The common mode rejection ratio is ideally, $CMRR = \underline{\hspace{2cm}}$


Why is that unlikely with real amplifier circuits?

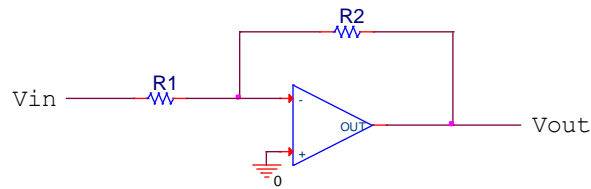2) Op-amp circuits (14 points)


All op-amps in this problem have power supplies of +9/-9V.



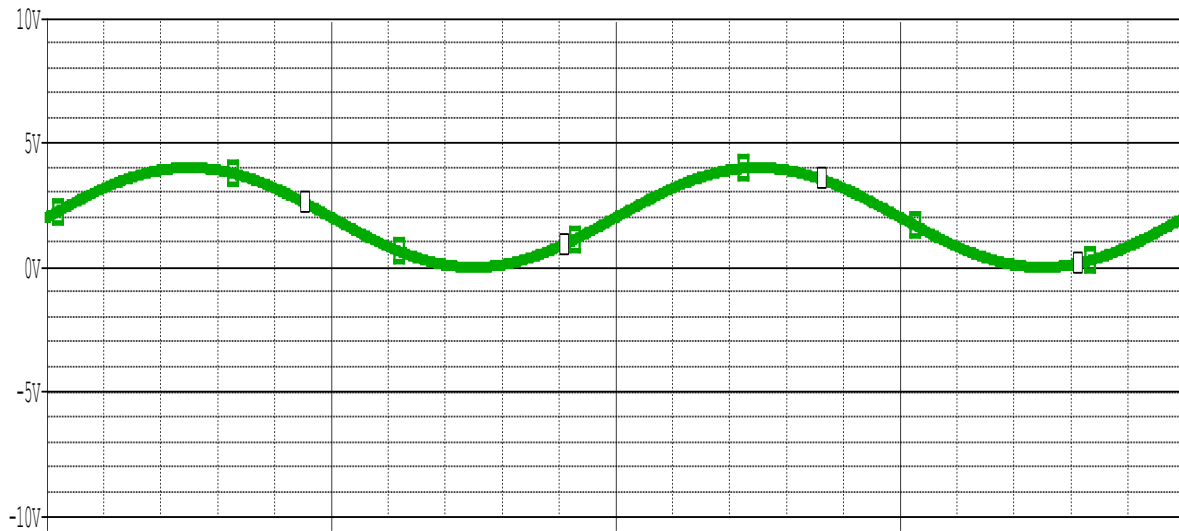
For $R1 = 1\text{k}\Omega$, $R2 = 2\text{k}\Omega$ and $V_{in} = 2\sin(1000t) + 2$ [V] (shown below), sketch the output voltage as a function of time on the same plot. Clearly label the minimum and maximum voltages. (6 pts)



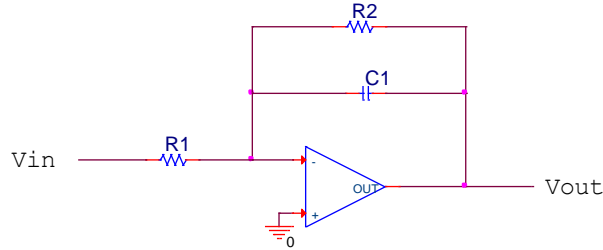All op-amps in this problem have power supplies of +9/-9V.




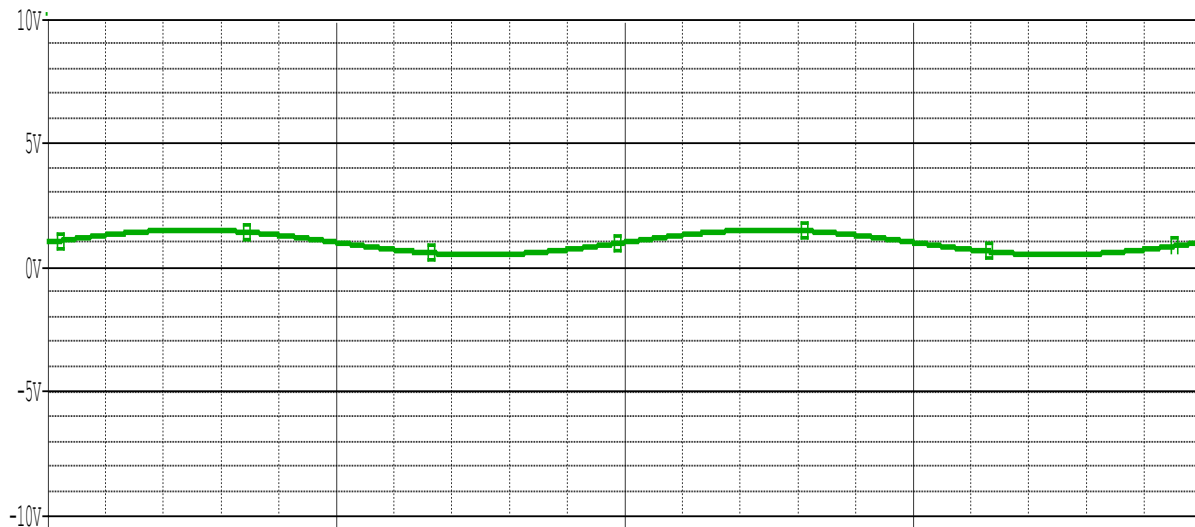For $R1 = 1\text{k}\Omega$, $R2 = 1\text{k}\Omega$, $C1 = 0.1\mu\text{F}$ and $V_{in} = 0.2\sin(1000t) + 1$ [V] (shown below), sketch the **steady state** output voltage as a function of time on the same plot. Clearly label the minimum and maximum voltages. (8 pts)




3) Amplifier Transfer Functions (16 points)

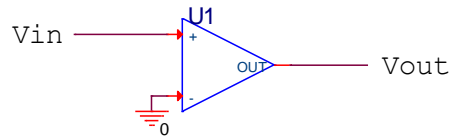
- a) The op-amps in the following two circuits have an internal gain of 10^5 V/V and a GBP of 1 MHz. For both the following two circuits, sketch the Bode magnitude plot. Label the axis as appropriate. Both plots should be on the same axis. Clearly indicate the circuit that corresponds to the plot. (8 pts)




Circuit A

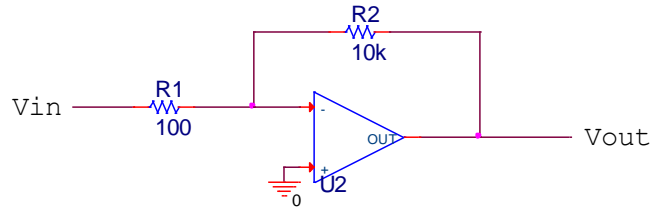


Circuit B

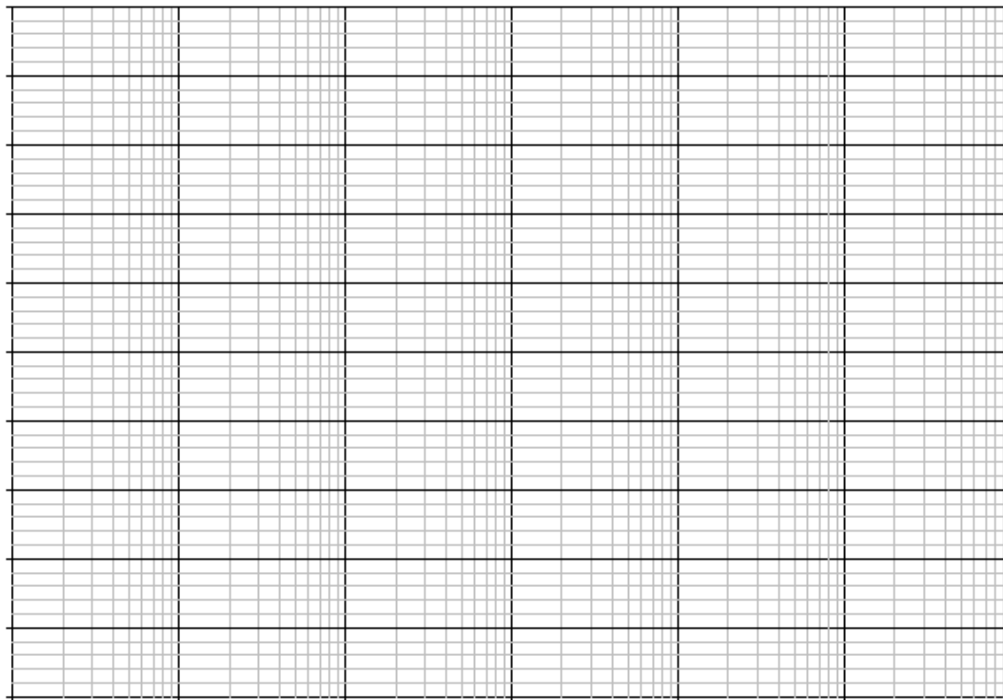

log(f)

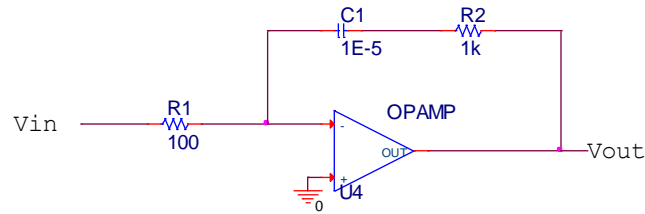

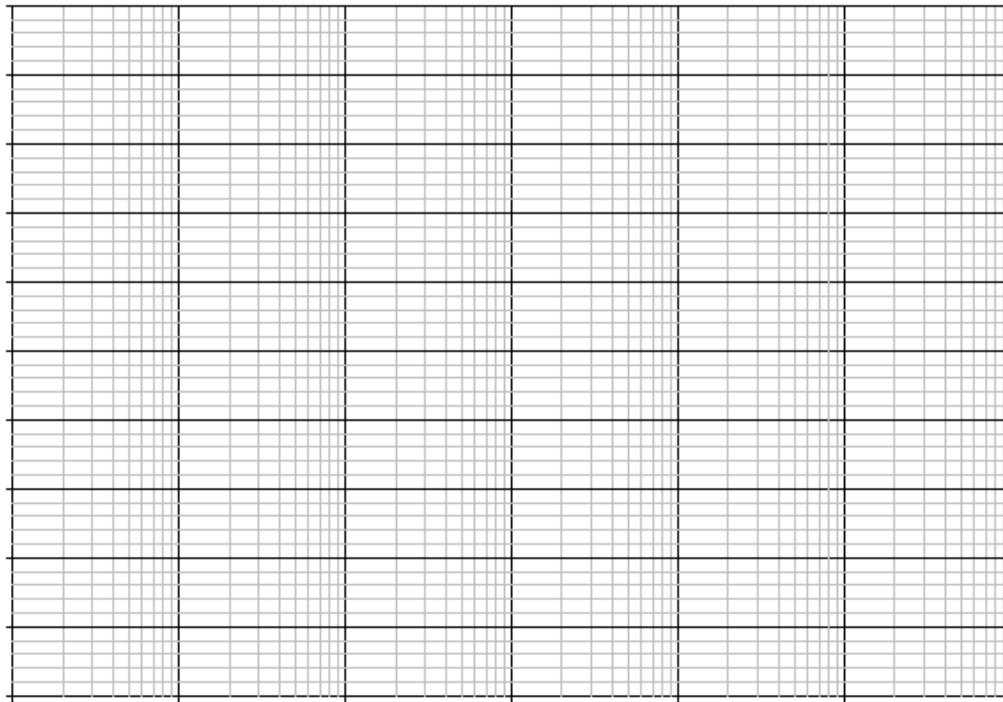
- b) Determine the transfer function for the above circuit and sketch the Bode magnitude plot. Label the axis as appropriate. (GBP is not part of this problem.) (8 pts)




$\log(\omega)$

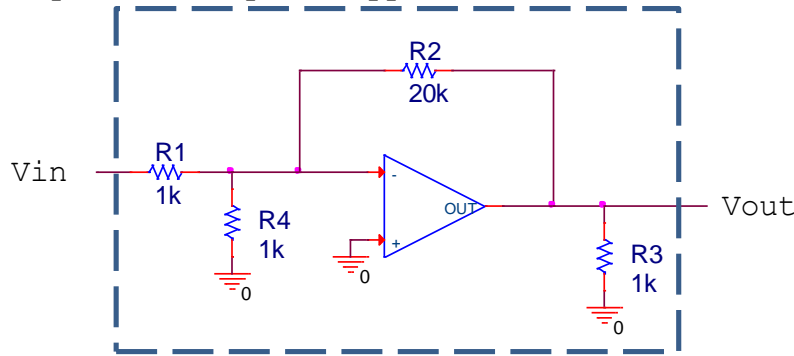4) Op-amp circuits and Dependent Source models (12 points)


All op-amps in this problem have power supplies of +9/-9V.



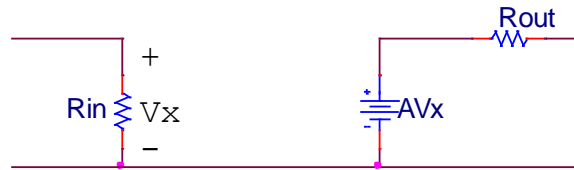
- a) For the indicated dashed box, identify R_{in} (looking 'in' from the 'left'), R_{out} (looking 'in' from the 'right') and the circuit gain, $A = V_{out}/V_{in}$. Add those numerical values to the following dependent source circuit. (6 pts)



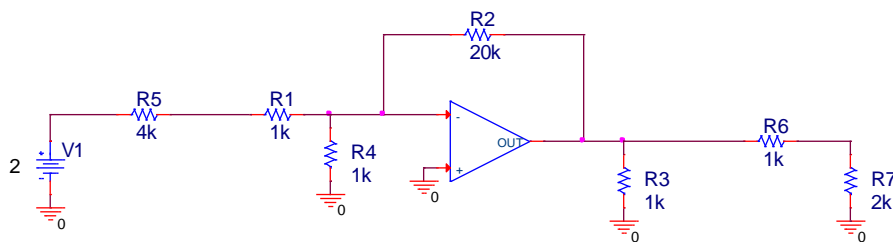- b) Determine V_{R7} for the following circuit. (6 pts)



5) Finite Internal Gain (10 points)

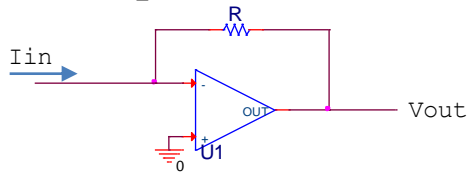

The above amplifier circuit is a transresistance amplifier with the transfer function defined as

$$H(s) = \frac{V_{out}(s)}{I_{in}(s)}.$$

- a) If the op-amp is ideal, determine the transfer function. (2 pts)


- b) If the op-amp has finite internal gain, A_{int} , determine the transfer function. As part of your analysis, include a schematic of the circuit, replacing the op-amp with the dependent source model. (6 pts)

- c) When $R = 1\text{k}\Omega$, $A_{int} = 10^5 \text{ V/V}$ and the op-amp has a GBP of 10 MHz, determine the approximate 3dB cutoff frequency. (2 pts)

6) DC Bias Characteristics (15 points)


The bias characteristics for the amplifier are

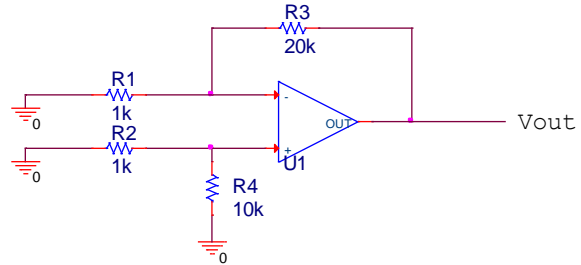- 1) $V_{DCOffset} = 4\text{mV}$
- 2) $I_{bias}^- = 5\mu\text{A}$
- 3) $I_{bias}^+ = 5\mu\text{A}$



- a) For each bias component, determine the output voltage. (3 pts each)





I_{bias}^+	[mV]
I_{bias}^-	[mV]
$V_{DCOffset}$	[mV]

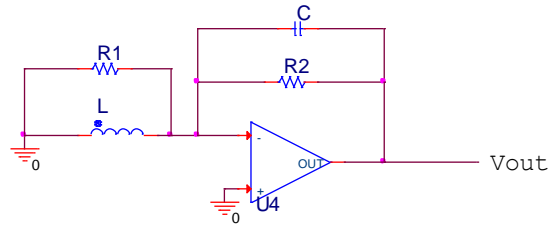


- b) For the above circuit, determine a symbolic expression for the output voltage due to the $V_{D\text{Offset}}$ bias term. (6 pts)

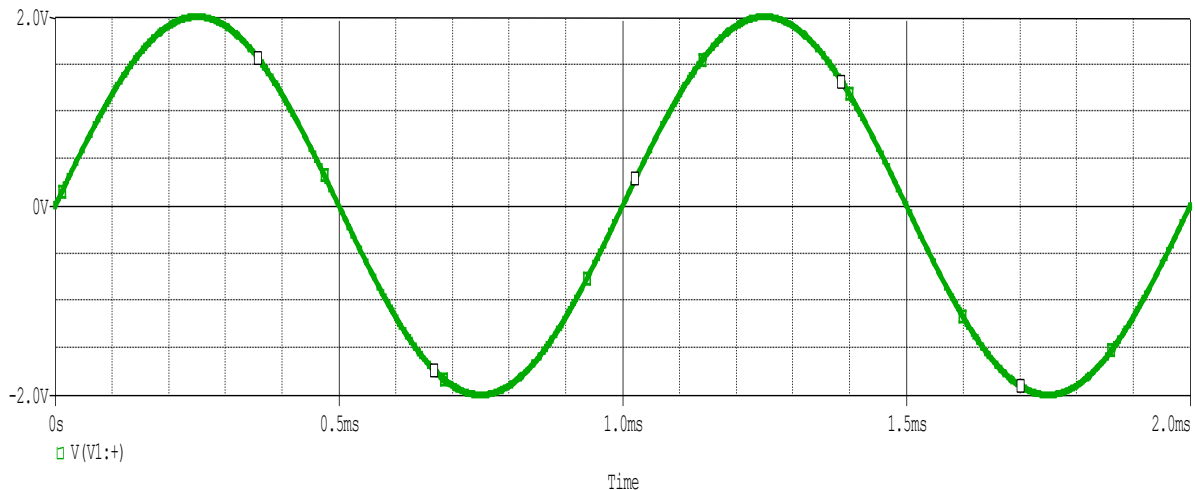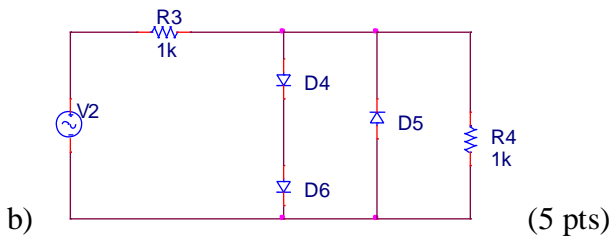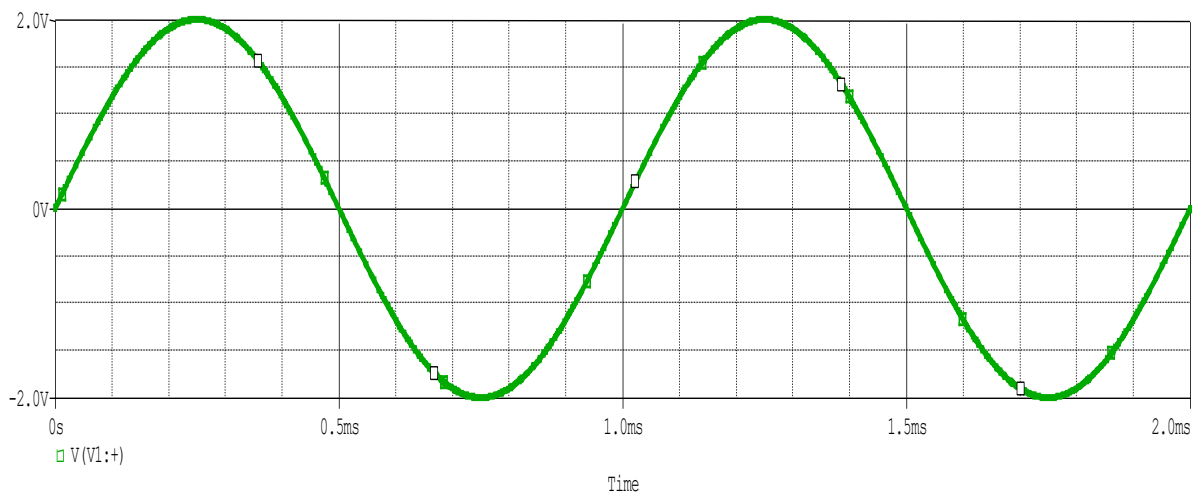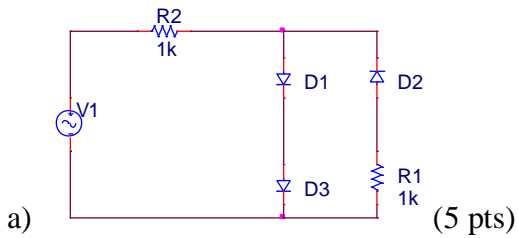7) Op-amp circuits and Dependent Source models (15 points)

All diodes on this page have a turn-on voltage of 0.5V. For each circuit and source voltage, plot the source current on the same graph. Label the maximum and minimum current values. (Pay attention to the voltage axis)



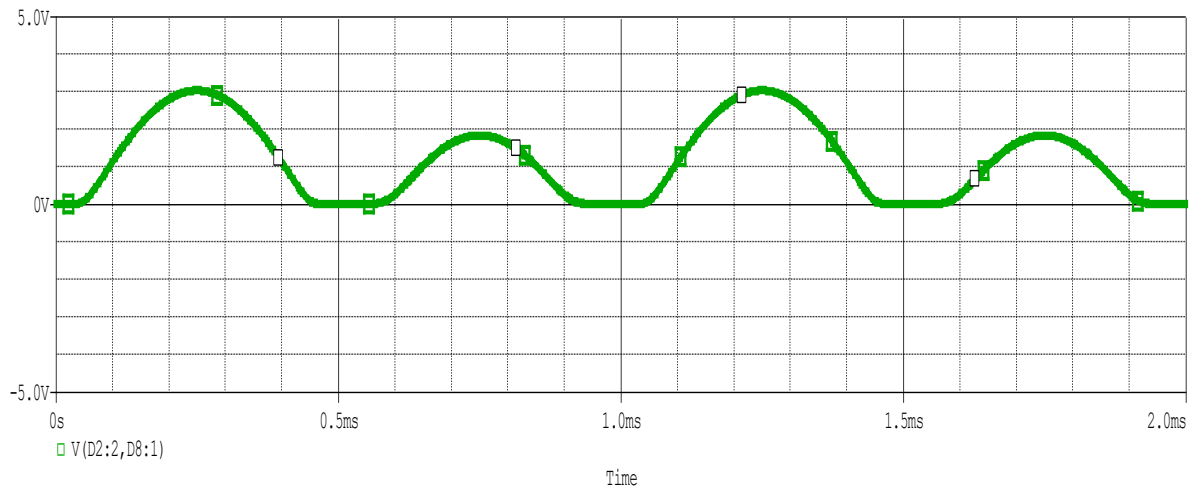
- c) Using diodes with $V_{\text{turn-on}} = 1\text{V}$, design a circuit that has the following output voltage. The source voltage is $5\sin(1000t)$. (5 pts)



8) Ideal Diodes – DC Analysis (14 points)


All diodes in this problem are ideal.

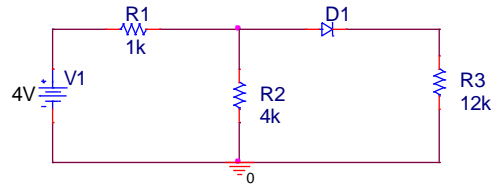- a) For a $V_{\text{turn-on}} = 1\text{V}$, determine the voltage across and current through the diode in the circuit shown to the right. (4 pts)




I_D	[mA]
V_D	[V]

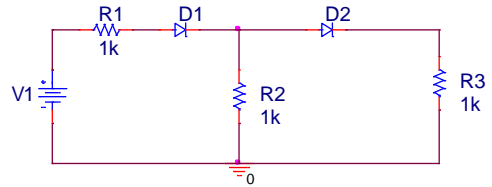- b) For a $V_{\text{turn-on}} = 2\text{V}$, determine the minimum source voltage to turn both diodes on. (4 pts)




V_{min}	[V]
------------------	-----

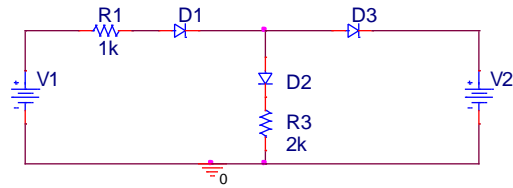

- c) For each diode having $V_{\text{turn-on}} = 1\text{V}$, $V1 = 5\text{V}$ and $V2 = 3\text{V}$, verify that guessing D1, D2 and D3 all on is a ‘bad’ guess. Be specific in your analysis. (6 pts)

9) Rectifiers (20 points)

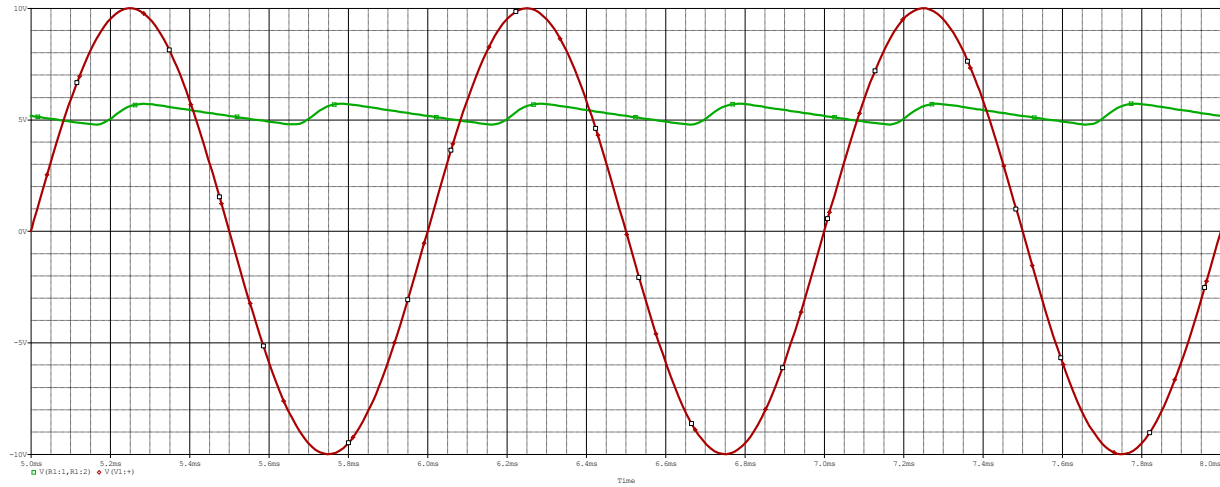


Dashed line: Source voltage

Solid line: Load voltage

x-axis: 5ms to 8ms

y-axis: -10V to 10V

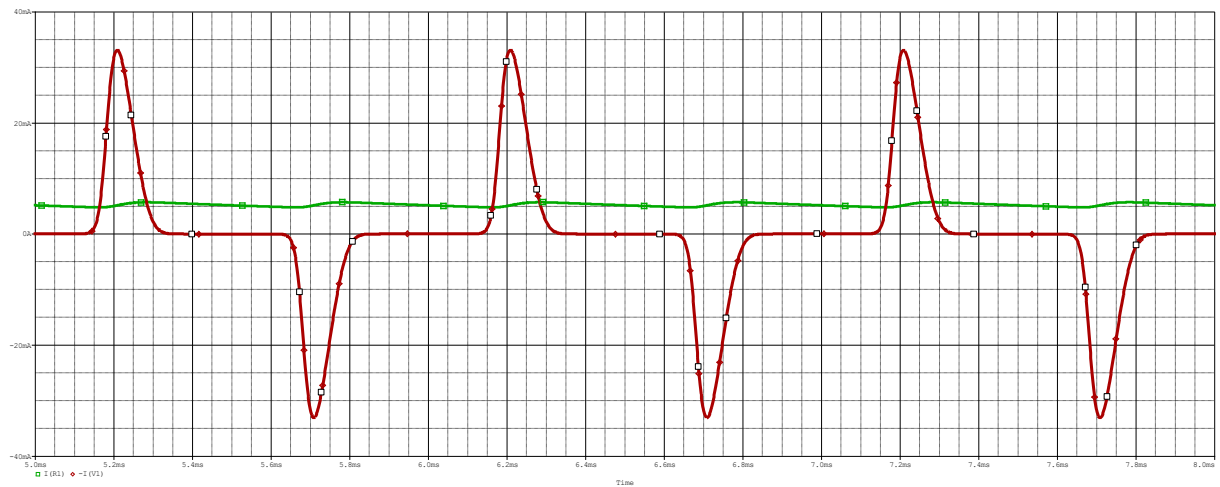

Dashed line: Source current

Solid line: Load current

x-axis: 5ms to 8ms

y-axis: -40mA to 40mA

The plots on the previous page were obtained from the simulation of a rectifier circuit, with the top plot being voltage plots and the bottom plot being current plots of the source and the load, respectively.

- a) Is the circuit a half-wave or full-wave rectifier? (1 pt) _____
- b) Estimate the turn-on voltage of a diode. (2 pts)
- c) Approximately determine the value of the load resistor. (1 pt)
- d) Approximately determine the value of the smoothing capacitor. (3 pts)
- e) Estimate the energy consumed by the load per cycle. (2 pts)
- f) Estimate the energy produced by the source per cycle. (3 pts)

